

Microprocessor System Design

Input / Output

Peripheral Interfacing

Omid Fatemi
(omid@fatemi.net)

Outline

- **Peripheral devices**
 - **Input devices**
 - **Output devices**
- **8 bit / 16-bit IO**
- **Simple Output device - interfacing LEDs**
- **Simple Input device - interfacing switches**

Peripheral

- **is an input and/or output device**
- **like a memory chip, it is mapped to a certain location (called the port address)**
- **unlike a memory chip, a peripheral is usually mapped to a single location**

Output Device

- like a memory chip, you can write to an output device
- You can write to a memory chip using the command `mov [bx], al`
- You can write to an output device using the command `out dx, al`

Input Device

- like a memory chip, you can read from an input device
- You can read from a memory chip using the command `mov al, [bx]`
- You can read from an input device using the command `in al, dx`

Memory mapped vs. peripheral

- Same instruction vs. independent instruction
- Entire address bus vs. part of address bus
- Same control signals vs. independent
- More IO ports vs. 65536 ports
- More commands and operations
- Uses memory space

Two formats for IN / OUT

Format 1

- **IN AL, port#**

Or

- **OUT port#, AL**

- **Example:**

```
– BACK:    IN AL,22H  
           CMP AL, 100  
           JNZ BACK
```

Format 2

- **MOV DX,port#
IN AL, DX**

Or

- **MOV DX, port#
OUT DX, AL**


8bit vs 16bit IO

- **8088 case:**
 - **MOV DX, 648H**
OUT DX, AX ;AX = 76A9H
 - **Address bus and ALE**
 - **Low byte (A9), IOW**
 - **Setup time**
 - **Address (649) and ALE**
 - **High byte (76), IOW**
 - **Setup time**
- **8086 case:**
 - **MOV DX, 648H**
OUT DX, AX ;AX = 76A9H
 - **Address bus and ALE**
 - **Word (76A9), IOW**
 - **Setup time**

Creating a Simple Output Device

- **Use 8-LED's**

Use 8 LED's

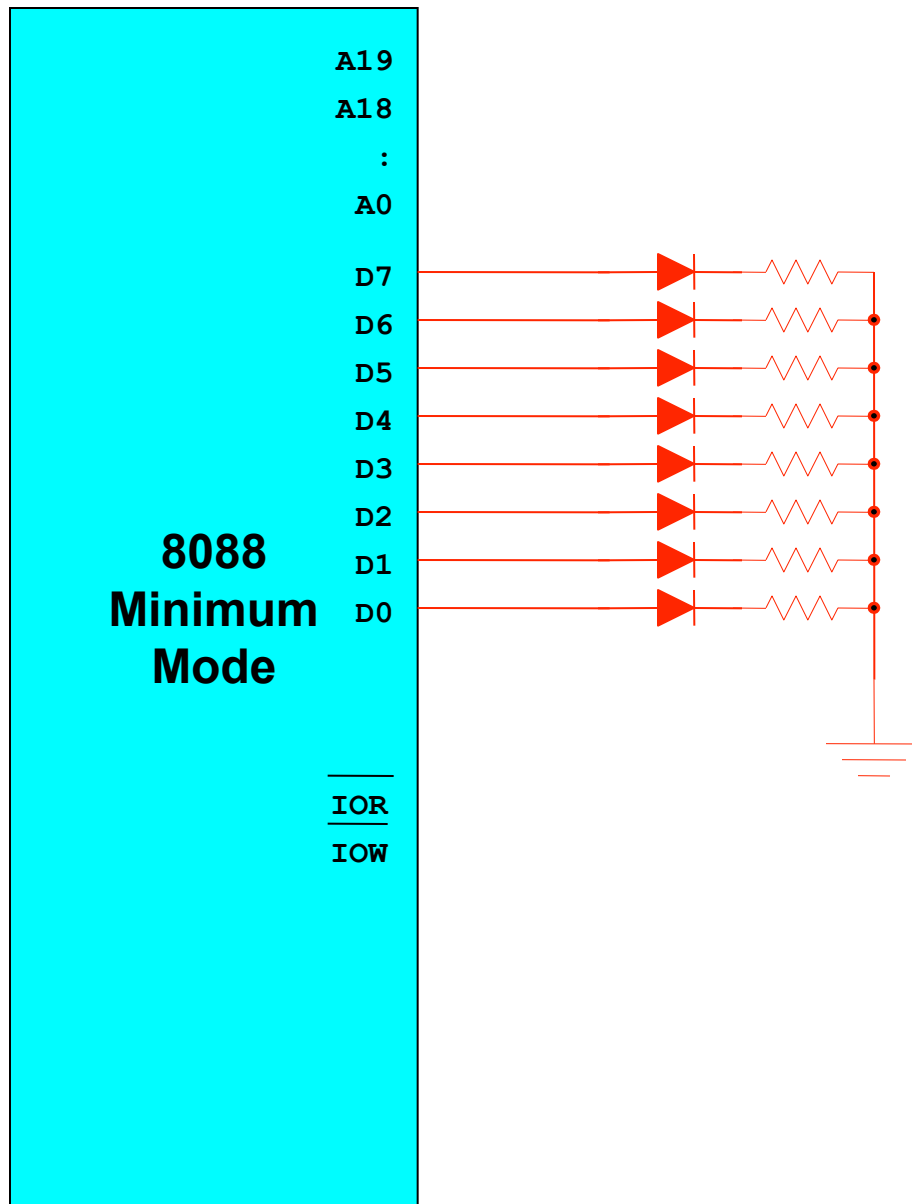


```
      :  
mov  al, 55  
out  dx, al  
      :  
      :  
      :
```

Creating a Simple Output Device

- **Use 8-LED's**
- **Use a chip and an address decoder such that the LED's will respond only to the command out and a specific address (let's assume that the address is F000)**

Use of 74LS245 and Address Decoder

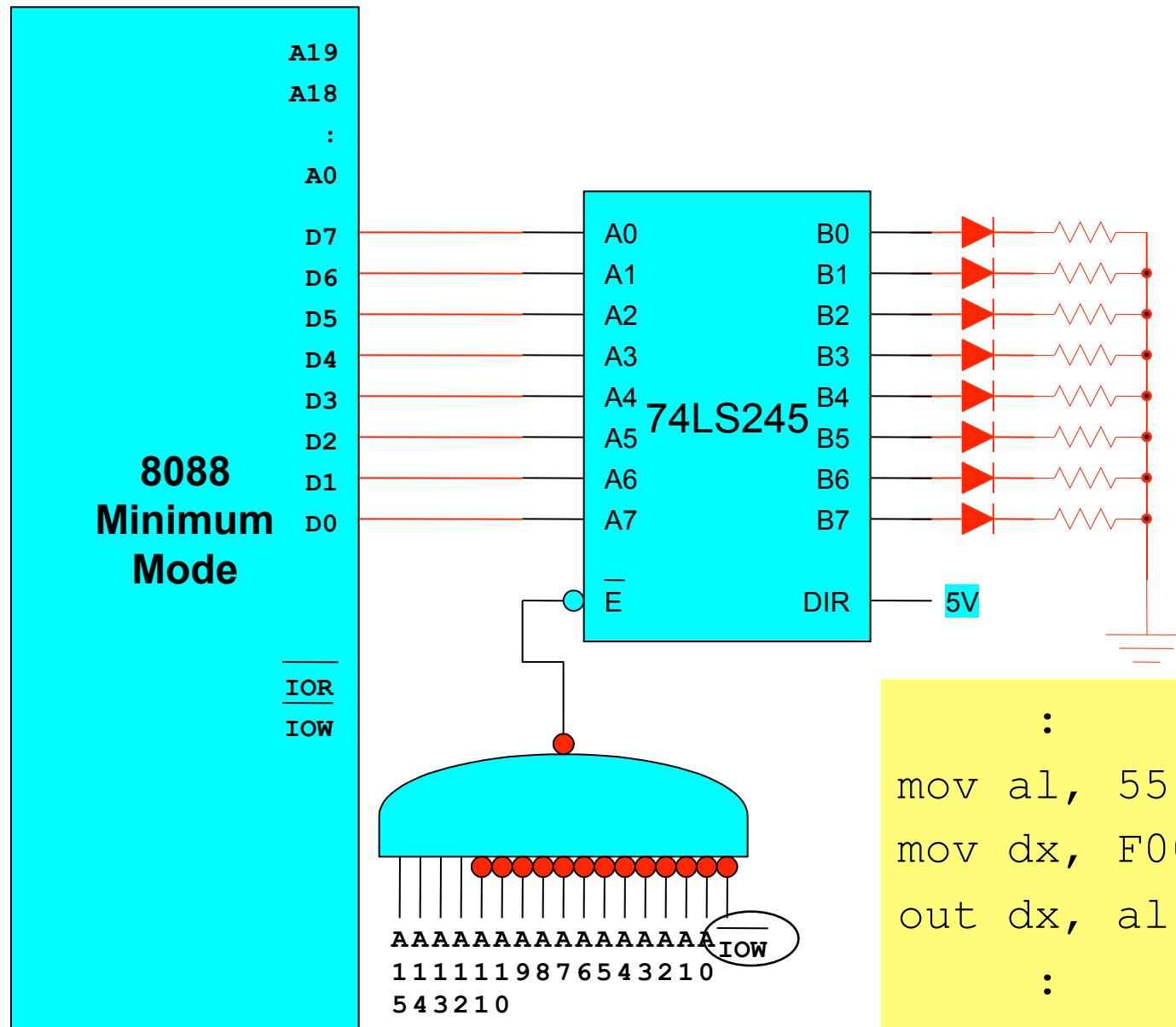


```

:
mov al, 55
mov dx, F000
out dx, al
:
  
```

Creating a Simple Output Device

- Use 8-LED's
- Loses the data
- Solution?
- Use a chip and an address decoder such that the LED's will not only respond to the command `out` and a specific address (let's assume that the address is `0x000`) but will also latch the data


Use of 74LS373 and Address Decoder

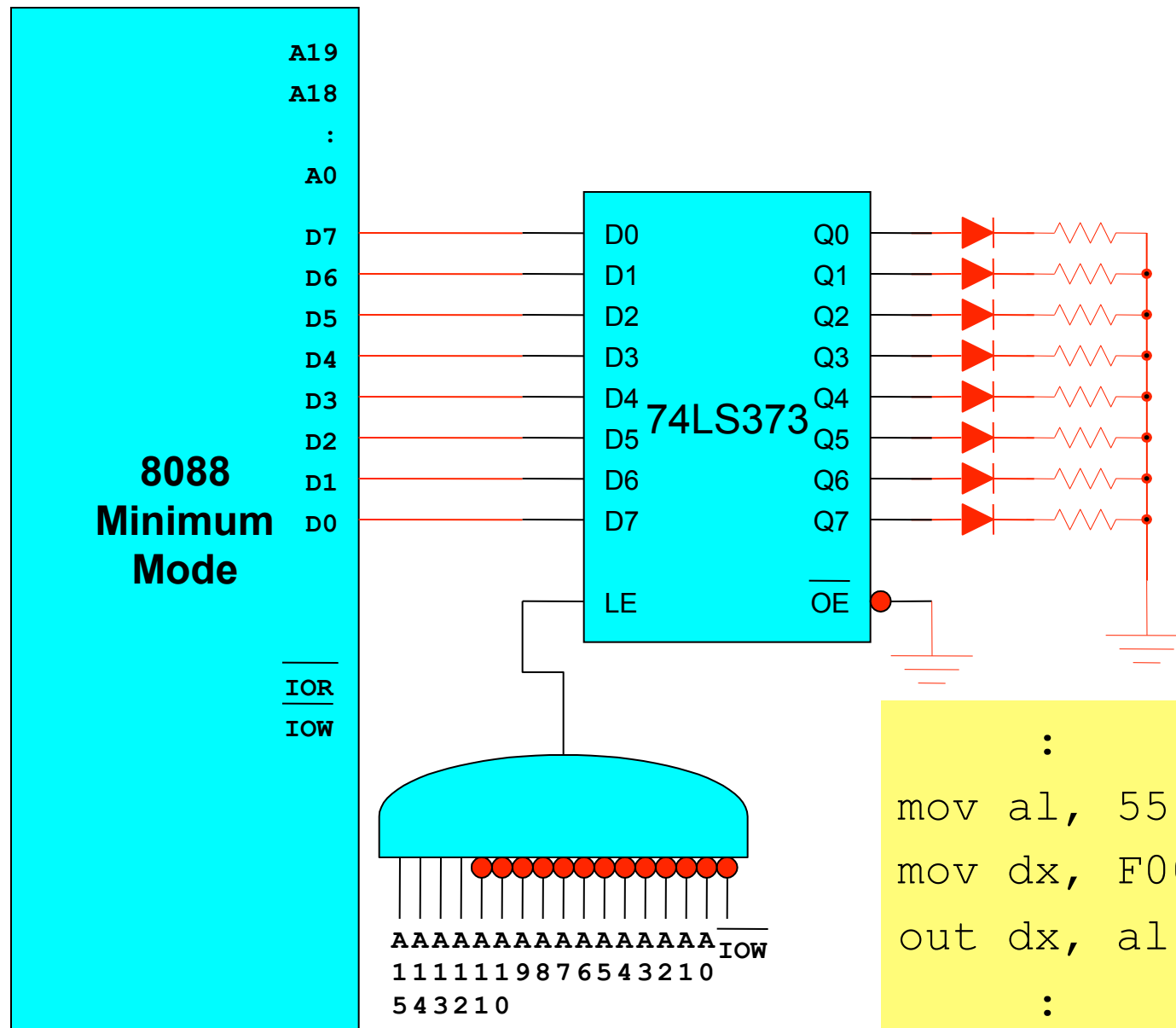

Creating a Simple Input Device

- **Use 8-Switches (keys)**
- **Use a chip and an address decoder such that the keys will be read only to the command in and a specific address (let's assume that the address is F000)**
- **How to interface a switch to computer?**


Use of 74LS245 and Address Decoder

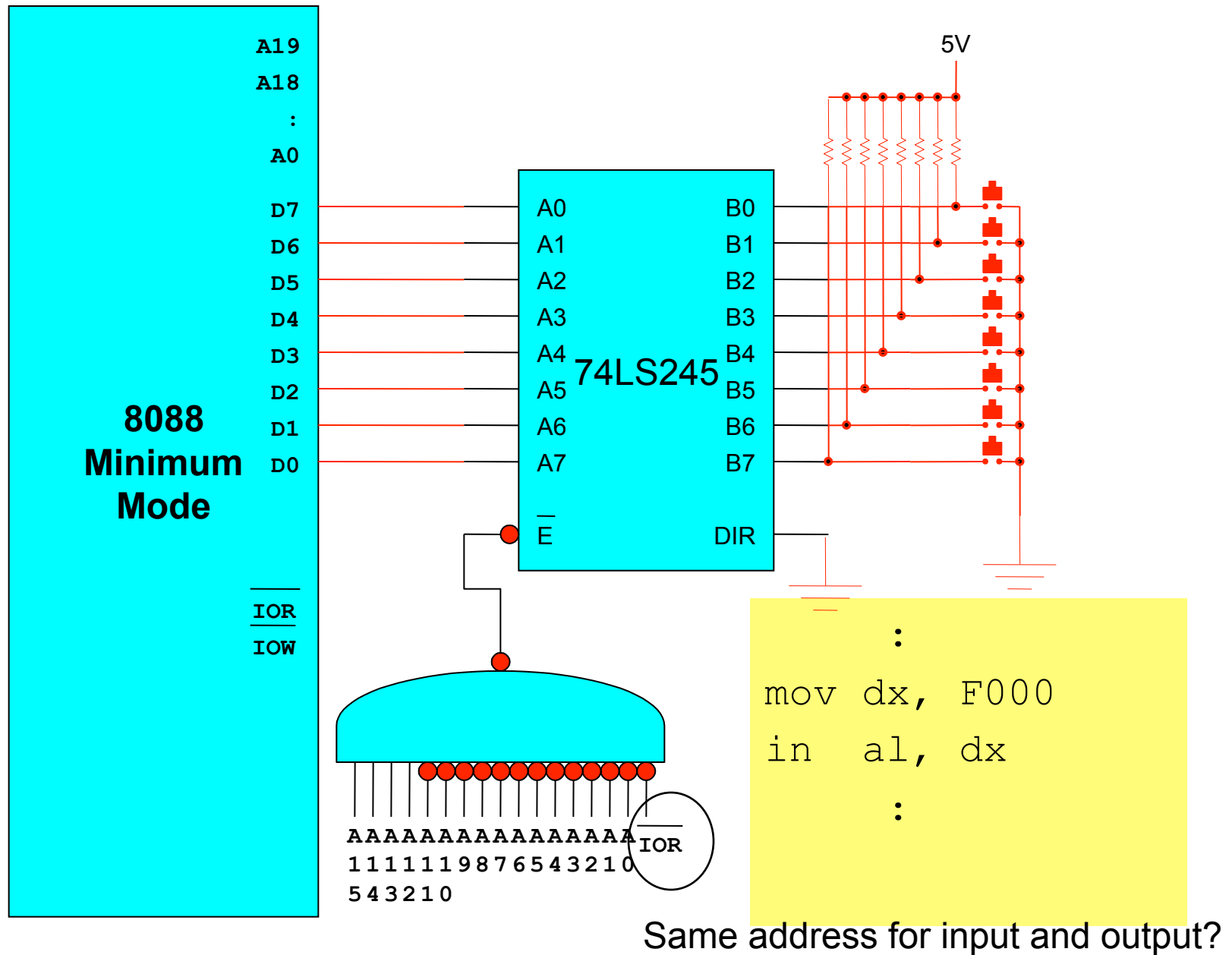


How do you know if a user has pressed a button?

- By Polling
- By Interrupt

Polling

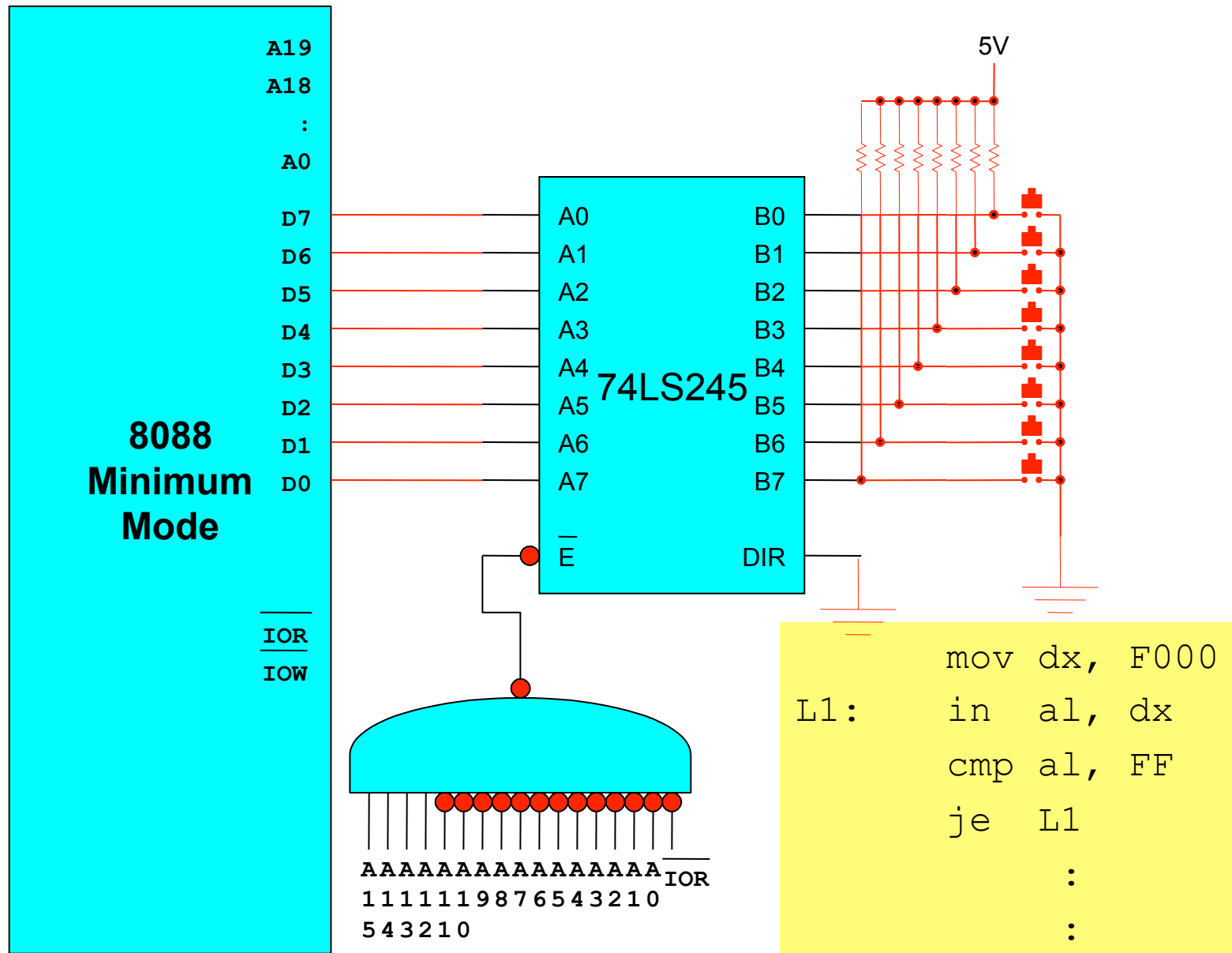

Output Port Design

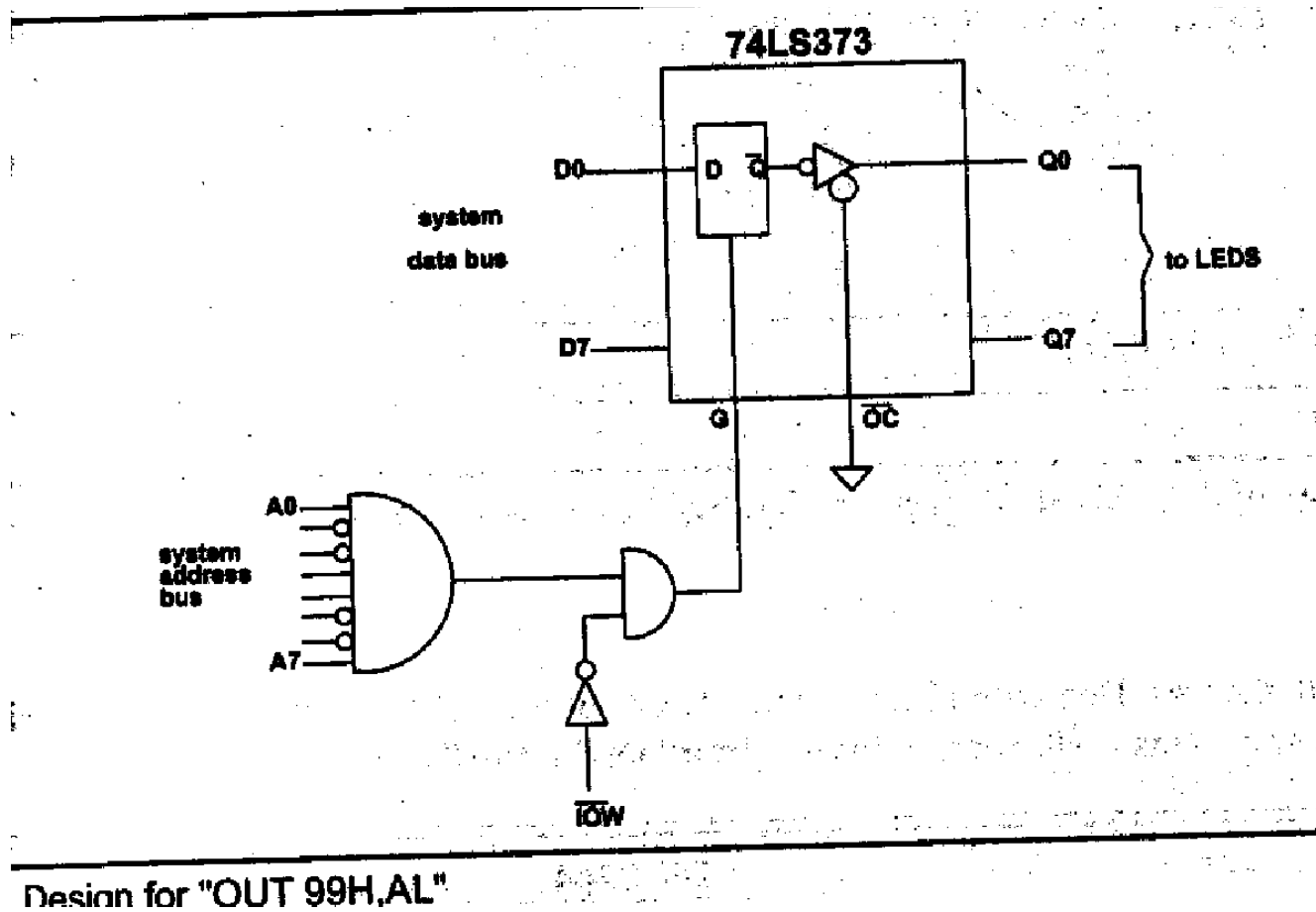

T1 – T4 of OUT 99H, AL ?

Input Port Design

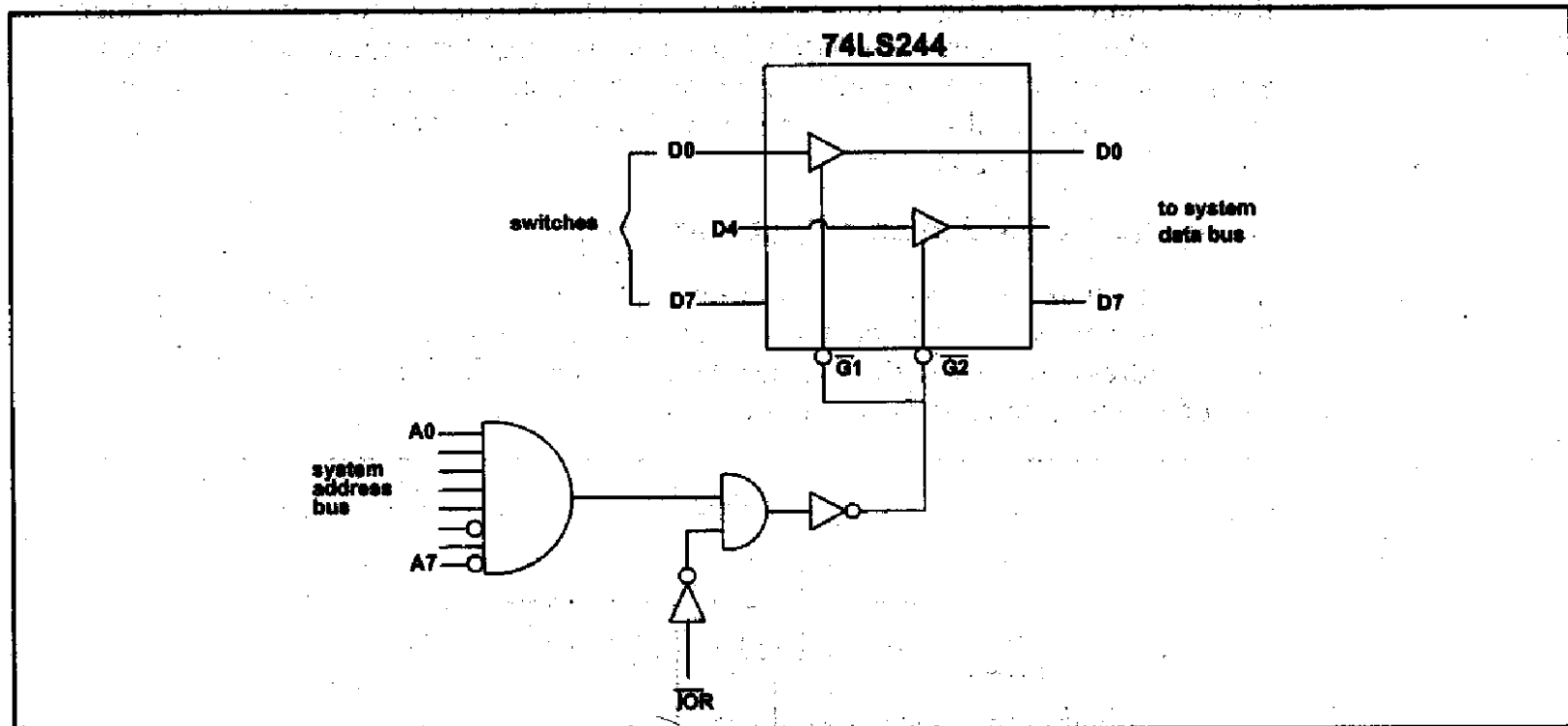


Figure 4-2. Design for "IN AL,5FH"

T1 – T4 of IN AL, 5FH ?