

CE233(CAD), Lecture 12:

Synthesis


Mehdi Modarressi

Department of Electrical and Computer Engineering,
University of Tehran

Reference

- See XST User Guide for a comprehensive list of synthesis guidelines for Xilinx FPGAs
- In particular study “XST HDL coding techniques” section

Digital systems design flow

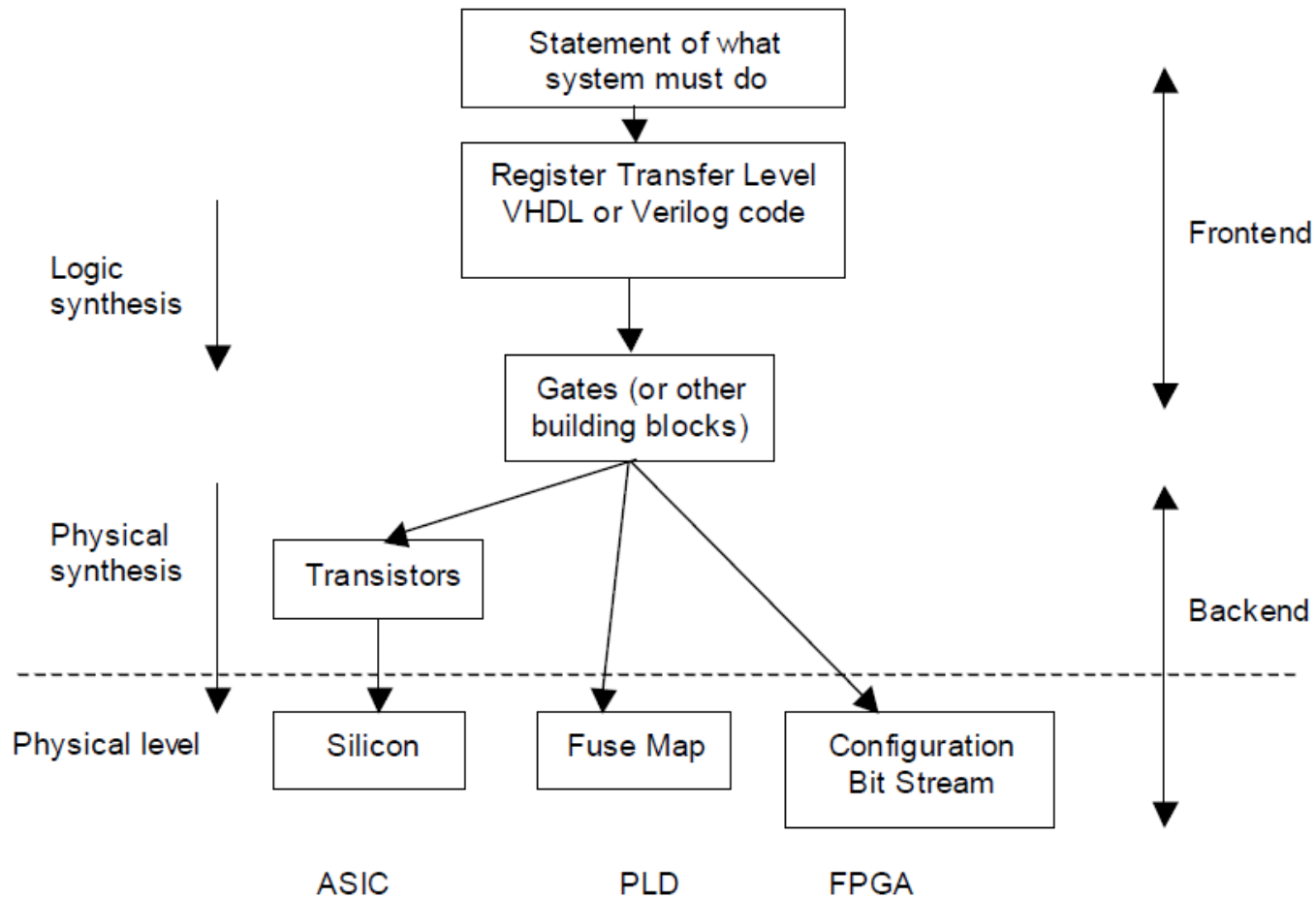

Digital systems design flow

- Once a hardware is described by VHDL, it is converted to a netlist (i.e. an interconnection) of basic building blocks (e.g. logic gates) by a synthesis tool
- Netlists are normally expressed in *EDIF* (Electronic Design Interchange Format)
 - An industry standard language
 - Used to easily port designs from one CAD tool to another
- See <http://www.iue.tuwien.ac.at/phd/minixhofer/node53.html> for a good reference for the EDIF format
- EDIF file format will be introduced more in the Lab. sessions

Implementation

- After synthesis, you run design implementation, which comprises the following steps:
 - **Translate** - merges the incoming netlists and constraints into a Xilinx design file.
 - **Map** - fits the design into the available resources on the target device based on the design and constraints
 - **Place and Route** - places and routes the design to the timing constraints.
 - **Generate Programming File** - creates a bitstream file that can be downloaded to the device.

Implementation Steps of Xilinx

- **Synthesis:** converting a design written in a HDL into a netlist (EDIF)
- **Netlist Translation** (NGDBUILD): takes user constraint file (UCF) and EDIF and translates them into Xilinx Native Generic Database (NGD) file that contains user constraints and FPGA parts
- **MAP** (MAP tool): mapping of a design into Xilinx FPGA components (outputs NCD file)
- **Place&Route** (PAR tool): PAR outputs an NCD file that contains complete place and route information
- Bitstream generation

Logic Synthesis

```
module x (a,b,c)
```

```
....
```

```
  Always@ (clk)
```

```
....
```


```
  assign a=b &c;
```

```
.....
```


```
endmodule;
```

In this lecture, we focus on logic synthesis


Logic synthesis

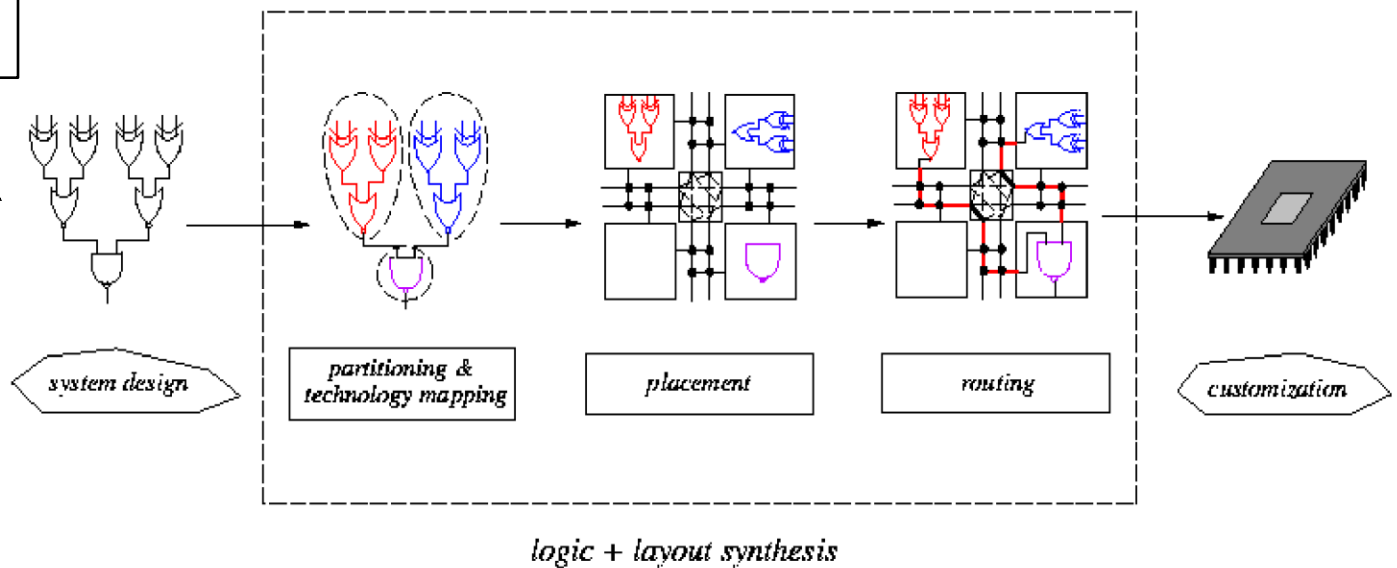

Logic Synthesis - Partitioning

 



Gate-level description

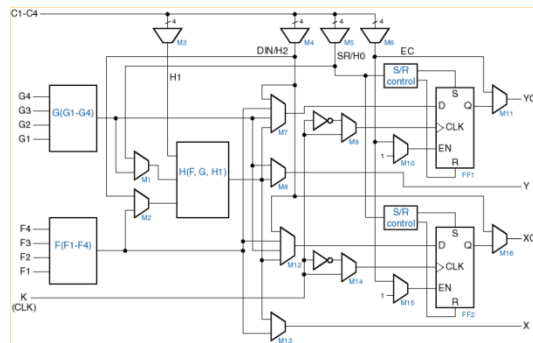

Technology Library (Target FPGA)
(just 2-input and 3-input LUTs)




Partitioned circuit

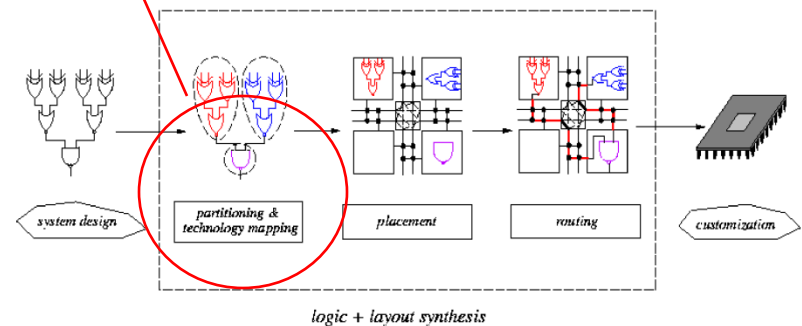 


Logic synthesis

- Behavioral coding used to be used for rapid prototyping
 - Now, we can get hardware out of it by synthesis tools
- Assembly coding vs. C/Java programming
- Gate-level modeling vs. behavioral modeling

Synthesizability

 

 - The VHDL subset that is synthesizable is tool specific
- Do not expect that your VHDL description is synthesizable with another tool!



Un-Synthesizable VHDL Subset

- Not supported: Ignored
 - No error, but ignored by the synthesis tool
 - Examples:
 - Initialization of variables or signals
 - Assert statements
 - Physical Type: Time
 - The synthesizer ignores the AFTER clause in expressions
 - Example: $x \leq y$ AFTER 100ns
- Not Supported: Illegal
 - Data types
 - Files, generic that are not integers

Synthesis

- General rules
 - General rules that determine how each piece of code is converted to hardware
- Hardware inferring
 - Specific ways of describing hardware in order to get a required component
 - Codes may be synthesized to unwanted hardware if the rules are not followed

Synthesis- General rules

- How to make simple hardware from VHDL structures
 - Operators
 - Signals and variables
 - Concurrent structures
 - Process statements
 -

VHDL -Hardware Correspondence

VHDL Construct	Hardware
Variables and Signals	Flip-flops, latches, wires
Arithmetic operators (+,-,*)	Adder, ALU, multiplier..
Logic operators	Gates
Relational operators	Comparator, ALU
Control Constructs (for,if-then, case,.....)	Decoders, Multiplexers, priority encoder, ..
Hierarchy Description	Hierarchical Hardware
Resolution Functions	Tri-state logic, wire-and, wire-or

Synthesis- Concurrent statements

- Concurrent statements are synthesized into gates and operators
- Only a subset of VHDL operators supported by synthesis tools
 - Supported operations: usually $+$, $-$, $=$, $>$, $<$, $<>$, abs , $*$
 - Generally, these operations are not supported for the real type, just for integer
- The designer must write VHDL description (behavioral or structural) of all un-supported operators: $/$, $**$
 - Many tools also accept very simple division operations
 - In Xilinx, you can generate a divider core by CORE Generator
- Specifying a range of integer is important for efficient synthesis
- In case of an integer operation, all hardware will be 32-bit wide

Efficient integer implementation

For Unsigned numbers:

USE `ieee.std_logic_unsigned.all`
and
signals (inputs/outputs) of the type
`STD_LOGIC_VECTOR`

OR

USE `ieee.std_logic_arith.all`
and
signals (inputs/outputs) of the type
`UNSIGNED`

For Signed numbers:

USE `ieee.std_logic_signed.all`
and
signals (inputs/outputs) of the type
`STD_LOGIC_VECTOR`

OR

USE `ieee.std_logic_arith.all`
and
signals (inputs/outputs) of the type
`SIGNED`

std_logic_arith

- The IEEE standard arithmetic package is an important package for arithmetic and logical functions
- The *std_logic_arith* defines two types: *SIGNED* and *UNSIGNED* unconstrained arrays of *std_logic*
- It overloads all arithmetic and relational operators of VHDL, for *SIGNED* or *UNSIGNED* and INTEGER
- With this overloading, we can use “+” for adding a signed or an unsigned *SIGNED* or *UNSIGNED* with an integer

Addition of Signed Numbers

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN      STD_LOGIC ;
           X, Y           : IN      SIGNED(15 DOWNT0 0) ;
           S               : OUT     SIGNED(15 DOWNT0 0) ;
           Cout, Overflow : OUT     STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : INTEGER;
BEGIN
    Sum<=X+Y;
    ...
END Behavior ;
```


The (UN)SIGNED Package

- The use of `std_logic_arith` requires specification of all objects as `SIGNED` or `UNSIGNED`
 - Conversion to `std_logic` becomes difficult
- The `std_logic_unsigned` package assumes all `std_logic_vector` declarations are unsigned and overloads all arithmetic and relational operators for them
- The `std_logic_signed` package assumes all `std_logic_vector` declarations are signed
- If a design requires both signed and unsigned arithmetic, the *std_logic_arith* or *NUMERIC_STD* should be used

Synthesis- process

- The statements within a process are executed sequentially
 
```
process(a,b,c,y)
begin
    a <= b + c;
    p <= a + y;
end;
```



Process- General rule

- Sensitivity list is usually ignored during synthesis
- Equivalent behavior of simulation model and hardware
 - All signals which are read are entered into the sensitivity list
 - If SEL is missing in the sensitivity list, what will the simulation be?

```
process (A, B, SEL)
begin
  if SEL = `1` then
    Z <= A;
  else
    Z <= B;
  end if;
end process;
```

```
process (A, B, C)
begin
  D <= (A AND B) OR C;
end process;
```

```
process (A, B)
begin
  D <= (A AND B) OR C;
end process;
```

Variables

- Variables are only used inside PROCESS statements
- Variables generate FFs, when they are read before they are assigned
- If they are assigned first and then read, they generate wires

```
signal input_foo, output_foo, clk : bit ;
...
process (clk)
    variable a, b : bit ;
begin
    if (clk'event and clk='1') then
        output_foo <= b ;
        b := a ;
        a := input_foo ;
    end if ;
end process ;
```

Shift register

```
signal input_foo, output_foo, clk : bit ;
...
process (clk)
    variable a, b : bit ;
begin
    if (clk'event and clk='1') then
        a := input_foo ;
        b := a ;
        output_foo <= b ;
    end if ;
end process ;
```

Wire

Hardware inferring- Common Macros

- Synthesis tool can infer some common macros from the code
 - Register
 - Latch
 - Multiplexer
 - Adder
 - Decoder
 -
- Some manufacture-specific directives to force synthesis tools to extract a macro
 - Example: MUX_EXTRACT constraint in Xilinx that tells the tool if it should use a MUX macro for each identified multiplexer in the VHDL code

Flip-flops

Only Clock
in sensitivity list (and all the
other asynchronous Signals like
RESET)

Instead of using:

if (C'event and C='1')

We can also use:

if (rising_edge(C))

- Defined in std_logic_1164
package


```
library ieee;
use ieee.std_logic_1164.all;

entity registers_1 is
    port (C, D : in std_logic;
          Q    : out std_logic);
end registers_1;

architecture archi of registers_1 is
begin


    process (C)
    begin
        if (C'event and C='1') then
            Q <= D;
        end if;
    end process;

end archi;
```

 

Register

 4-Bit Register With
Positive-Edge Clock,
Asynchronous Set, and
Clock Enable



```
library ieee;
use ieee.std_logic_1164.all;

entity registers_5 is
    port(C, CE, PRE : in std_logic;
          D          : in std_logic_vector (3 downto 0);
          Q          : out std_logic_vector (3 downto 0));
end registers_5;

architecture archi of registers_5 is
begin

    process (C, PRE)
    begin
        if (PRE='1') then
            Q <= "1111";
        elsif (C'event and C='1') then
            if (CE='1') then
                Q <= D;
            end if;
        end if;
    end process;

end archi;
```


Latch

4-Bit Latch With Inverted Gate and Asynchronous Set

```
library ieee;
use ieee.std_logic_1164.all;

entity latches_3 is
    port(D      : in std_logic_vector(3 downto 0);
         G, PRE : in std_logic;
         Q      : out std_logic_vector(3 downto 0));
end latches_3;

 
architecture archi of latches_3 is
begin
    process (PRE, G, D)
    begin
        if (PRE='1') then
            Q <= "1111";
        elsif (G='0') then
            Q <= D;
        end if;
    end process;
end archi;
```



A simple latch


```
library ieee;
use ieee.std_logic_1164.all;
entity latches_1 is
    port(G, D : in std_logic;
         Q : out std_logic);
end latches_1;

 architecture archi of latches_1 is
begin
    process (G, D)
    begin
        if (G='1') then
            Q <= D;
        end if;
    end process;
end archi;
```




Tri-state gate
 
```
entity three_state is
  port(IN1, ENABLE : in std_logic;
        OUT1 : out std_logic );
end;
architecture rtl of three_state is
begin
  process (IN1, ENABLE) begin
    if (ENABLE = '1') then
      OUT1 <= IN1;
    else
      OUT1 <= 'Z'; -- assigns high-impedance state
    end if;
  end process;
end rtl;
```



Shift register

 8-Bit Shift-Left Register
With Positive-Edge
Clock, Serial In and
Serial Out



```
library ieee;
use ieee.std_logic_1164.all;

entity shift_registers_1 is
    port(C, SI : in std_logic;
         SO : out std_logic);
end shift_registers_1;

architecture archi of shift_registers_1 is
    signal tmp: std_logic_vector(7 downto 0);
begin

    process (C)
    begin
        if (C'event and C='1') then
            for i in 0 to 6 loop
                tmp(i+1) <= tmp(i);
            end loop;
            tmp(0) <= SI;
        end if;
    end process;

    SO <= tmp(7);

end archi;
```

RAM

- If a given template can be implemented using Block and Distributed RAM, Xilinx tools implement BLOCK ones

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity rams_01 is
    port (clk   : in std_logic;
          we    : in std_logic;
          en    : in std_logic;
          addr  : in std_logic_vector(5 downto 0);
          di    : in std_logic_vector(15 downto 0);
          do    : out std_logic_vector(15 downto 0));
end rams_01;

architecture syn of rams_01 is
    type ram_type is array (63 downto 0) of std_logic_vector (15 downto 0);
    signal RAM: ram_type;
begin

    process (clk)
    begin
        if clk'event and clk = '1' then
            if en = '1' then
                if we = '1' then
                    RAM(conv_integer(addr)) <= di;
                end if;
                do <= RAM(conv_integer(addr)) ;
            end if;
        end if;
    end process;

end syn;
```

ROM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity rams_21a is
    port (clk : in std_logic;
          en  : in std_logic;
          addr : in std_logic_vector(5 downto 0);
          data : out std_logic_vector(19 downto 0));
end rams_21a;

architecture syn of rams_21a is
```

```
    type rom_type is array (63 downto 0) of std_logic_vector (19 downto 0);
    signal ROM : rom_type:= (X"0200A", X"00300", X"08101", X"04000", X"08601", X"0233A",
                             X"00300", X"08602", X"02310", X"0203B", X"08300", X"04002",
                             X"08201", X"00500", X"04001", X"02500", X"00340", X"00241",
                             X"04002", X"08300", X"08201", X"00500", X"08101", X"00602",
                             X"04003", X"0241E", X"00301", X"00102", X"02122", X"02021",
                             X"00301", X"00102", X"02222", X"04001", X"00342", X"0232B",
                             X"00900", X"00302", X"00102", X"04002", X"00900", X"08201",
                             X"02023", X"00303", X"02433", X"00301", X"04004", X"00301",
                             X"00102", X"02137", X"02036", X"00301", X"00102", X"02237",
                             X"04004", X"00304", X"04040", X"02500", X"02500", X"02500",
                             X"0030D", X"02341", X"08201", X"0400D");
```

```
begin


    process (clk)
    begin
        if (clk'event and clk = '1') then
            if (en = '1') then
                data <= ROM(conv_integer(addr));
            end if;
        end if;
    end process;

end syn;
```

- Xilinx tools use block RAM resources to implement ROMs

Decoder

 - 1-of-8 Decoder
(One-Hot)
VHDL Coding
Example
- No Decoder
Inference if there
are unused
decoder outputs



X10647


```
library ieee;
use ieee.std_logic_1164.all;

entity decoders_1 is
    port (sel: in std_logic_vector (2 downto 0);
          res: out std_logic_vector (7 downto 0));
end decoders_1;

architecture archi of decoders_1 is
begin
    res <= "00000001" when sel = "000" else
           "00000010" when sel = "001" else
           "00000100" when sel = "010" else
           "00001000" when sel = "011" else
           "00010000" when sel = "100" else
           "00100000" when sel = "101" else
           "01000000" when sel = "110" else
           "10000000";
end archi;
```

Multiplexer

- 4-to-1 1-Bit MUX
Using Case
Statement

 


```
library ieee;
use ieee.std_logic_1164.all;

entity multiplexers_2 is
    port (a, b, c, d : in std_logic;
          s : in std_logic_vector (1 downto 0);
          o : out std_logic);
end multiplexers_2;

architecture archi of multiplexers_2 is
begin
    process (a, b, c, d, s)
    begin
        case s is
            when "00" => o <= a;
            when "01" => o <= b;
            when "10" => o <= c;
            when others => o <= d;
        end case;
    end process;
end archi;
```


Latch in Case statements

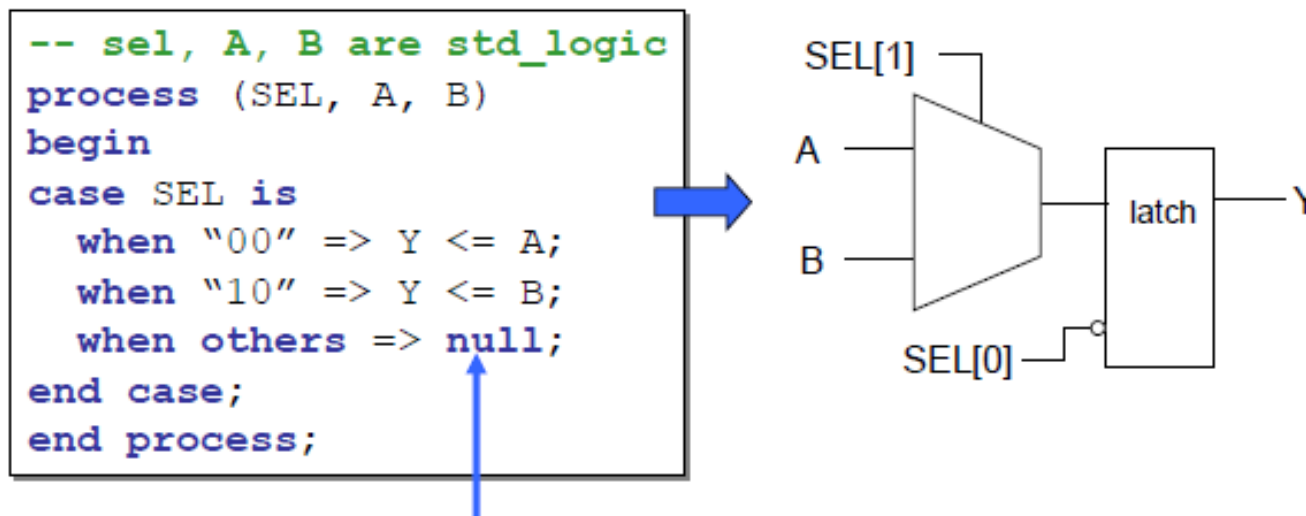
- *CASE* statement should be mutually exclusive and exhaustive in order for synthesis tools to efficiently derive a single MUX equivalent circuit
- Unless an unwanted latch will be synthesized



To avoid unwanted latches, actually define Y for the "others" condition, for example:
when others => Y <= '0' ;

Latch in *if* statements
 
```
process(a,b)
  variable x,y,z;
begin
  ...
  if cond = '1' then
    x := a + b;
  end if;
  y := x + 1;
  ...
end process;
```



Latch elimination in *If* statements

- Two ways to remove latches:
 - Using default value
 - Covering all cases by *ELSE*

Using ELSE

```
IF A = B THEN
    AeqB <= '1' ;
ELSE
    AeqB <= '0' ;
```

Using default values


```
AeqB <= '0' ;
IF A = B THEN
    AeqB <= '1' ;
```

If statement

```
Library IEEE;  
use IEEE.Std_Logic_1164.all;  
entity IF_EXAMPLE is  
  port (A, B, C, X : in std_ulogic_vector(3 downto 0);  
        Z          : out std_ulogic_vector(3 downto 0));  
end IF_EXAMPLE;
```

```
architecture A of IF_EXAMPLE is  
begin  
  process (A, B, C, X)  
  begin  
    if ( X = "1110" ) then  
      Z <= A;  
    elsif (X = "0101") then  
      Z <= B;  
    else  
      Z <= C;  
    end if;  
  end process;  
end A;
```


Hardware realisation

 

For statement



```
-- lokale Variablen :- für "Loop-Enrolling"  
library ieee;  
  
use ieee.std_logic_1164.all;  
entity parity is  
    generic (bus_size : integer := 8);  
    port (input_bus : in std_logic_vector (bus_size-1 downto 0);  
          even_numbits, odd_numbits : out std_logic );  
end parity ;  
  
architecture behave of parity is  
begin  
    process (input_bus)  
        variable temp : std_logic;  
    begin  
        temp := '0';  
        for i in input_bus'low to input_bus'high loop  
            temp := temp xor input_bus(i) ;  
        end loop ;  
        odd_numbits <= temp ;  
        even_numbits <= not temp;  
    end process;  
end behave;
```

 - Will be synthesized by replicating the corresponding hardware
 - By unrolling the loop
- For synthesis, the range specified for the loop variable must be a compile-time constant, otherwise the construct is not often synthesizable
- Synthesis in parallel or serial:
 - Example: parity generation



Resource sharing
  
```
if sel = '1' then  
  sum := a + b;  
else  
  sum := c + d;  
end if
```



Resource sharing: Sharing an operator under mutually exclusive conditions

Resource sharing- another example

```
signal a,b,c,d : integer range 0 to 255 ;
```

```
...
```

```
process (a,b,c,d) begin
```

```
    if ( a+b = c ) then      <statements>
```

Requires two adders

```
    elsif ( a+b = d ) then <more_statements>
```

```
    end if ;
```

```
end process ;
```

```
process (a,b,c,d)
```

```
    variable tmp : integer range 0 to 255 ;
```

```
begin
```

```
    tmp := a+b ;
```

```
    if ( tmp = c ) then <statements>
```

```
    elsif ( tmp = d ) then <more_statements>
```

```
    end if ;
```

```
end process ;
```

Requires one adder




Resource sharing

- Synthesis tools often reduce resources by resource sharing automatically, often provided that:
 - Expressions drive the same signal
 - Operators are of the same type (e.g., both are adders) and have the same width


Source Code Optimization

- Use parenthesis to optimize the speed
- Often done automatically by synthesis tools

 OUT1 <= IN1 + IN2 + IN3 + IN4 + IN5 + IN6




 OUT2 <= ((IN1 + IN2) + (IN3 + IN4)) + (IN5 + IN6)



Source Code Optimization
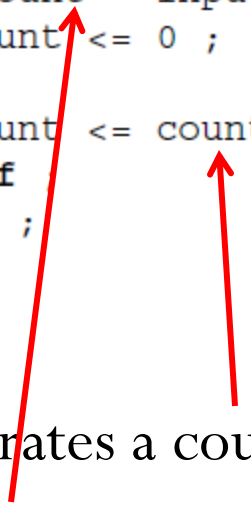
```
process begin
    wait until clk'event and clk='1' ;
    if (count = input_signal) then
        count <= 0 ;
    else
        count <= count + 1 ;
    end if
end process ;
```



- Generates a counter and a full comparator

```
process begin
    wait until clk'event and clk='1' ;
    if (count = 0) then
        count <= input_signal ;
    else
        count <= count - 1 ;
    end if ;
end process ;
```

- If the specifications allows reading the input at reset, simpler hardware can be obtained
- One counter and a comparator to zero that is very simpler than a full comparator

Bus generation

- Use std_logic vectors with multiple tri-state drivers
- Driver code:

```
entity three-state is
    port (    input_signal_1 : in std_logic_vector (7 downto 0);
            ena_1   : in std_logic ;
            output_signal : out std_logic_vector(7 downto 0)
            ) ;
end three-state ;


architecture rtl of three-state is
begin
    output_signal <= input_signal_1 when ena_1 = '1'
                    else "ZZZZZZZZ" ;
end rtl ;
```

Tristate bus

- Code for a tri-state bus with control logic

```
-- binary decoder
with src_select select
  oe <= "0001" when "00",
        "0010" when "01",
        "0100" when "10",
        "1000" when others; -- "11

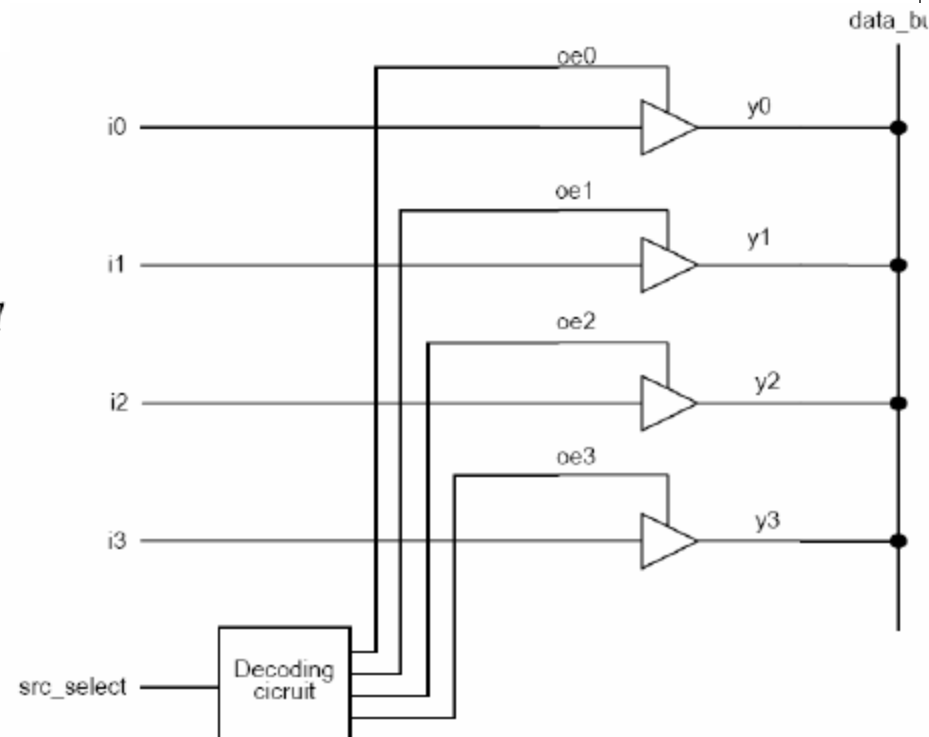-- tri-state buffers
y0 <= i0 when oe(0)='1' else 'Z';
y1 <= i1 when oe(1)='1' else 'Z';
y2 <= i2 when oe(2)='1' else 'Z';
y3 <= i3 when oe(3)='1' else 'Z';
data_bus <= y0;
data_bus <= y1;
data_bus <= y2;
data_bus <= y3;
```





Sequential logic

- To build a sequential logic, we can divide it into combinational logic and memory elements (FF or Register)
 - The output of combinational logic is fed to a memory element and is given to the rest of system by clock
- Alternatively, we can move the entire code into a process that is sensitive to a clock signal

  Exercise

Write a VHDL description that generates this implementation



Xilinx Naming Conventions

- In addition to naming rules we talked about before, Xilinx has some extra naming conventions for naming signals, variables, and instances of entities
- See in page 60 of “Xilinx - Synthesis and Simulation Design Guide”