



ECE381(CAD), Lecture 10:

FSM and FSMD

Mehdi Modarressi

Department of Electrical and Computer Engineering,
University of Tehran

Some pictures and examples are taken from “FPGA Prototyping By VHDL
Examples- Xilinx Spartan-3 Version”

FSM and FSMD

- Reading:
 - “FPGA Prototyping By VHDL Examples- Xilinx Spartan-3 Version”, Chapters 5 and 6

Introduction

- FSM (finite state machine)
- FSMD (finite state machine with datapath)
- Some design examples
 - Pipeline
 - Bus
 - Debouncer
 -

Datapath and control path


- Each digital circuit is composed of two parts
 - Control path
 - Data path
- Datapath is the functional units that implement the computation or required operations and services
 - Like ALU in a CPU
- Control path controls the behavior of the functional units
 - Activating datapath components, feeding data to them,...

FSM

- Control path operation: Examines the external commands and also the current status of the system and activates proper control signals to control operation of a datapath
- FSMs are used to describe the control path of a digital circuit


FSM

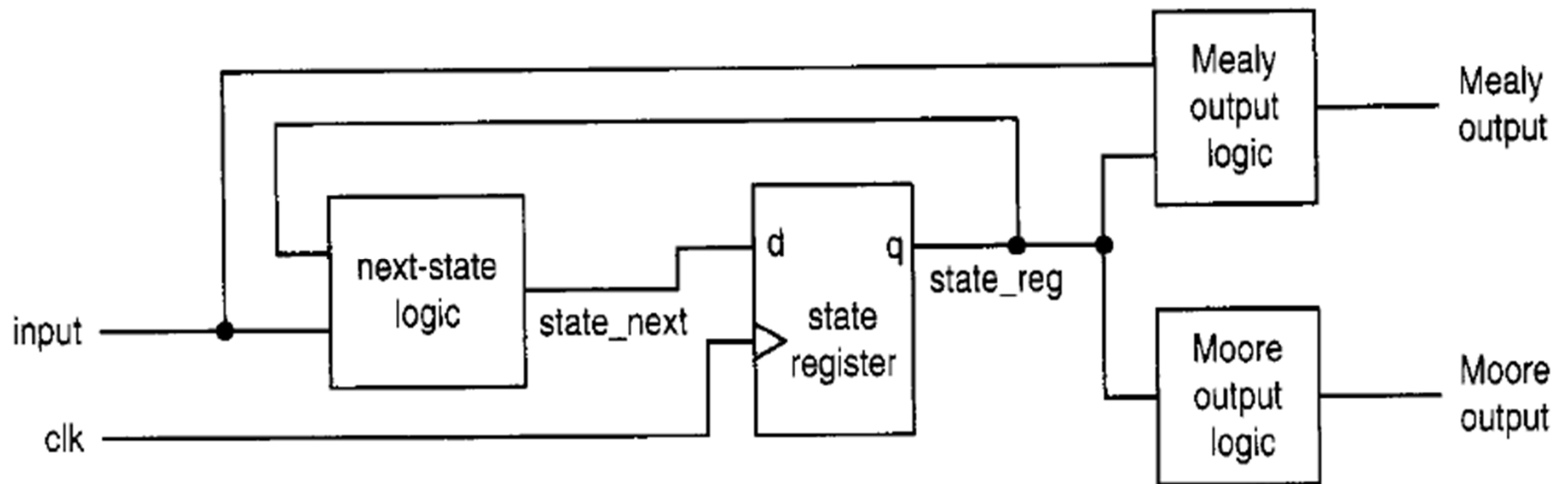- Moore: the output is only a function of state
- Mealy : the output is a function of state and external input




FSM representation

 - An FSM is usually specified by a state diagram
- A state diagram is composed of nodes, which represent states and are drawn as circles, and annotated transitional arcs



FSM modeling by VHDL

 - Example from “The designers guide to VHDL”, page 110
- An FSM with both Mealy and Moore outputs




FSM modeling by VHDL

- Use the VHDL's enumerated data type to represent the FSM's states
- 3-process coding method
 - Use one process for state transition, one for next state calculation, and one for output generation

FSM modeling by VHDL


```
library ieee;
use ieee.std_logic_1164.all;
entity fsm_eg is
  port(
    clk, reset: in std_logic;
    a, b: in std_logic;
    y0, y1: out std_logic
  );
end fsm_eg;

 10 architecture mult_seg_arch of fsm_eg is
  type eg_state_type is (s0, s1, s2);
  signal state_reg, state_next: eg_state_type;
begin
```





PROCESS-1: State transition
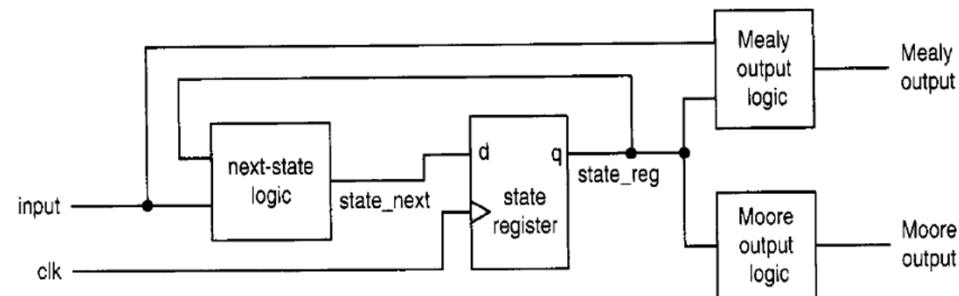
```
-- state register
process(clk,reset)
begin
    if (reset='1') then
        state_reg <= s0;
    elsif (clk'event and clk='1') then
        state_reg <= state_next;
    end if;
end process;
```



PROCESS-2: State calculation

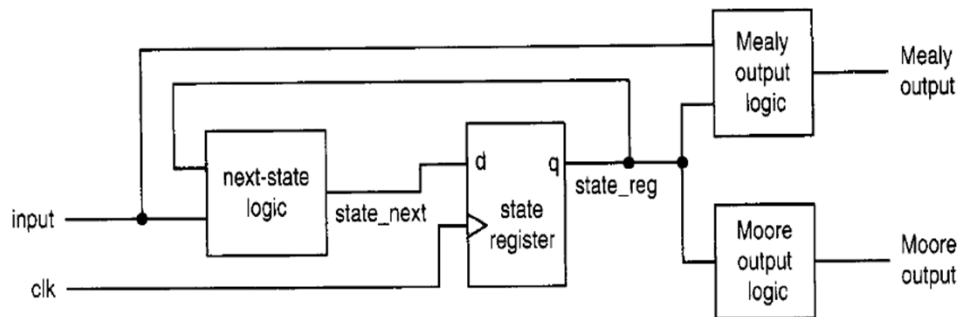 

```
-- next-state logic
process(state_reg,a,b)
begin
  case state_reg is
    when s0 =>
      if a='1' then
        if b='1' then
          state_next <= s2;
        else
          state_next <= s1;
        end if;
      else
        state_next <= s0;
      end if;
    when s1 =>
      if (a='1') then
        state_next <= s0;
      else
        state_next <= s1;
      end if;
    when s2 =>
      state_next <= s0;
  end case;
end process;
```

PROCESS-3: Output generation

```


— Mealy output logic
process(state_reg,a,b)
begin
  case state_reg is
    when s0 =>
      if (a='1') and (b='1') then
        y0 <= '1';
      else
        y0 <= '0';
      end if;
    when s1 | s2 =>
      y0 <= '0';
  end case;
end process;
end mult_seg_arch;

```

```

— Moore output logic
process(state_reg)
begin
  case state_reg is
    when s0|s2 =>
      y1 <= '0';
    when s1 =>
      y1 <= '1';
  end case;
end process;

```

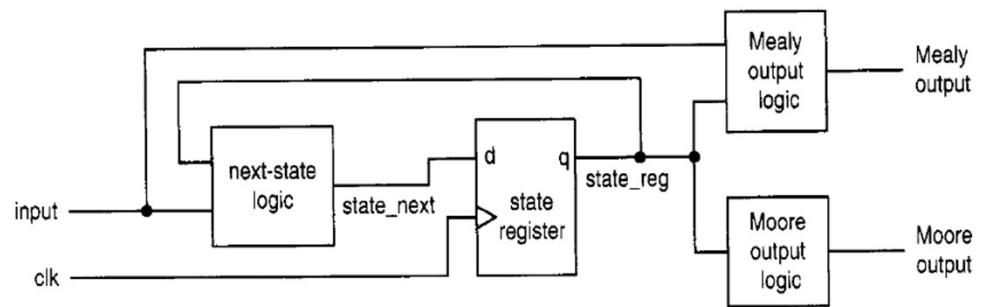

```


-- state register
process(clk,reset)
begin
    if (reset='1') then
        state_reg <= s0;
    elsif (clk'event and clk='1') then
        state_reg <= state_next;
    end if;
end process;

```

```

-- next-state logic
process(state_reg,a,b)
begin
    case state_reg is
        when s0 =>
            if a='1' then
                if b='1' then
                    state_next <= s2;
                else
                    state_next <= s1;
                end if;
            else
                state_next <= s0;
            end if;
        when s1 =>
            if (a='1') then
                state_next <= s0;
            else
                state_next <= s1;
            end if;
        when s2 =>
            state_next <= s0;
    end case;
end process;


```

 

```


-- Moore output logic
process(state_reg)
begin
    case state_reg is
        when s0|s2 =>
            y1 <= '0';
        when s1 =>
            y1 <= '1';
    end case;
end process;

```

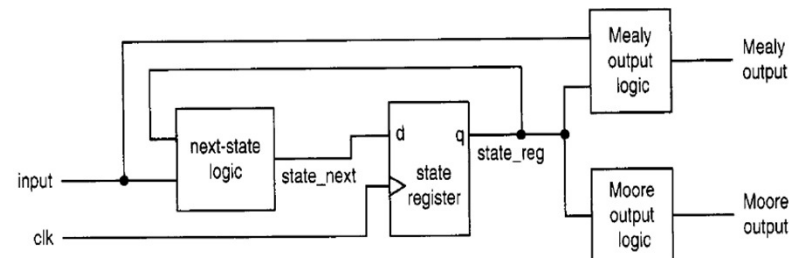


Example- Rising-edge detector

Moore

 

The zero and one states indicate that the input signal has been '0' and '1' for awhile

Mealy

 

Exercise


Consider a parking lot with a single entry and exit gate. Two pairs of photo sensors are used to monitor the activity of cars, as shown in Figure 5.11. When an object is between the photo transmitter and the photo receiver, the light is blocked and the corresponding output is asserted to '1'. By monitoring the events of two sensors, we can determine whether a car is entering or exiting or a pedestrian is passing through. For example, the following sequence indicates that a car enters the lot:

- Initially, both sensors are unblocked (i.e., the a and b signals are "00").
- Sensor a is blocked (i.e., the a and b signals are "10").
- Both sensors are blocked (i.e., the a and b signals are "11").
- Sensor a is unblocked (i.e., the a and b signals are "01").
- Both sensors become unblocked (i.e., the a and b signals are "00").

Design a parking lot occupancy counter as follows:


Design an FSM with two input signals a and b, and 4 output signals P_in, P_out, C_in, C_out that assert one clock signal when a pedestrian enters, a pedestrian exits, a car enters, and a car exits, respectively.

Implement the FSM by VHDL

 

FSMD

 - Finite state machine with datapath
- Combines an FSM and regular sequential circuits



RTL


- The FSMD is used to implement systems described at the Register Transfer Level (RTL)
- An RT operation specifies data manipulation and transfer for a single destination register

$$r_{\text{dest}} \leftarrow f(r_{\text{src1}}, r_{\text{src2}}, \dots, r_{\text{srcn}})$$

- Elementary operations - called *microoperations*
 - load, count, shift, add, bitwise "OR", etc.
 - Example:
 - $R0 \leftarrow R1 \oplus R2$
 - $R6 \leftarrow R7 + R8 - 1$

RT description methodology

 
- Arrow (\rightarrow): data transfer
 - e.g. $R1 \leftarrow R2$
- Brackets []: Specifies a memory address
 - e.g. $R0 \leftarrow M[AR]$
- Comma: separates parallel operations
- Colon: states a condition
 - If ($K1 = 1$) then ($R2 \leftarrow R1$)
 - $\Leftrightarrow K1: (R2 \leftarrow R1)$



RTL

- RT operations are synchronized by an embedded clock
- The result from the $f(.)$ function is not stored to the destination register until the next rising edge of the clock

$$a \leftarrow a - b + 1$$

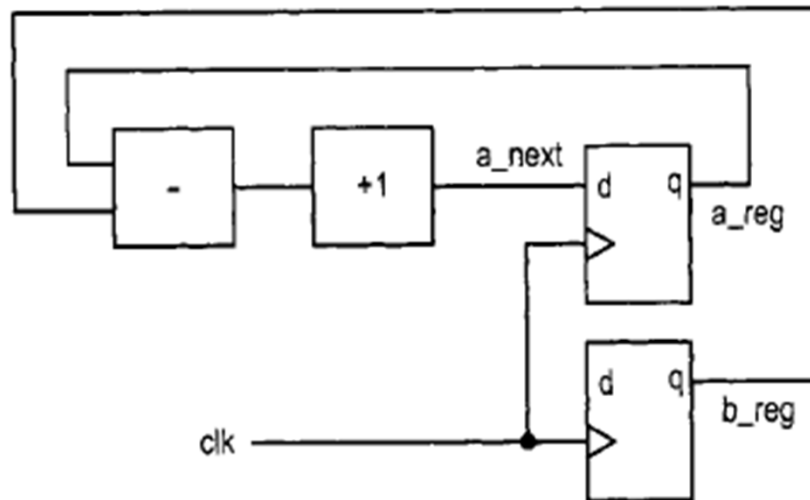


RTL


- A circuit based on the RT methodology specifies which RT operations should be executed in each step
- An RT operation is done in a clock-by-clock basis
 - Its timing is similar to a state transition of an FSM

ASM chart

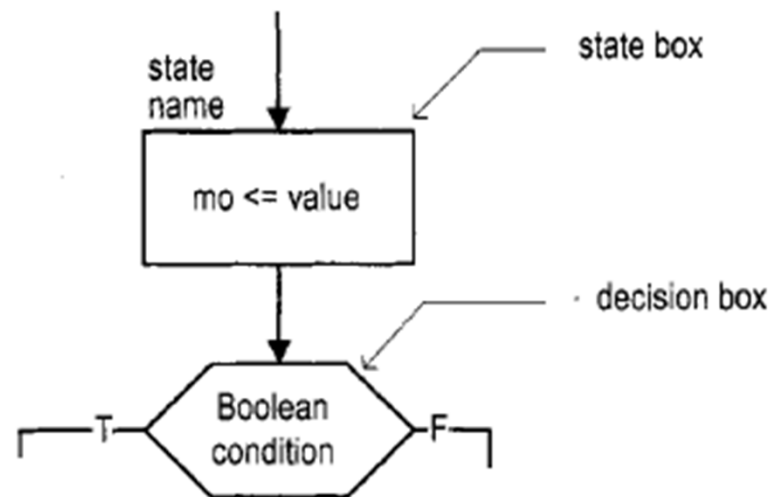
- ASM: algorithmic state machine
- Composed of a network of ASM blocks
 - State blocks: represents a state in an FSM
 - Decision blocks: tests the input condition and determines which exit path to take




Elements of ASM chart

 

(a) State box

 


(b) Decision box

 

 (c) Conditional output box


State box

- The symbol is a rectangle, with a label (state name) and output control operations(Moore type) written inside
- It has a single exit path (arrow)




Decision box

 - The symbol is a diamond
- A condition variable and multiple exit paths, labeled
- with values of the input condition
- It has a single entry path.




Conditional output box

 - The symbol is a rounded rectangle
- Denotes output signals that are of the Mealy type.
- Always after a decision box
- Single entry and exit path





ASMD chart

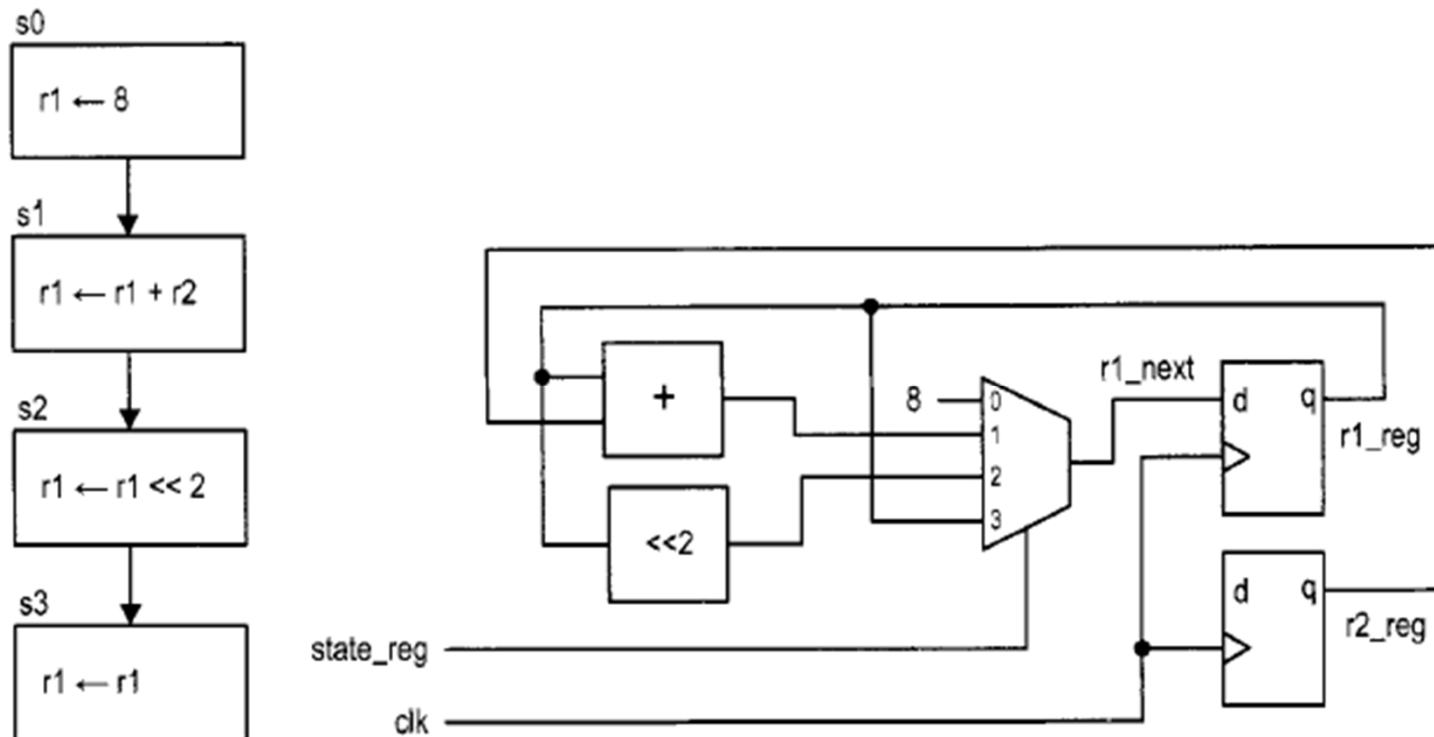- ASM with datapath
- A clock is embedded in the chart
 - Registers are updated when exiting the current ASMD block





ASMD chart

  


ASM block

- ASM block

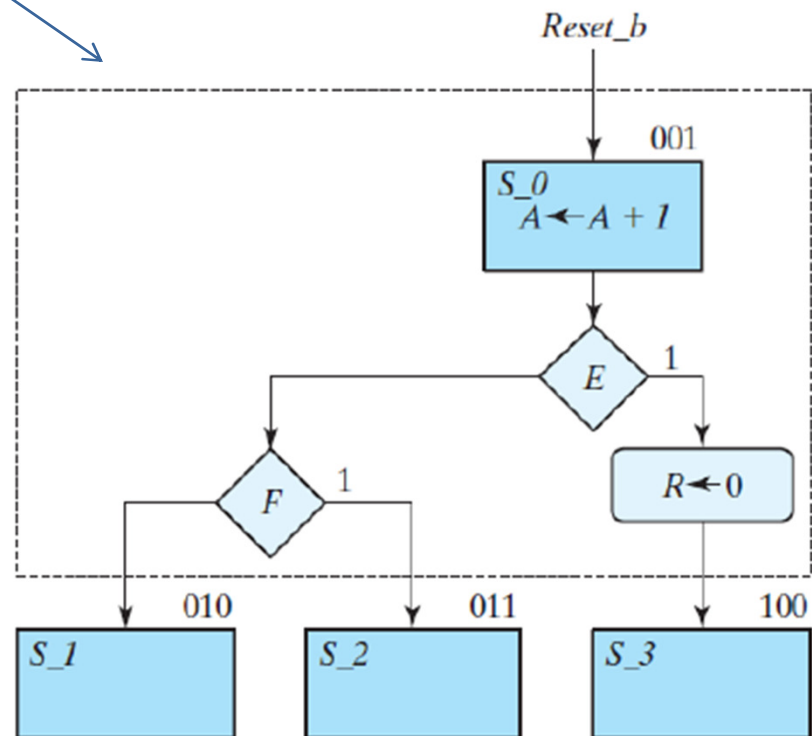 


ASMD timing

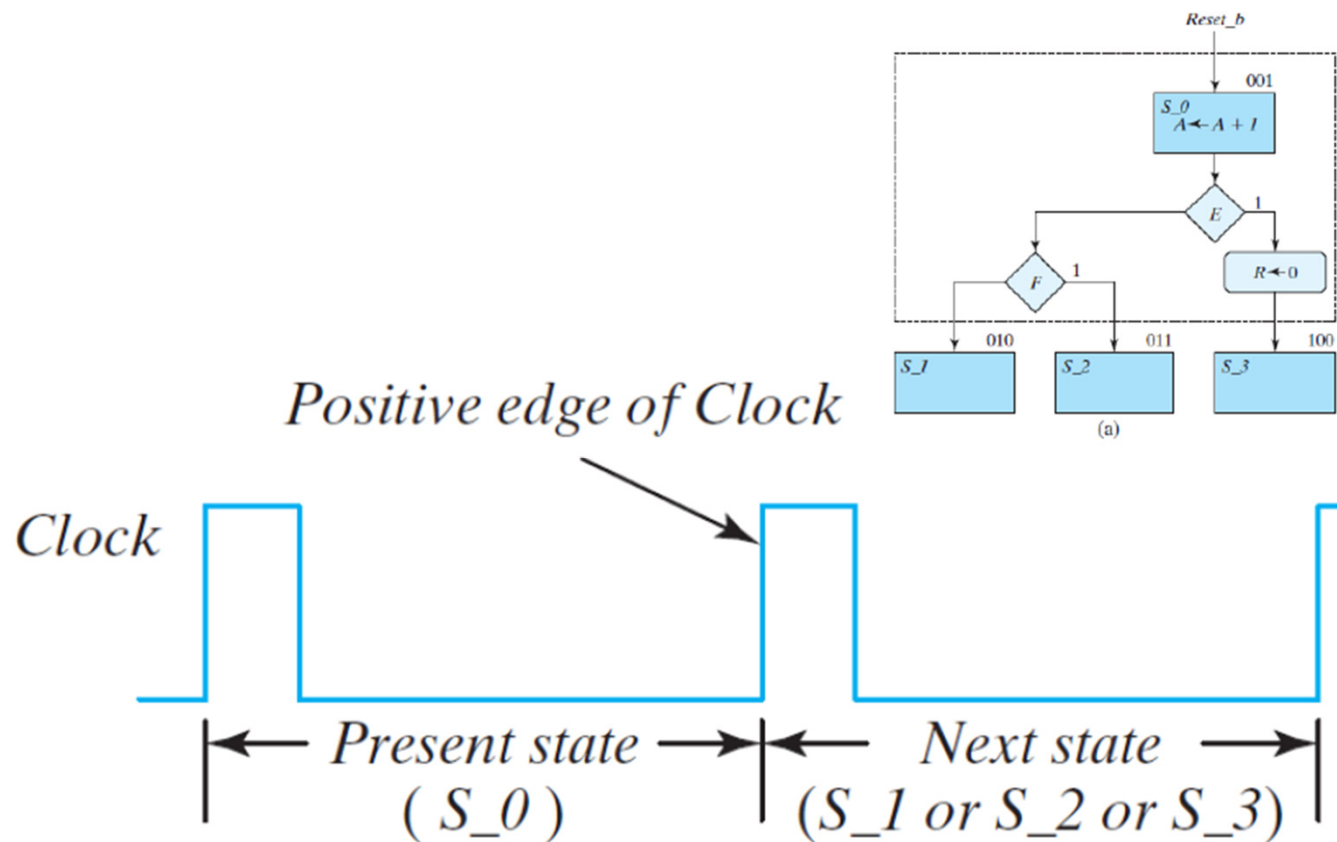- Control passes one branch in the ASM block during the clock period and waits for the clock to enter the next state box




ASMD timing

 - The destination registers are updated when exiting the current ASMD block, but not within the block
 - May introduce errors when a register is used in a decision box
- If the new value of r is desired, we should use r_next , the output of the combinational logic



“ $:=$ ” is used for immediate assignment

State diagram- ASM equivalence

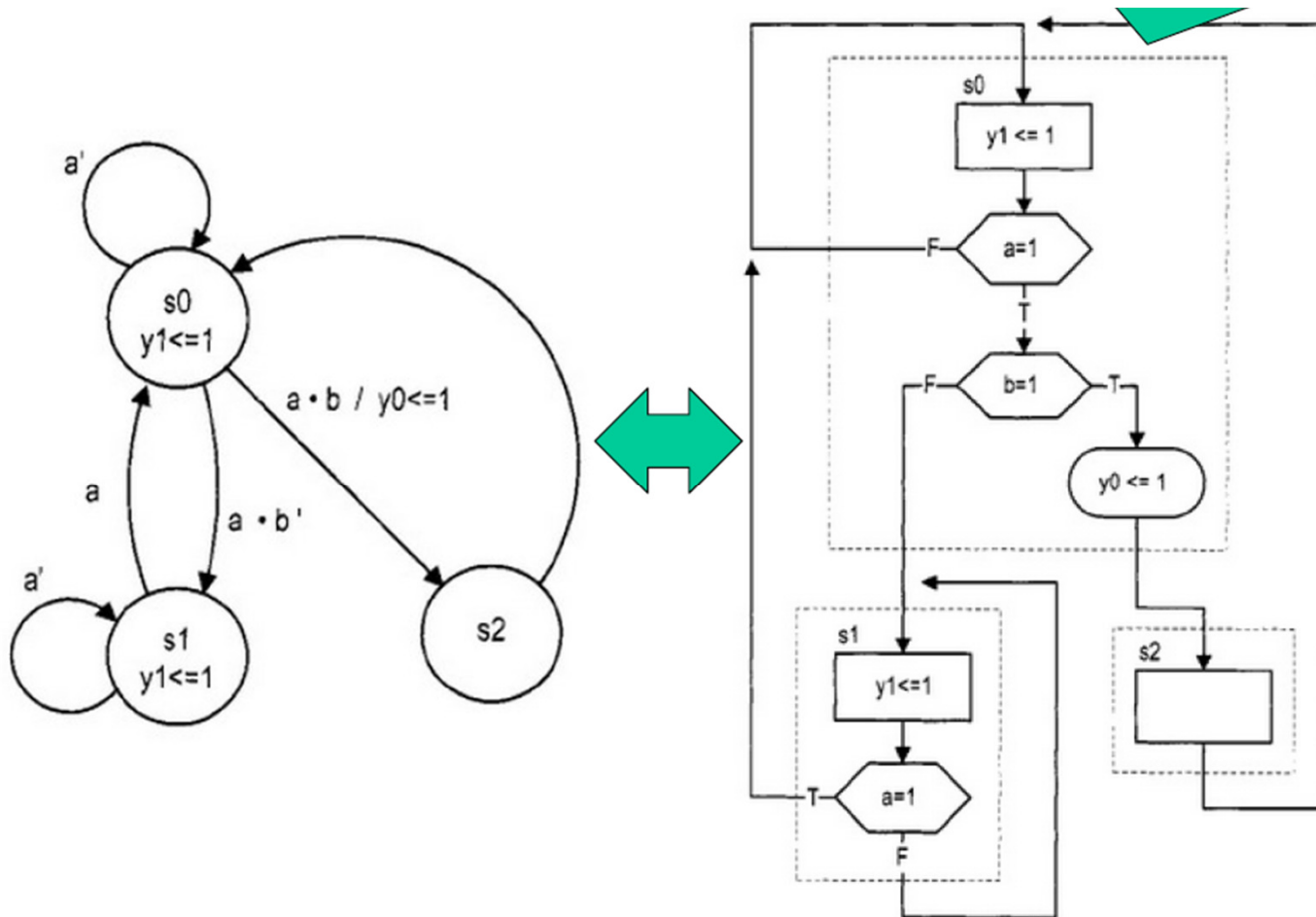


Example: Fibonacci number

- Fibonacci number circuit
- A sequence of integers

$$fib(i) = \begin{cases} 0 & \text{if } i = 0 \\ 1 & \text{if } i = 1 \\ fib(i-1) + fib(i-2) & \text{if } i > 1 \end{cases}$$

ASMD

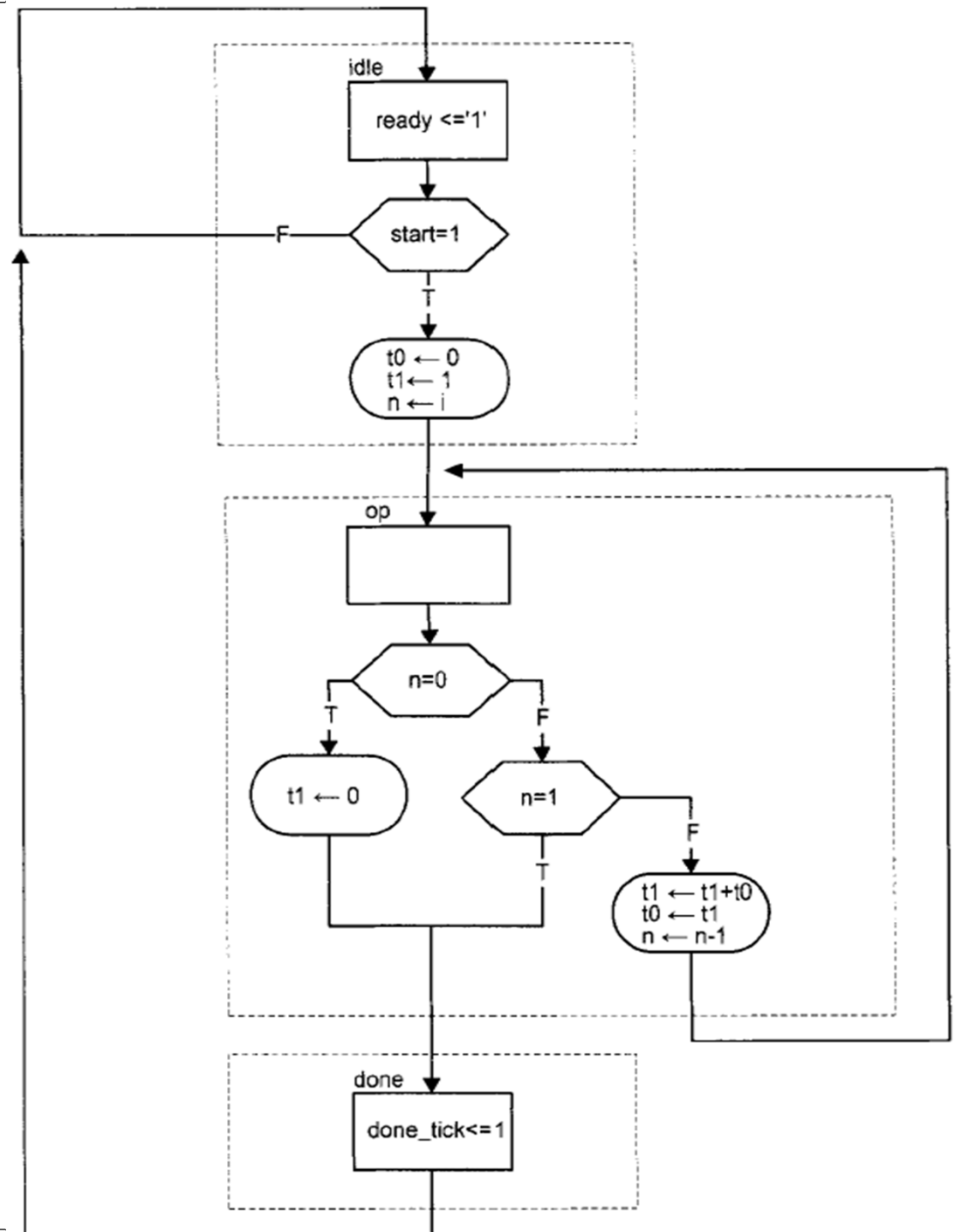- t1 and t0 are temporary storage registers
- n is the index register
- Input:
 - i: the number of required iterations
 - Start: Commands the beginning of operation
- Output:
 - F: the last generated number
 - Ready: indicates that the circuit is idle and ready to take new input
 - done-tick: asserted for one clock cycle when the operation is completed



VHDL code

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity fib is
    port(
        clk, reset: in std_logic;
        start: in std_logic;
        i: in std_logic_vector(4 downto 0);
        ready, done_tick: out std_logic;
        f: out std_logic_vector(19 downto 0)
    );
end fib;

architecture arch of fib is
    type state_type is (idle,op,done);
    signal state_reg, state_next: state_type;
    signal t0_reg, t0_next, t1_reg, t1_next: unsigned(19 downto 0);
    signal n_reg, n_next: unsigned(4 downto 0);

begin
```

VHDL code

- We use a 3-process implementation, much like the FSM implementation in previous lecture
 - but we should also handle the datapath registers in the next state calculation and assignment processes

Process 1: State and
datapath register
assignment

```
-- fsmd state and data registers
process(clk,reset)
begin
    if reset='1' then
        state_reg <= idle;
        t0_reg <= (others=>'0');
        t1_reg <= (others=>'0');
        n_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
        state_reg <= state_next;
        t0_reg <= t0_next;
        t1_reg <= t1_next;
        n_reg <= n_next;
    end if;
end process;
```

```

-- fsmd next-state logic
process(state_reg,n_reg,t0_reg,t1_reg,start,i,n_next)
begin
    ready <='0';
    done_tick <= '0';
    state_next <= state_reg;
    t0_next <= t0_reg;
    t1_next <= t1_reg;
    n_next <= n_reg;
    case state_reg is
        when idle =>
            ready <= '1';
            if start='1' then
                t0_next <= (others=>'0');
                t1_next <= (0=>'1', others=>'0');
                n_next <= unsigned(i);
                state_next <= op;
            end if;
        when op =>
            if n_reg=0 then
                t1_next <= (others=>'0');
                state_next <= done;
            elsif n_reg=1 then
                state_next <= done;
            else
                t1_next <= t1_reg + t0_reg;
                t0_next <= t1_reg;
                n_next <= n_reg - 1;
            end if;
        when done =>
            done_tick <= '1';
            state_next <= idle;
    end case;
end process;

```

Process 2: next
state and datapath
register

```

-- output
f <= std_logic_vector(t1_reg);

```

Process 3: output
generation, we actually
use a dataflow
assignment, as the
output is very simple