

CE233(CAD), Lecture 3:

Xilinx FPGAs

Mehdi Modarressi

Department of Electrical and Computer Engineering,
University of Tehran

- Reading:
 - *Spartan-3 Generation FPGA User Guide, Xilinx ug331 (v1.8)*
 - “FPGA Prototyping By VHDL Examples- Xilinx Spartan-3 Version”, Chapter 2
 - “The Design Warrior's Guide to FPGAs”, Chapter 4

Xilinx FPGAs



Xilinx FPGA History


Xilinx modern FPGAs



'08 Spartan-3A XA	'99 Virtex-E
'08 Virtex-5 FXT	'99 Spartan-II
'08 Virtex-5 TXT	'99 QPro-Virtex
'07 QPro Virtex-4	'98 Virtex
'07 QPro Virtex-IIPro	'98 SpartanXL
'07 Spartan-3AN	'98 Spartan
'07 Spartan-3A DSP	'98 XQ4000XL
'06 Virtex-5 LX/LXT/SXT	'98 XQR4000XL
'06 Spartan-3A	'97 XC4000XV
'05 Spartan-3E	'97 XC4000XLA
'04 Virtex-4 LX/SX/FX	'97 XC4000XL
'04 Spartan-3 XA	'97 XQ4000E/EX
'04 Spartan-IIE XA	'96 XC4000E/EX
'04 QPro-R Virtex-II	'96 XC6200
'04 QPro Virtex-II	'95 XC8100
'04 QPro Virtex-E	'95 XC5200
'04 Spartan-3L	'94 XC4000D/L
'03 Virtex-II ProX	'93 XC4000H
'03 Spartan-3	'93 XC3100A/L
'02 Virtex-II Pro	'93 XC3100
'02 Spartan-IIE IQ	'93 XC3000A/L
'02 Spartan-II IQ	'93 XC2000L
'02 SpartanXL IQ	'92 XC4000A
'01 Spartan-IIE	'91 XC4000
'01 QPro-R Virtex	'87 XC3000
'00 Virtex-II	'85 XC2000

 Example: Xilinx XC4000

- A simple FPGA introduced in the 80's
- Array of *Configurable Logic Blocks (CLBs)*
- SRAM-based




Lookup table (LUT)

- Each XC4000 CLB implements the logic functions using a lookup table (LUT)
 - An alternative to PAL-based implementation
- An n-input LUT can implement any n-input function

a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Truth table

$$F = (a + b) \times c'$$


 


LUT vs PAL


$$F = (a + b) \times c'$$

a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Truth table

  


Xilinx XC4000 FPGAs- CLB

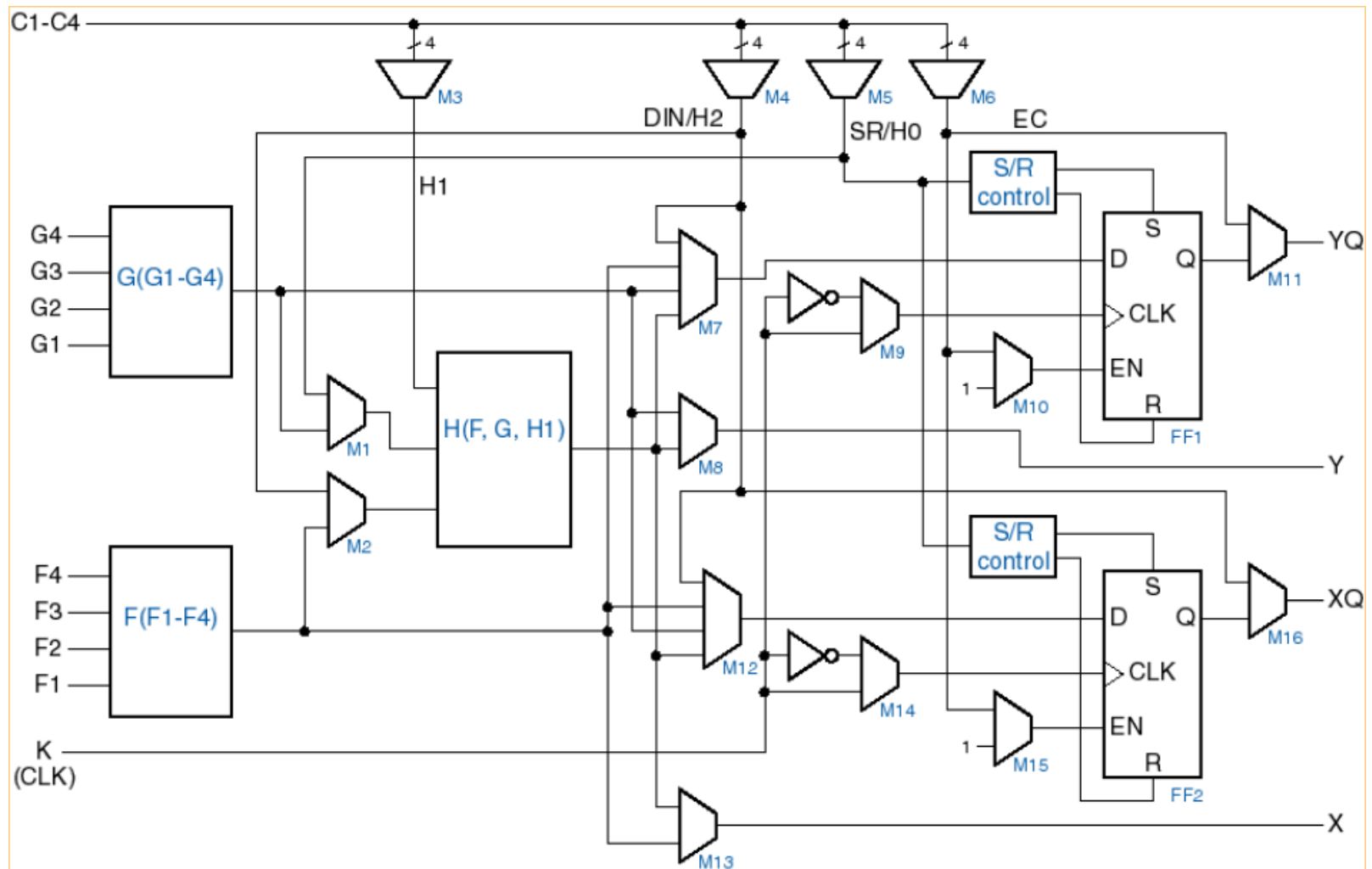

Xilinx XC4000 FPGAs- CLB

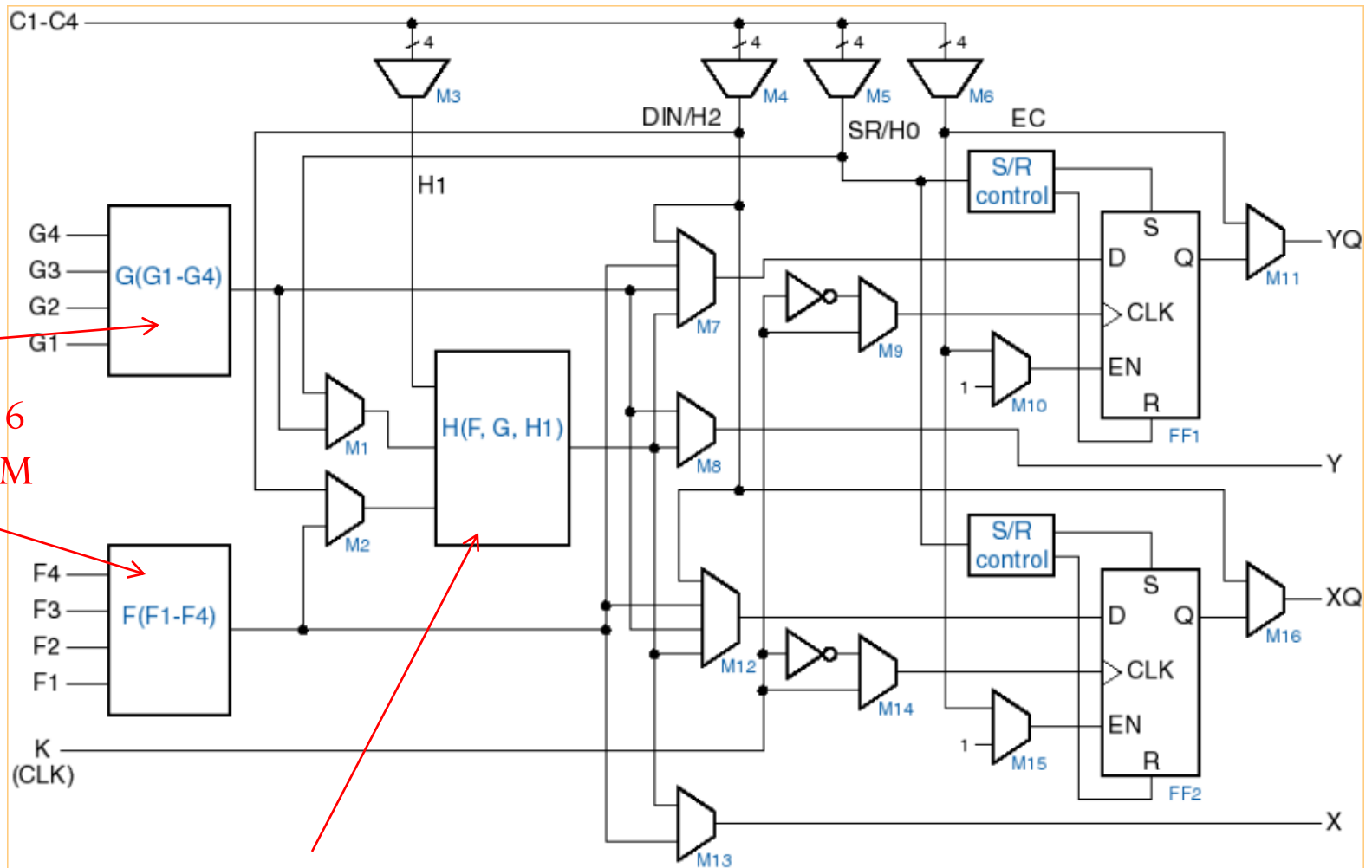
F and G
LUTs: 4
input -> 16
bits of RAM
(each)



H LUT : 3 input -> 8 bits of RAM


Xilinx XC4000 CLB configuration

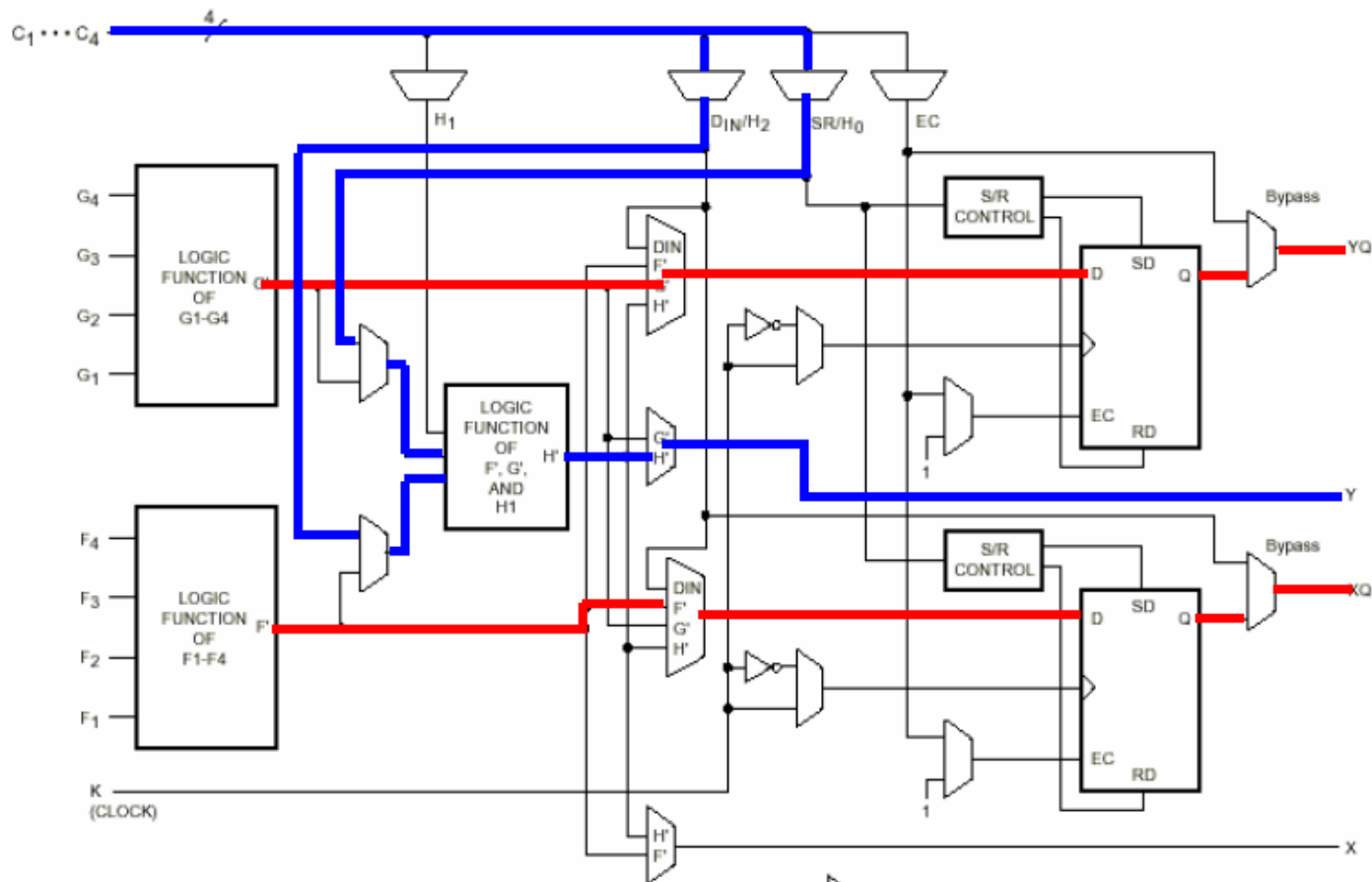- Two 4-input functions, registered output input functions, and one 2-input function with combinational output




Xilinx C4000 CLB configuration


- 5-input function, combinational output

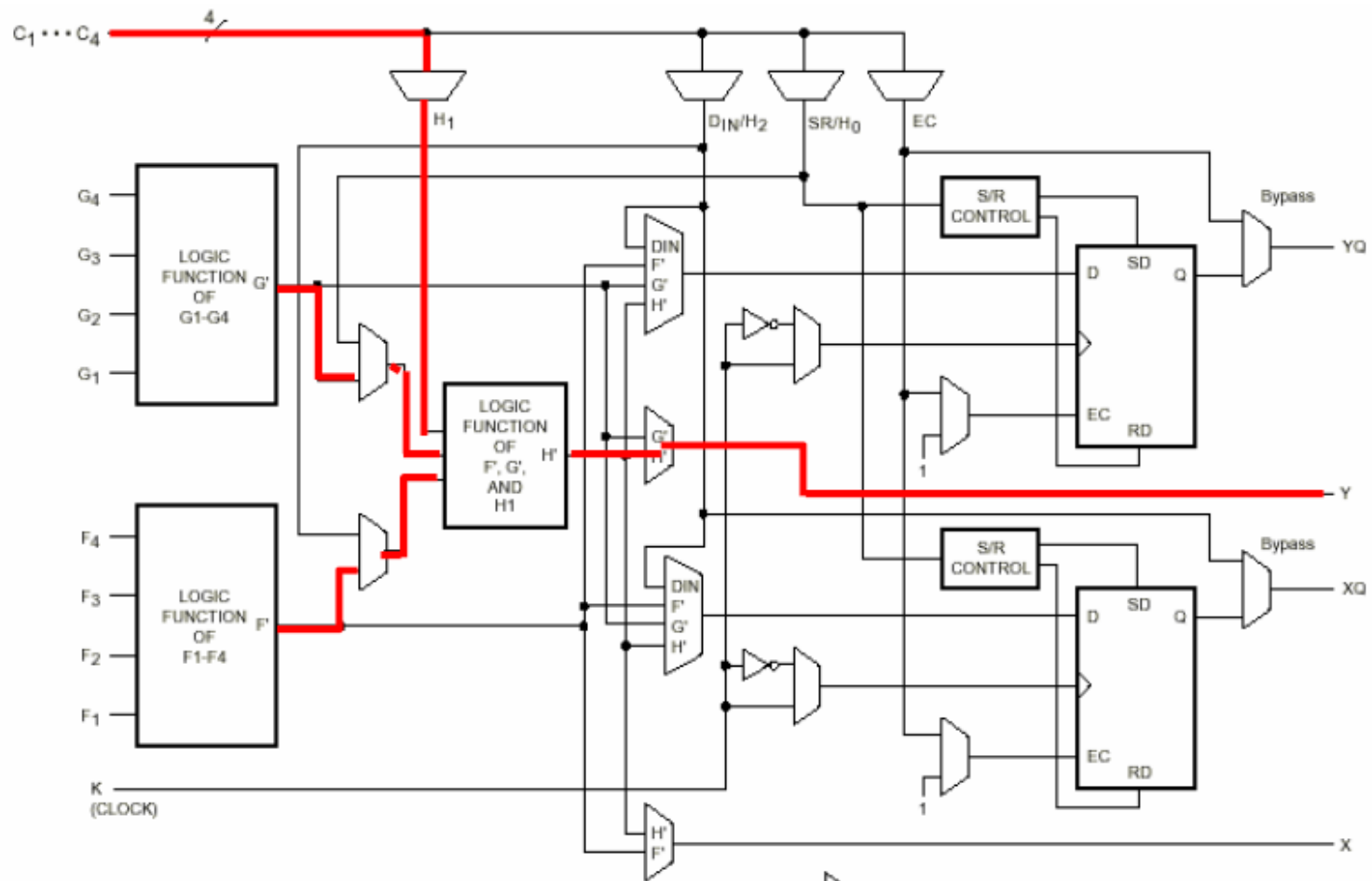

(X+1)-Input functions by x-input LUTs

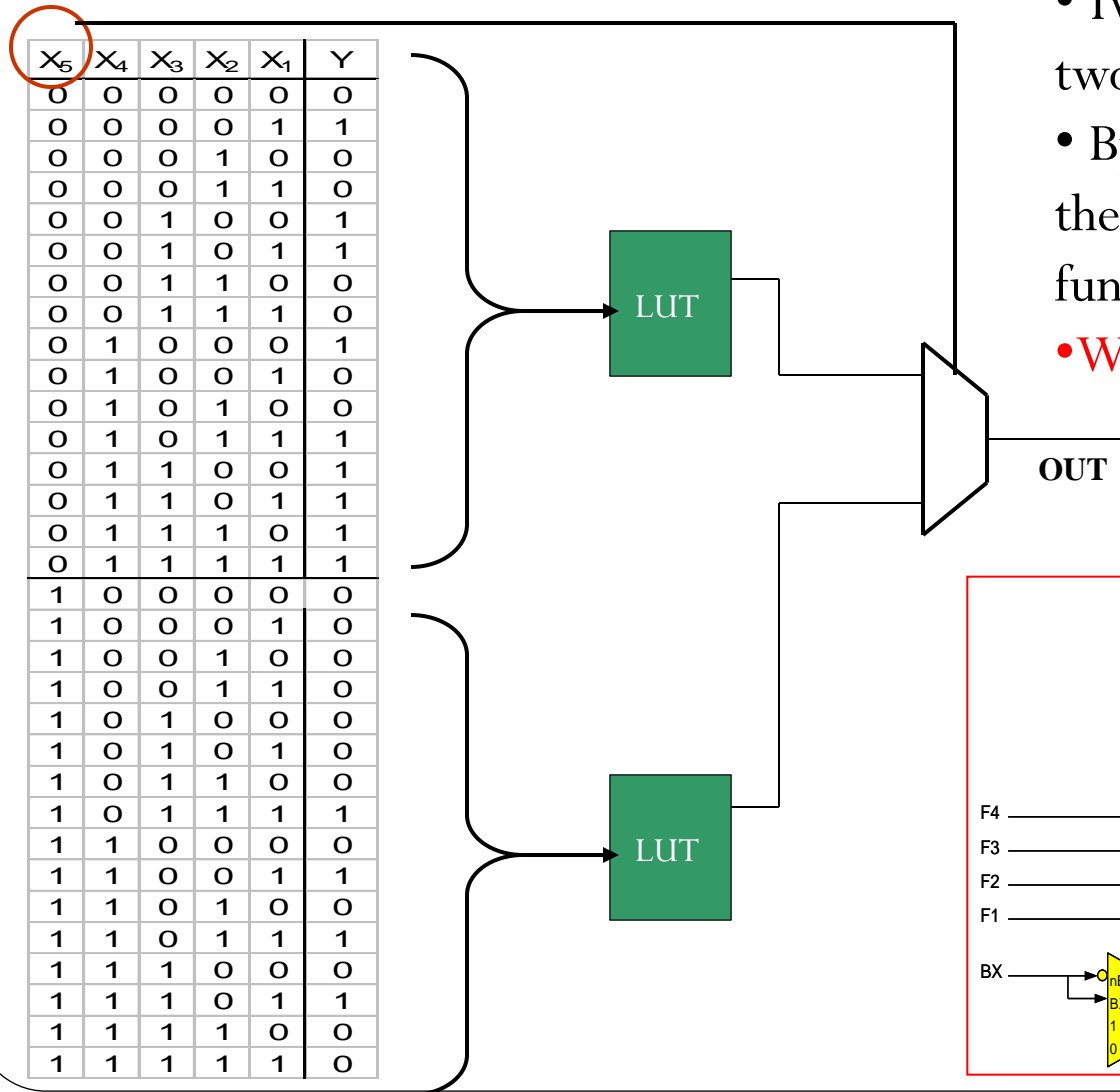

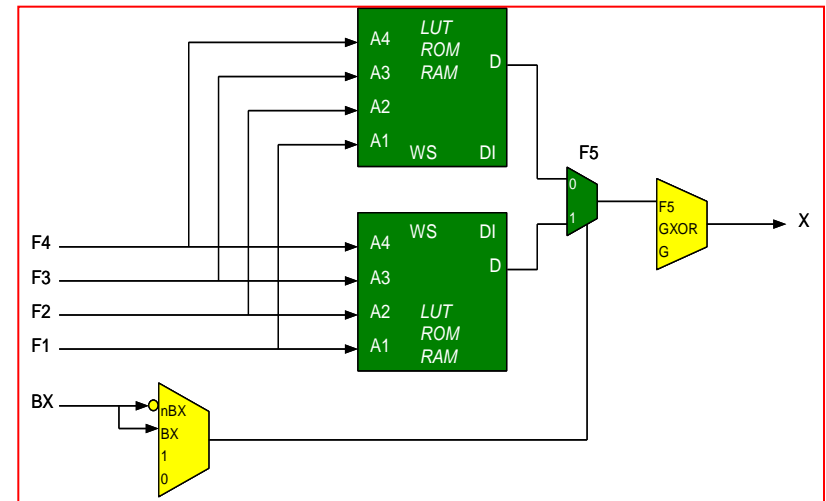- Two 4-input LUTs can implement two 4-input functions
- By adding a multiplexer like below, they can implement any 5-input functions
- Why?



$(X+1)$ -Input functions by x -input LUTs

- Two n -input LUTs and one 3-input LUT can implement any $(n+1)$ -input function
- Why?
- Prove as an exercise!

Example

- Implement the following functions on a single CLB of the XC4000 FPGA:


$$X = A'B' (C + D)$$

$$Y = AK + BK + C'D'K + AEJL$$

- Use look up table F to implement X
- Use look up table G for AEJL
- Use F, G and H for Y:

$$\begin{aligned} Y &= K(A+B + C'D') + AEJL \\ &= KX' + AEJL = KF' + G \end{aligned}$$


Programming a CLB

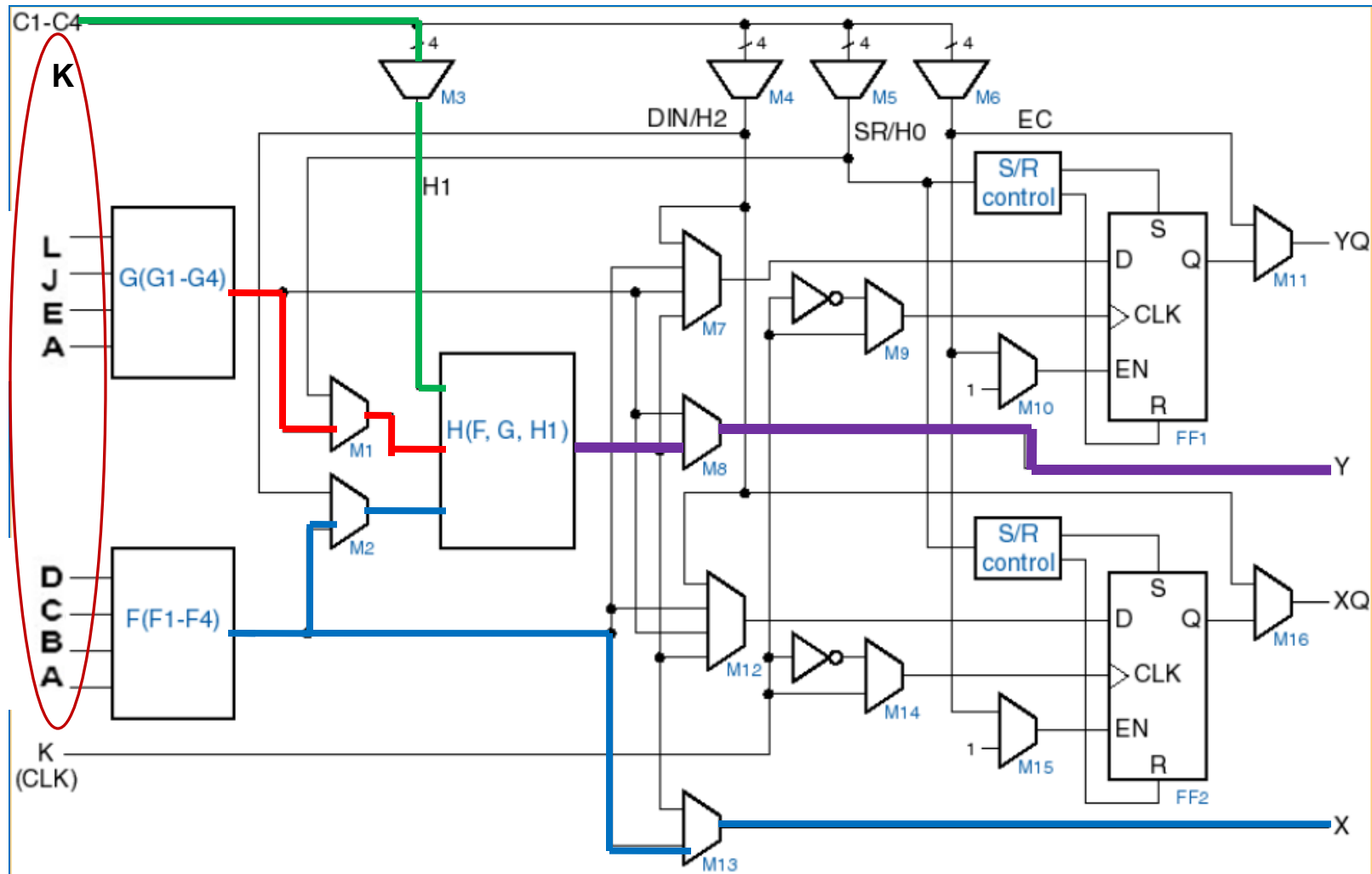


$$X = A'B'(C + D)$$

$$Y = AK + BK + C'D'K + AEJL$$


FPGA interconnects

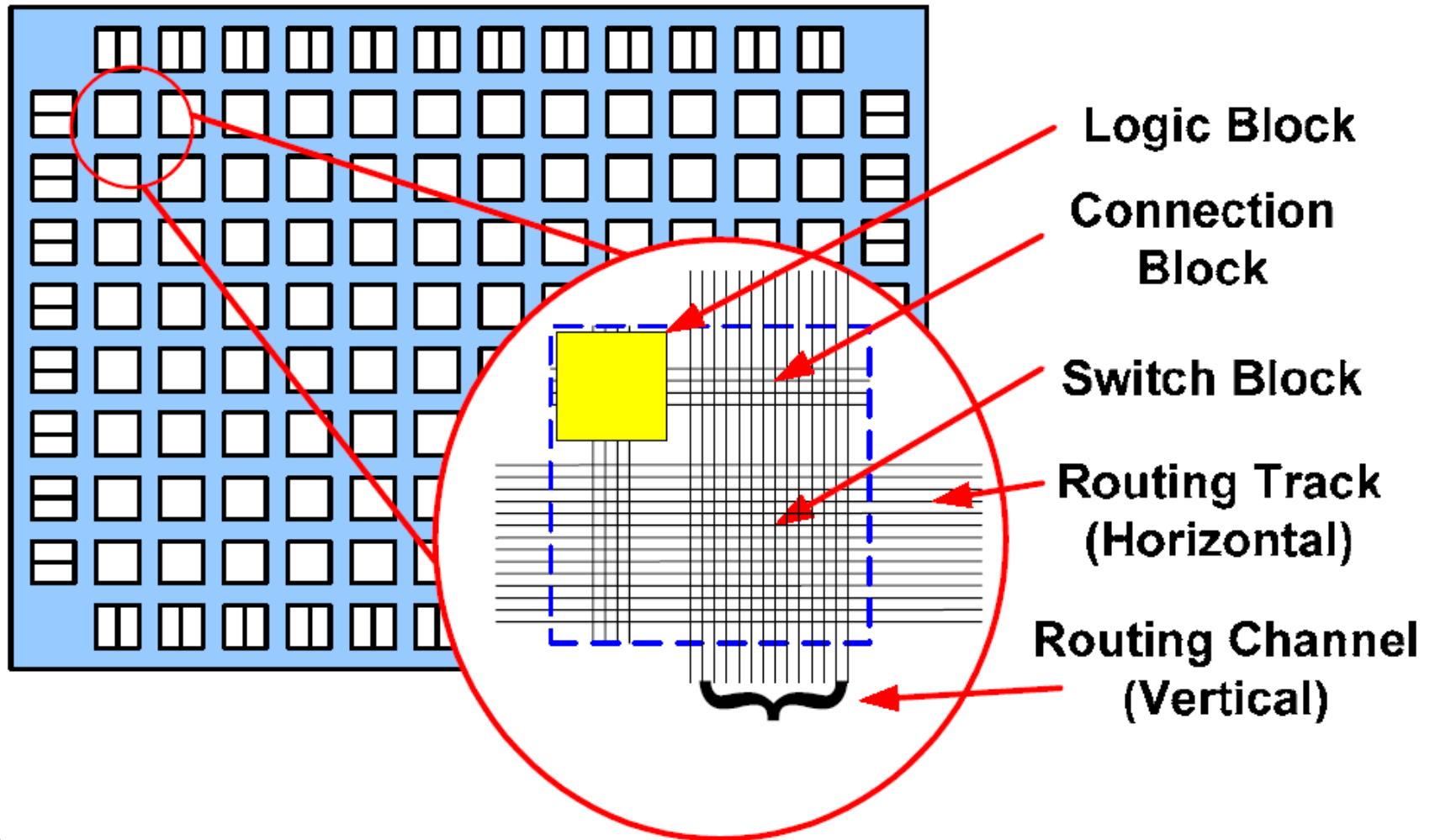


FPGA interconnects- switch box

 

 - Switch Blocks connect horizontal and vertical channels
- A trade-off between flexibility and switch size




 $F_s = 3$, the most common switch
Low flexibility, good size



$F_s = n-1=6$: too big but very flexible


XC4000 interconnects

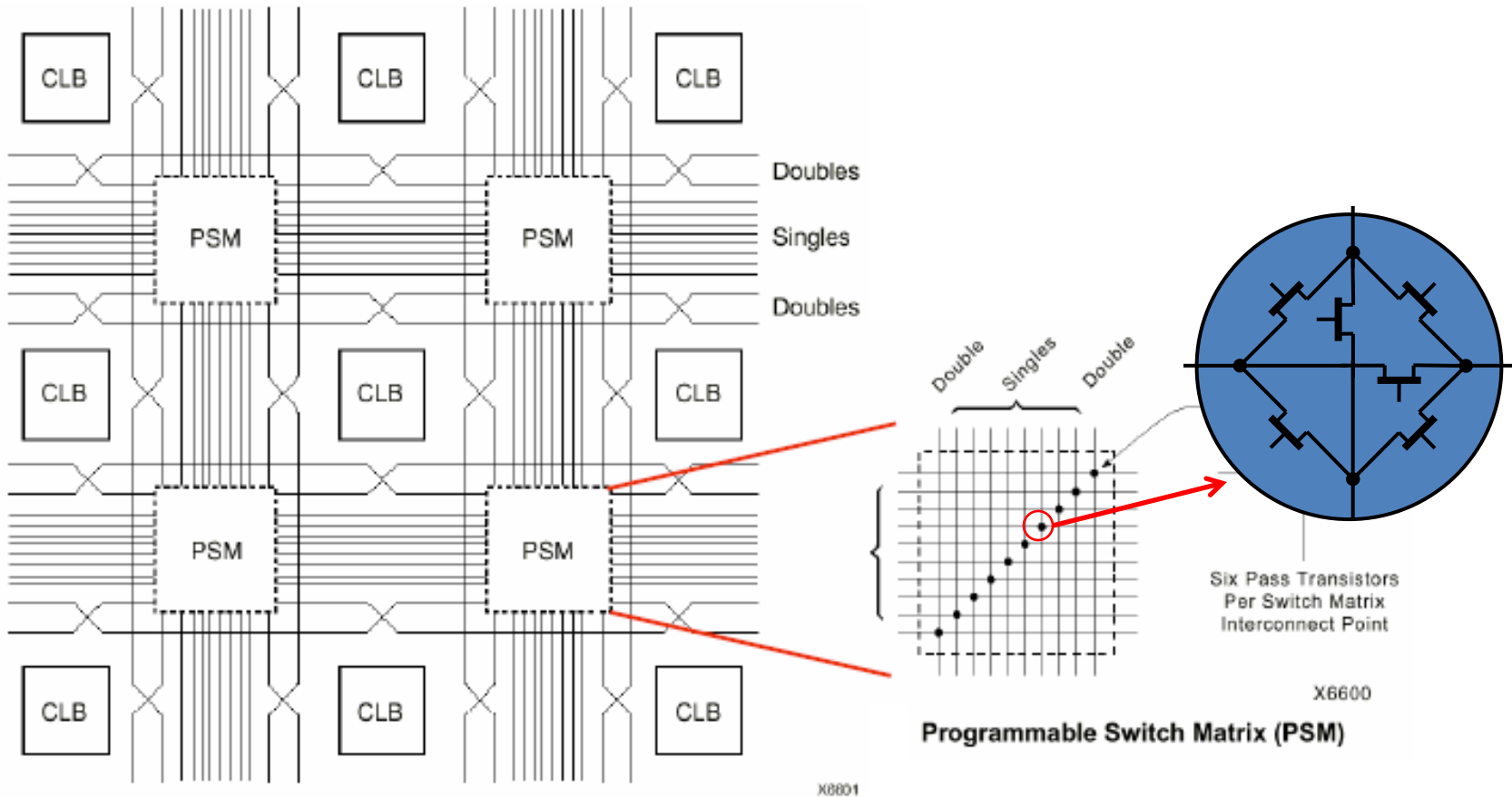

$F_s=3$, why?


Connection box

 - How to connect CLB to wires?
- Solution: Connection box
 - Device that allows inputs and outputs of CLB to connect to different wires




Connection box

 - Connection box characteristics
 - Topology
 - Defines the specific wires each CLB I/O can connect to
 - Examples: same flexibility, different topology




FPGA interconnects

 


Connect Logic Blocks using wires and Programmable Switches

FPGA interconnects- wires

 
- Typically, an FPGA contains a mix of segment lengths:
 - Some wires that span only one logic block
 - Some wires that span more than one logic block
 - Some wires that span the whole chip
- If a segment is too short, must traverse many segments to reach your destination
 - If a segment is too long, waste routing capacity, extra capacitance: too slow!




FPGA interconnects- wires

 

 - Short segments are good for local connections
- Long segments are good for global connections
- Most FPGA's have a variety of segment lengths




Long wires

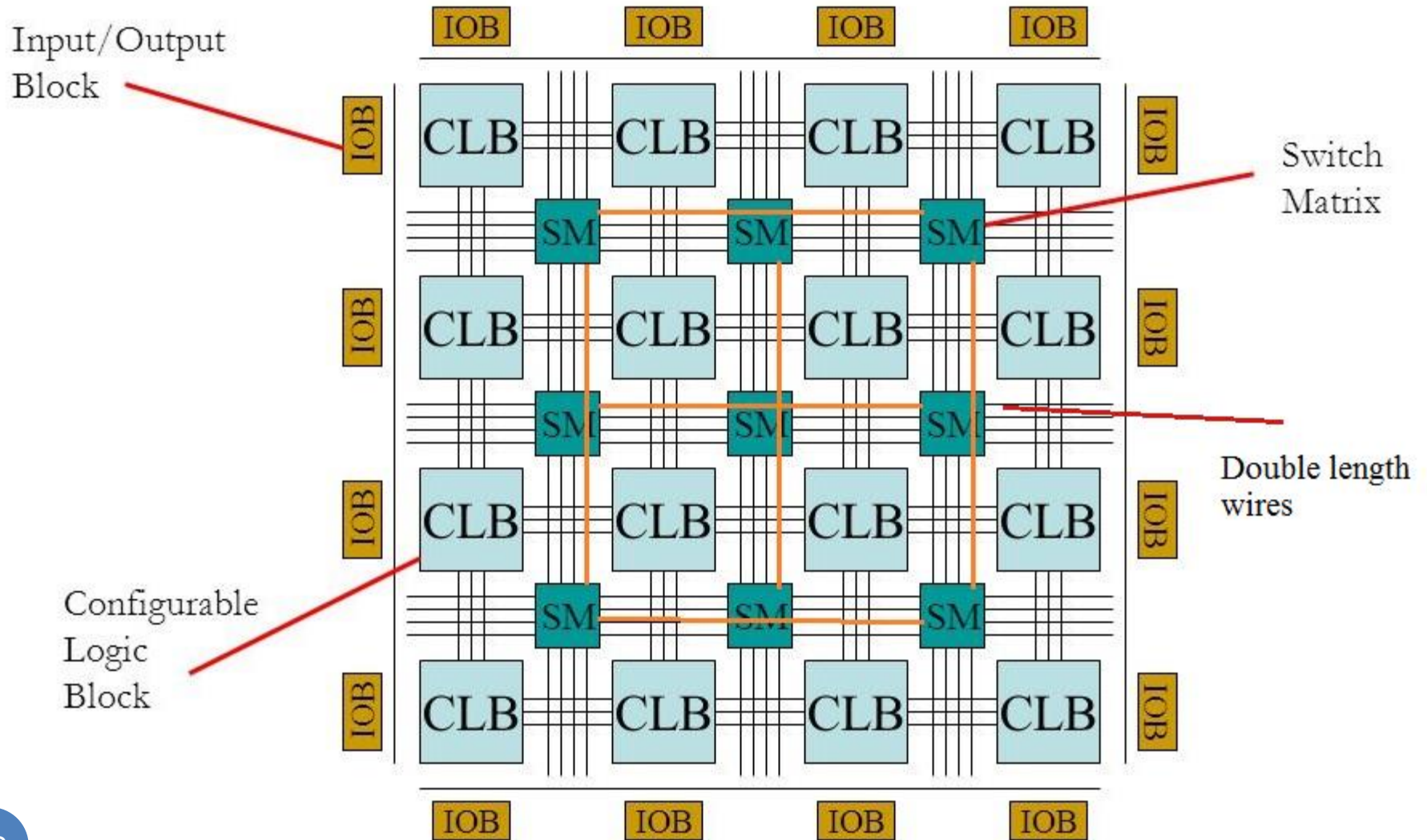

Spartan-3 FPGAs

 - Spartan: Cost-effective FPGA family of Xilinx
 - Spartan-6 is the last generation of the family
 - Cheaper and smaller than Virtex (the high-performance FPGAs of Xilinx)
- The industry's first 90 nm FPGA
- Different generations: Spartan-3, Spartan-3E, Spartan-3A



Spartan-3

- In the CAD lab, you will work with Spartan-3 XCS400 FPGAs


Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM Bits	Block RAM Bits	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S50	50K	1,728	16	12	192	768	12K	72K	4	2	124	56
XC3S200	200K	4,320	24	20	480	1,920	30K	216K	12	4	173	76
XC3S400	400K	8,064	32	28	896	3,584	56K	288K	16	4	264	116
XC3S1000	1000K	17,280	48	40	1,920	7,680	120K	432K	24	4	391	175
XC3S1500	1500K	29,952	64	52	3,328	13,312	208K	576K	32	4	487	221
XC3S2000	2000K	46,080	80	64	5,120	20,480	320K	720K	40	4	565	270
XC3S4000	4000K	62,208	96	72	6,912	27,648	432K	1,728K	96	4	633	300
XC3S5000	5000K	74,880	104	80	8,320	33,280	520K	1,872K	104	4	633	300

Logic cell

- Logic cell: LUT + Flip-flop
- The additional features in a slice, such as the wide multiplexers, carry logic, and arithmetic gates, add to the capacity of a slice
 - Implementing logic that would otherwise require additional LUTs
- Benchmarks show that the overall slice is equivalent to 2.25 simple logic cells

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM Bits	Block RAM Bits	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S50	50K	1,728	16	12	192	768	12K	72K	4	2	124	56
XC3S200	200K	4,320	24	20	480	1,920	30K	216K	12	4	173	76
XC3S400	400K	8,064	32	28	896	3,584	56K	288K	16	4	264	116
XC3S1000	1000K	17,280	48	40	1,920	7,680	120K	432K	24	4	391	175
XC3S1500	1500K	29,952	64	52	3,328	13,312	208K	576K	32	4	487	221
XC3S2000	2000K	46,080	80	64	5,120	20,480	320K	720K	40	4	565	270
XC3S4000	4000K	62,208	96	72	6,912	27,648	432K	1,728K	96	4	633	300
XC3S5000	5000K	74,880	104	80	8,320	33,280	520K	1,872K	104	4	633	300

Spartan-3 architecture

 


Spartan-3 components

- Configurable Logic Blocks (CLB)
- Flexible Synchronous Memory (BlockRAM)
- Programmable Input Output Blocks (IOB)
- Dedicated multipliers

Configurable Logic Blocks (CLB)


- Main logic resource for implementing synchronous as well as combinatorial circuits
- Arranged in a regular array of rows and columns

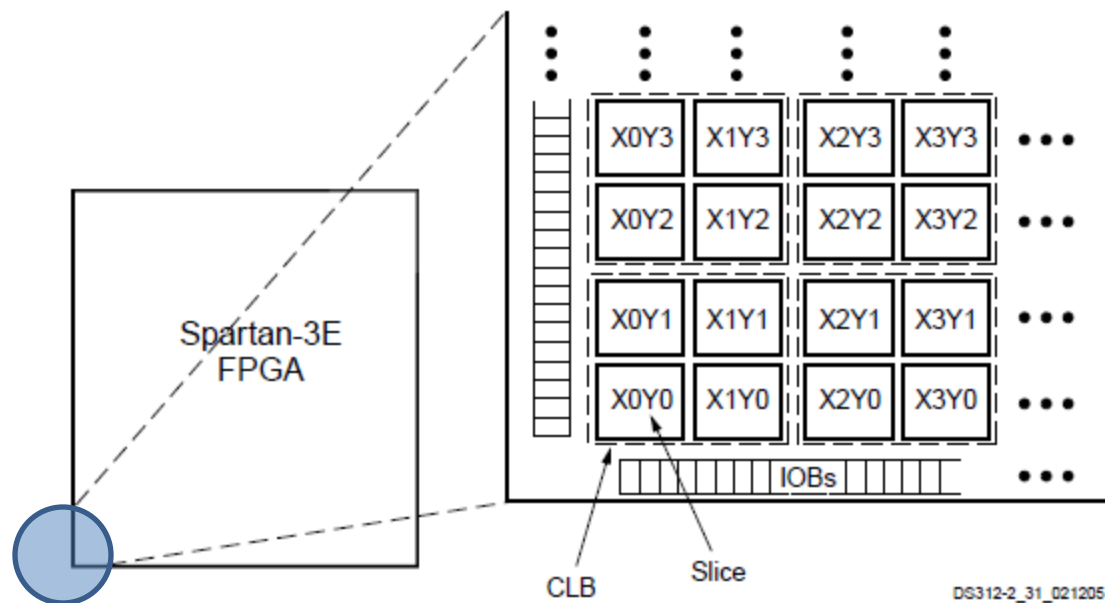

DS312-2_31_021205


CLB and slice

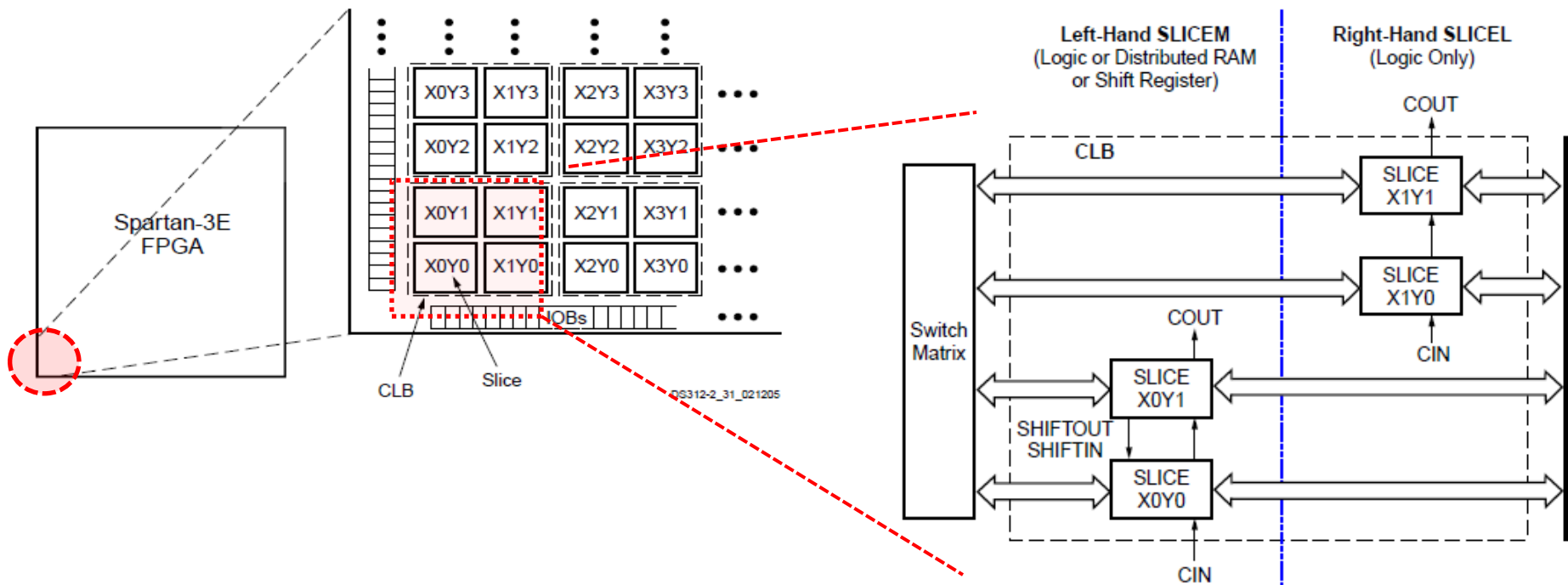- Each Spartan-3 CLB contains four slices
- Fast interconnects among the slices of a CLB




SLICEM and SLICEL

 - Slices are grouped in pairs in two columns
- Left-hand SLICEM (Memory)
 - In addition to logic implementation, LUTs can be configured as memory or 16-bit shift register
- Right-hand SLICEL (Logic)
 - LUTs can be used as logic only




CLB and slice- slice architecture

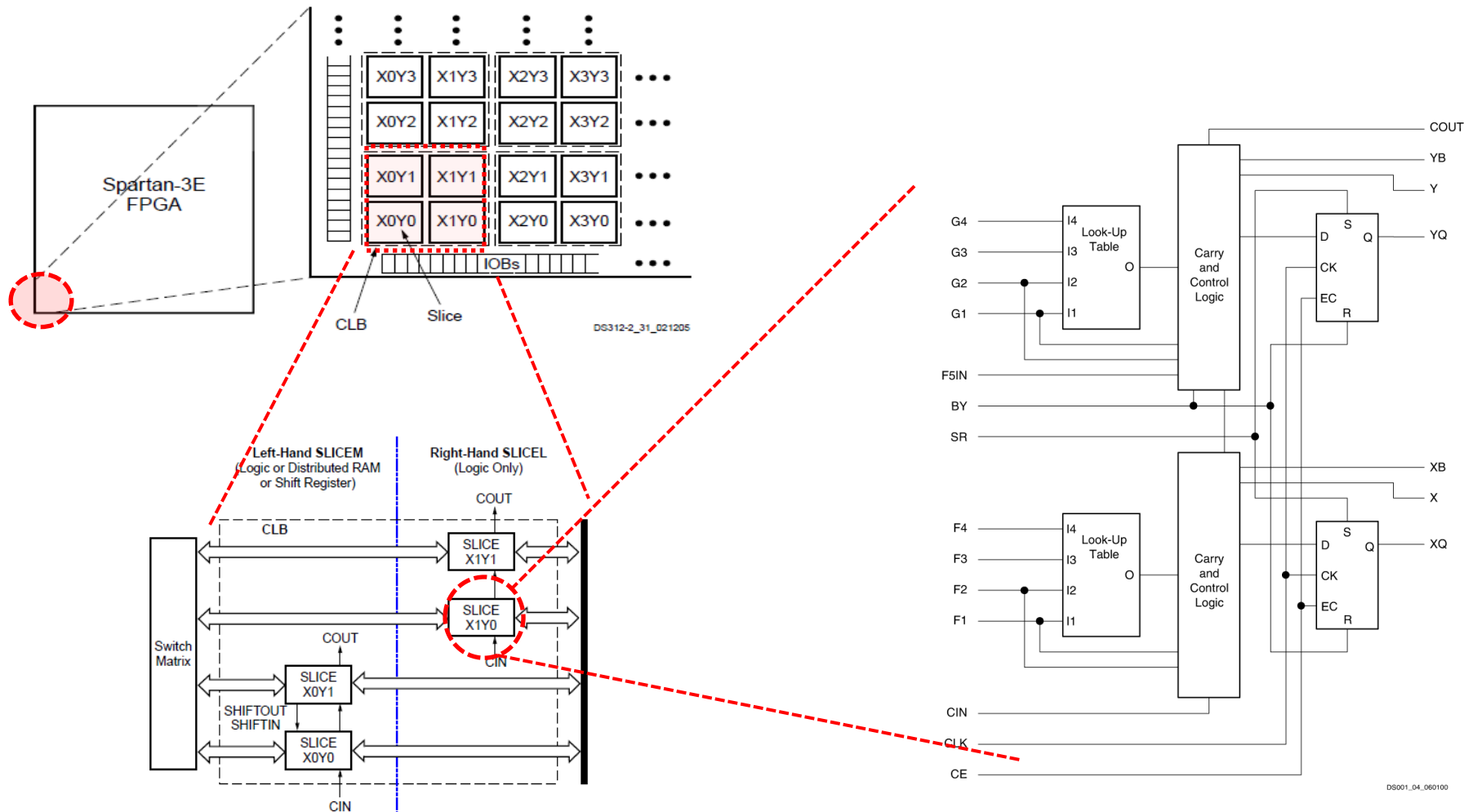


SLICE structure

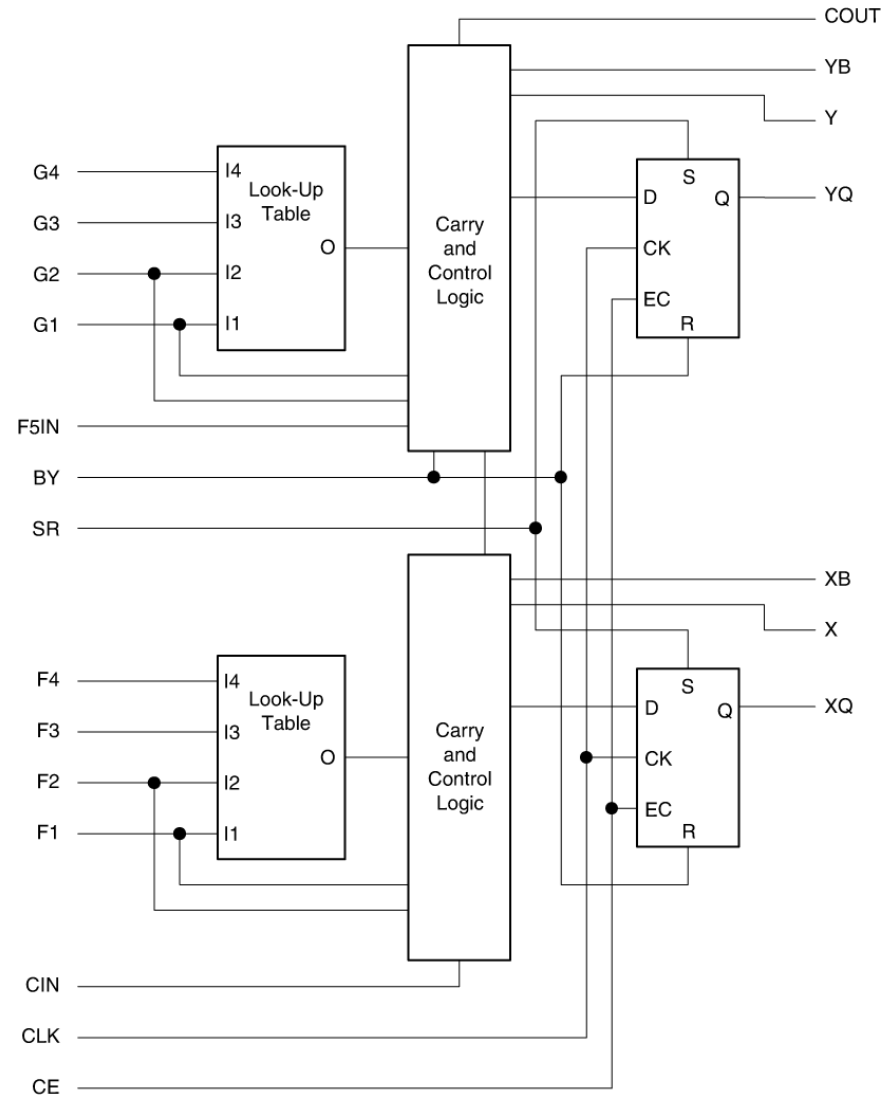- SLICEL: two 4-input look-up tables followed by two D flip-flops plus carry & control logic (for arithmetic operations)
- SLICEM: like SLICEL, but with some extra logic to enable LUT4s to instead be used as RAM or a shift register





SLICE structure

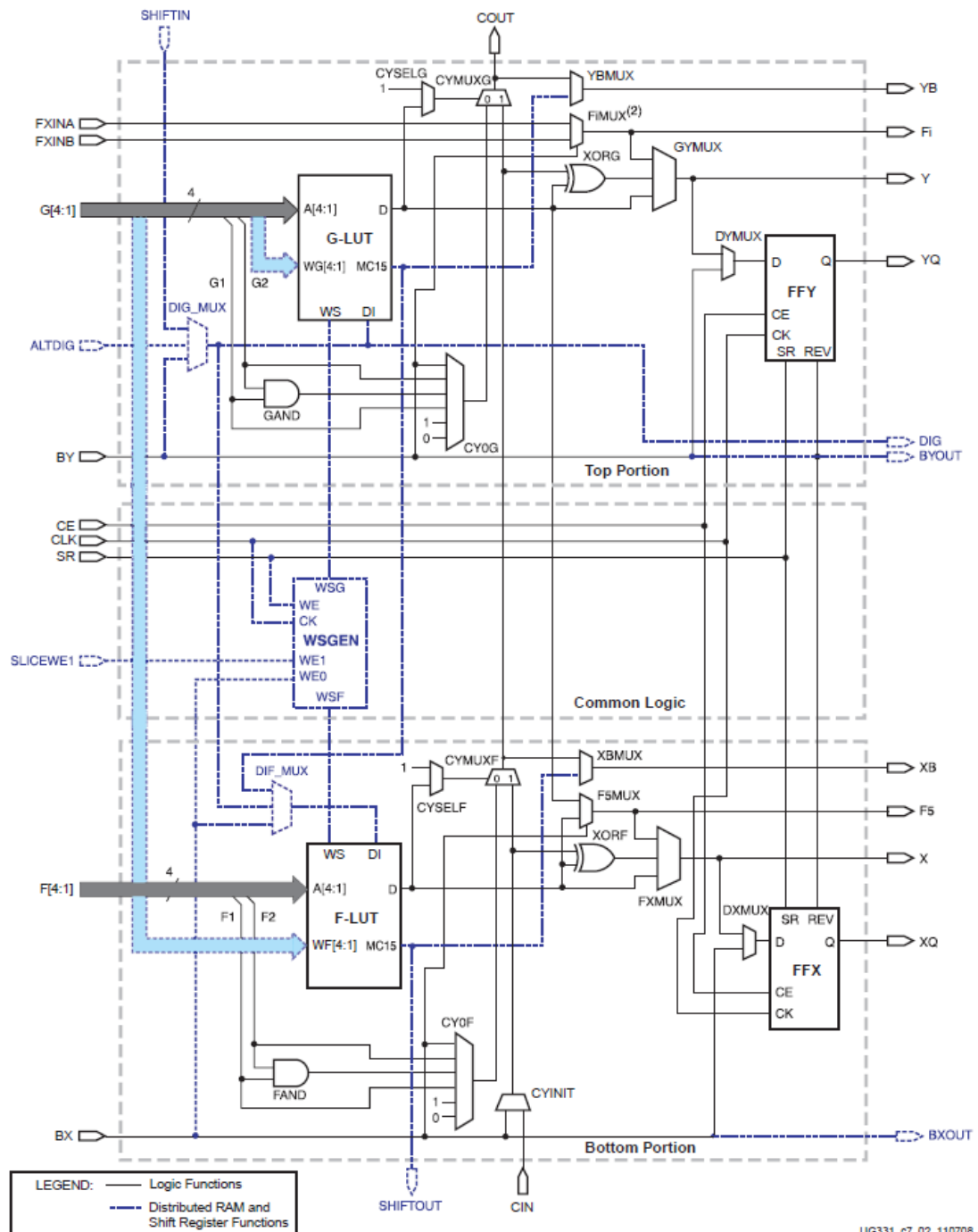- The details of the slice architecture
- More detailed than the figure in the previous slide!
 - The control and carry logic are shown
- The blue parts are the extra logic of SLICEM




Main logic paths

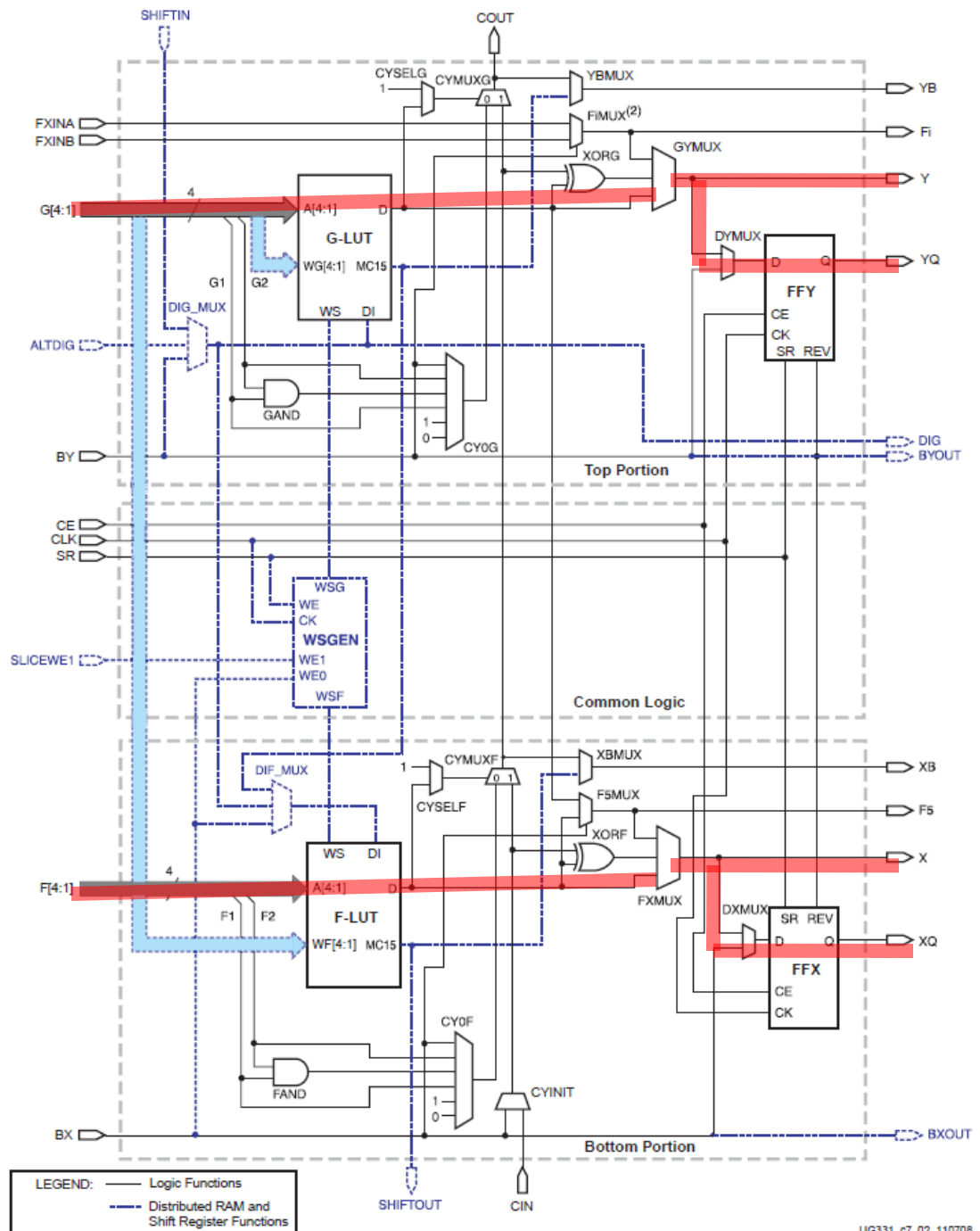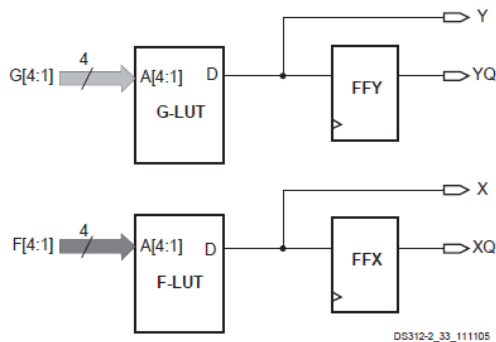- Two 4-input functions, combinational or sequential output




Wide multiplexers

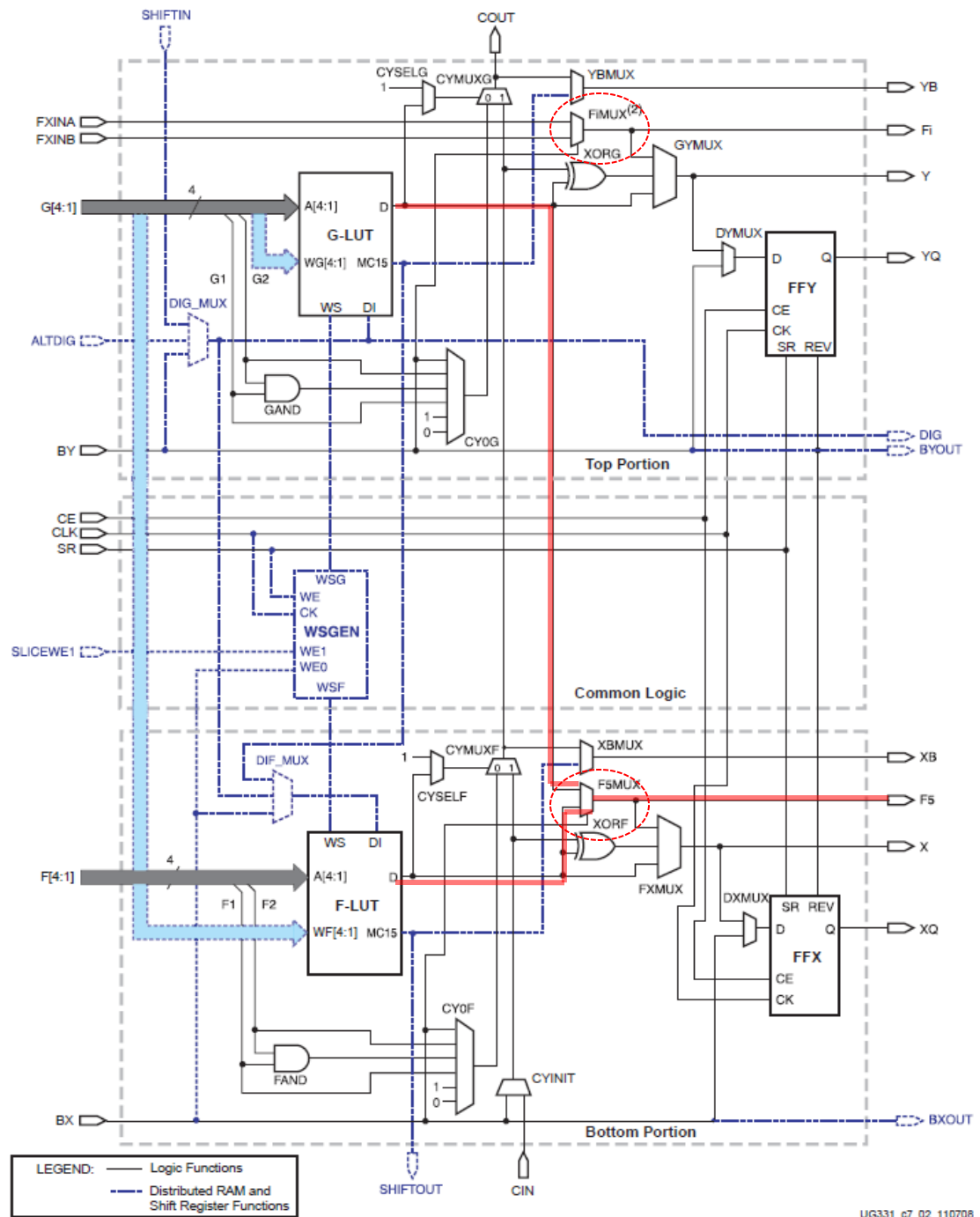- Combine LUTs to build more complex logic operations
- Each slice has two of these multiplexers
 - F5MUX in the bottom
 - FiMUX in the top



Wide multiplexers in a CLB

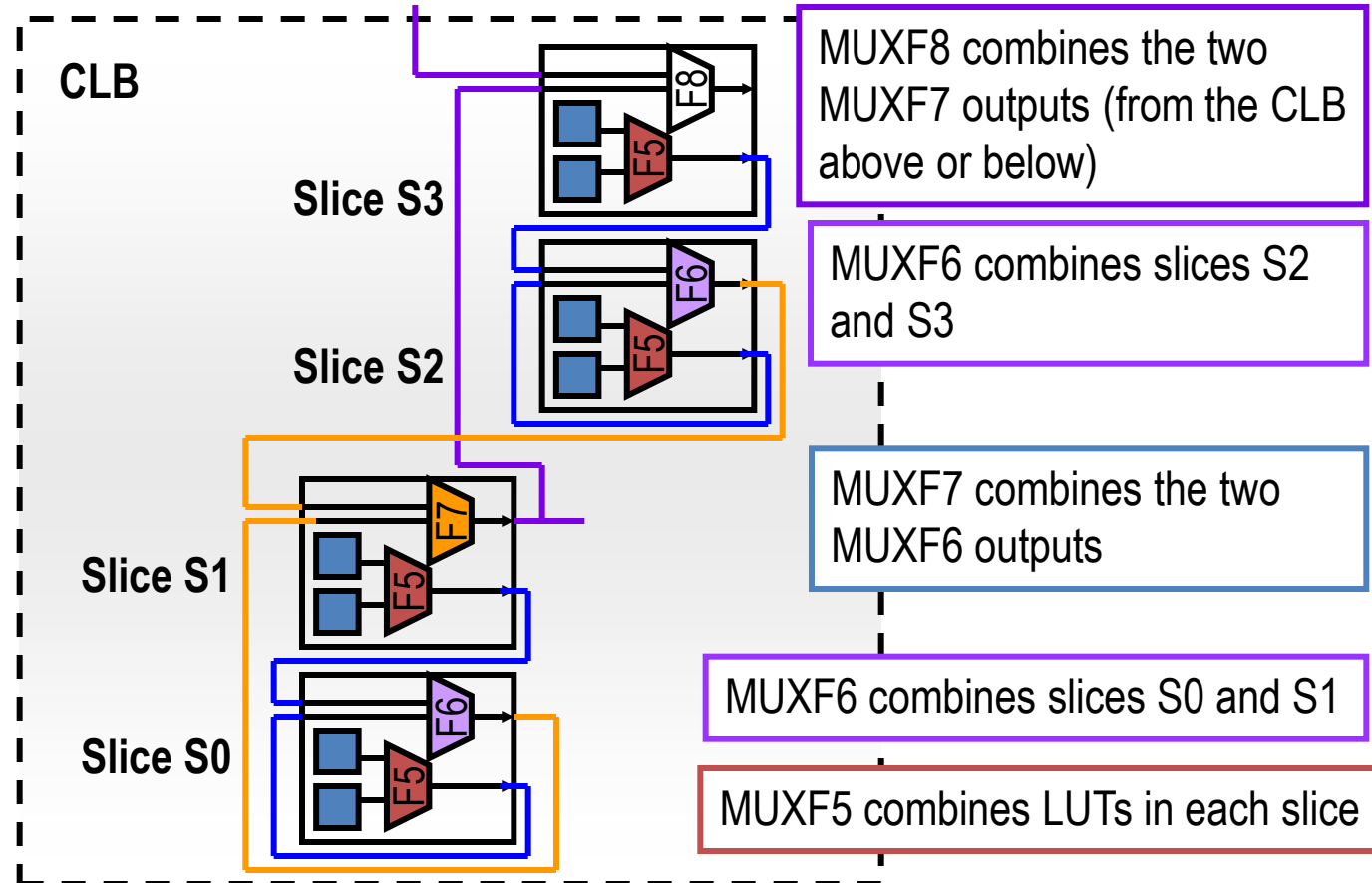- F5MUX :
multiplexes the two LUTs in a slice
- F_i MUX :
- $i=6,7,8$
- multiplexes the F5MUX and F_i MUX of the same slice or other slices



Cascading LUTs

- Previous slide used wide multiplexers to implement large functions
- It can implement any function with 4, 5, 6, 7, and 8 inputs
- Some functions can be re-formed and implemented by cascading LUTs, rather than combining with multiplexers
 - May use smaller number of LUTs
 - Not applicable always, depends on the function

Cascading LUTs


- Example: 2 cascaded LUTs for a 7-input function.
- How many LUTs when using wide MUXes?

$$Y = ABCDE \text{ or } ABCDFG$$

$$Y = (ABCD) \text{ and } (E \text{ or } FG)$$


$$ABCD = X$$

$$Y = X \text{ and } E \text{ or } FG$$

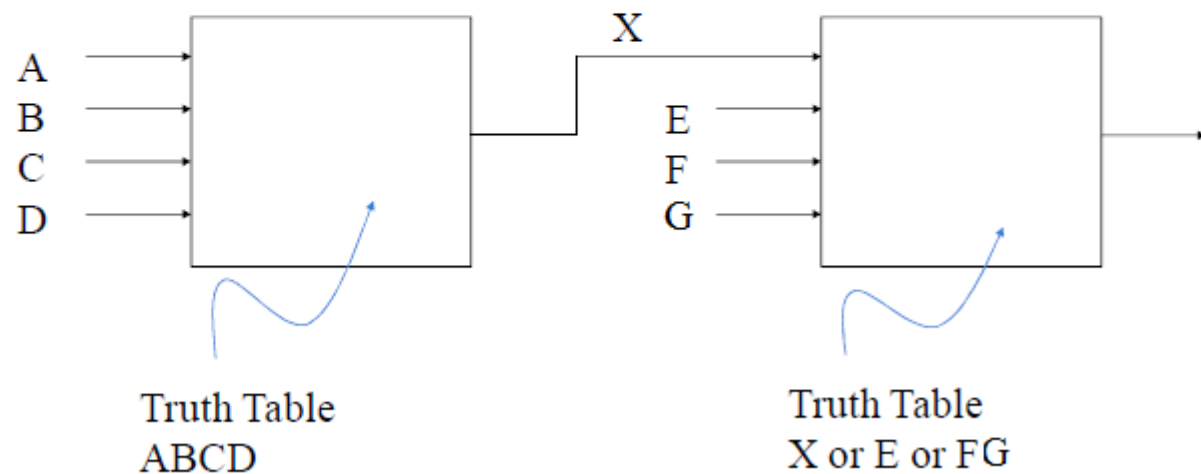


CLB arithmetic logic

 - Adder is the base of many arithmetic operations
- Special logic in CLBs to implement adder
- Adders are traditionally constructed by cascading full adders
- Good modularity but long latency due to the serial operation
 - Carry must be propagated from the first to the last full adder: the n^{th} . adder cannot start until the carry of the $n-1^{\text{th}}$. full adder is calculated



UG331_c11_01_072906

Ripple carry adder

 

- Critical path in a k-bit ripple carry adder


CLB arithmetic logic

- We can predict the carry of each full adder (FA) from its inputs
- If $a=b=0$, no carry will be produced by the FA (regardless of the `carry_in`)
- If $a=b=1$, a carry will be produced by the FA (regardless of the `carry_in`)
- If $a \neq b$, the input carry will be propagated to the output

A	B	Propagate	Generate
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Carry look-ahead adder

Conventional serial
full adder

 


UG331_c11_01_072908

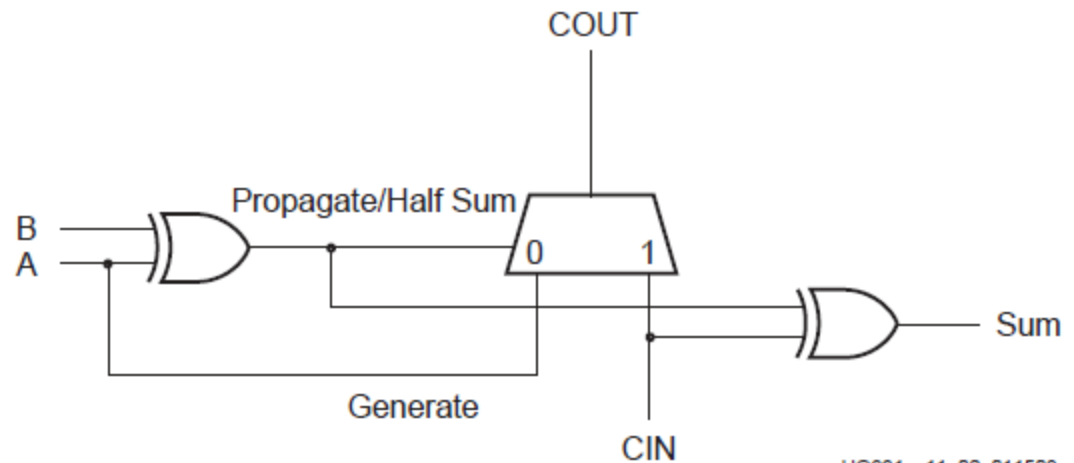Full-adder with carry
look-ahead
Implemented in
SPARTAN-3



UG331_c11_02_011508


Carry look-ahead adder in SPARTAN

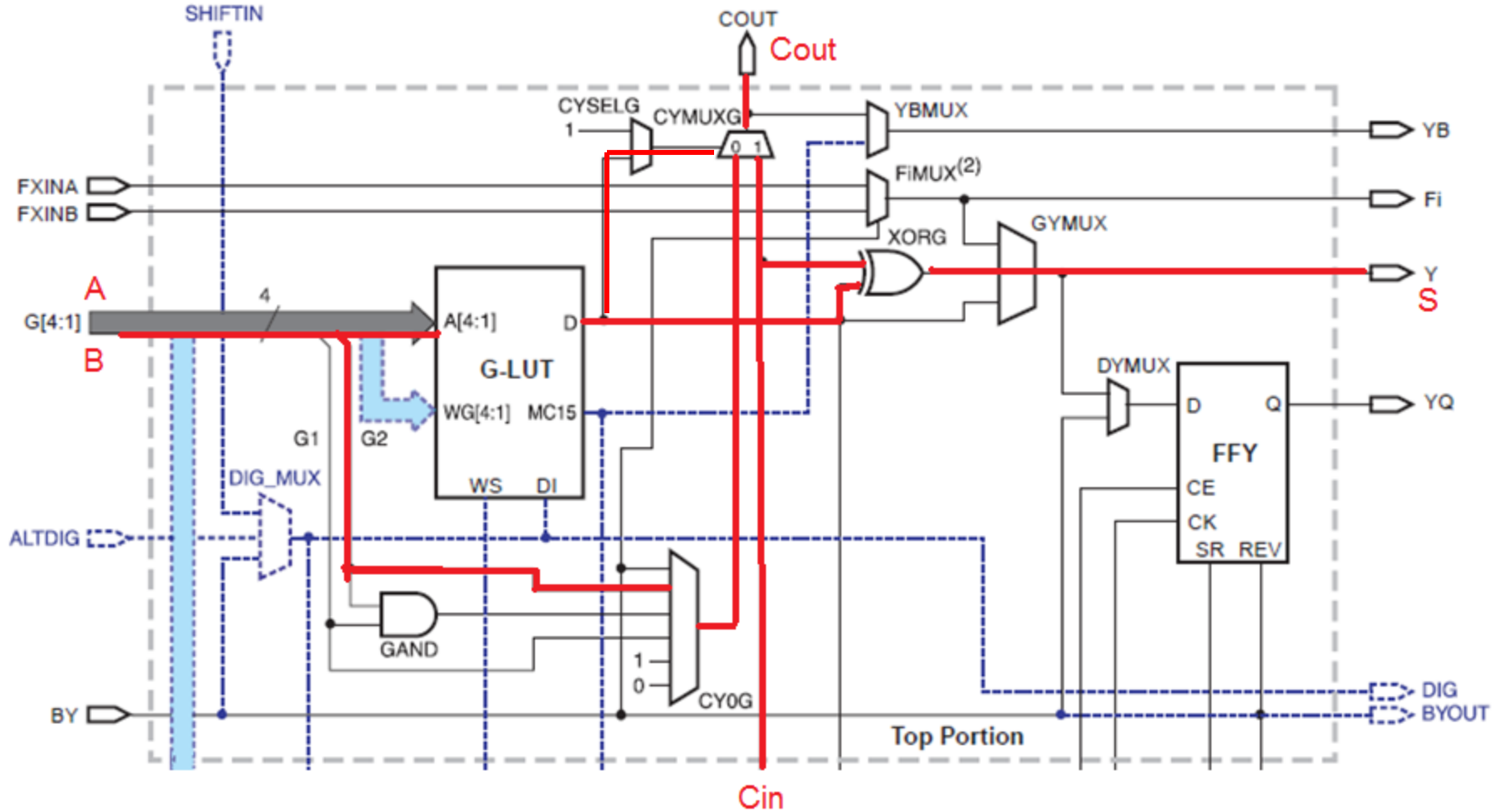

- Adder data-path in one slice (the upper part of slice is shown)
- Implements an FA to add two 1-bit inputs A and B



Adder by Spartan-3

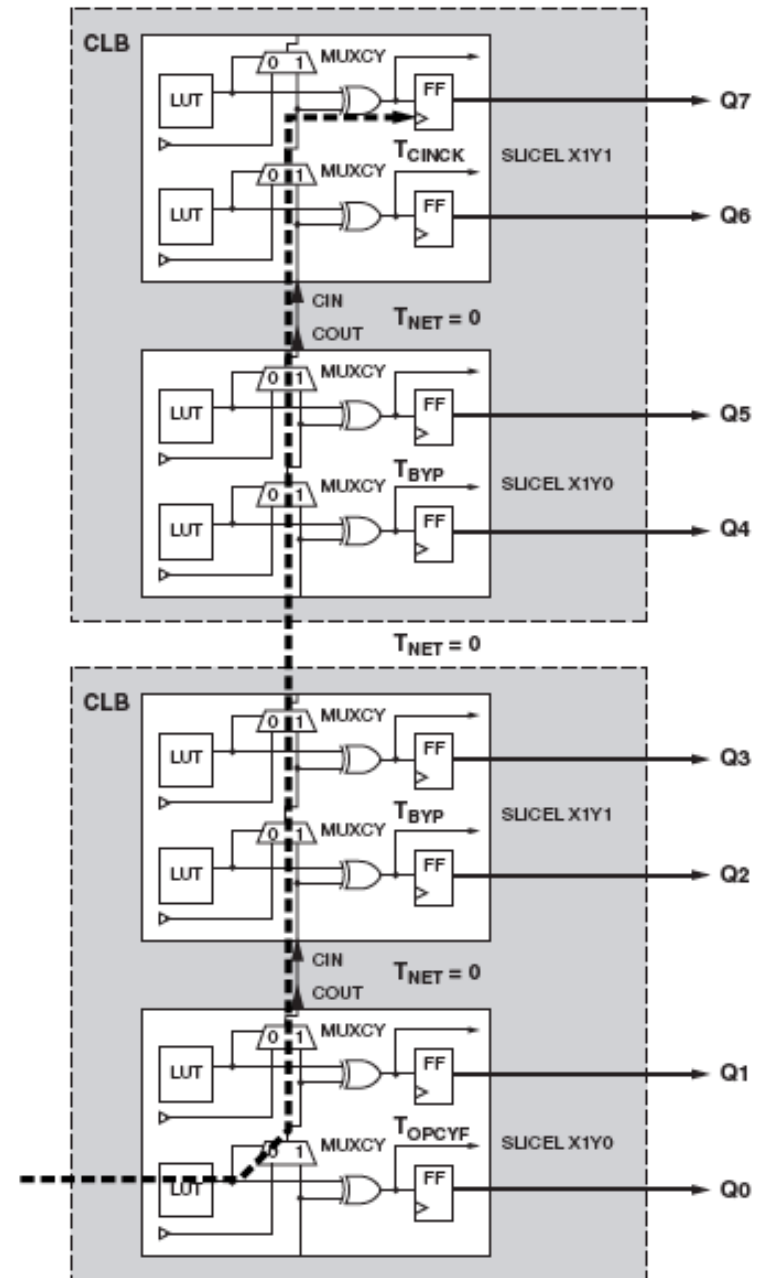- 8-bit adder using 4 slices of Spartan-3




Distributed RAM

 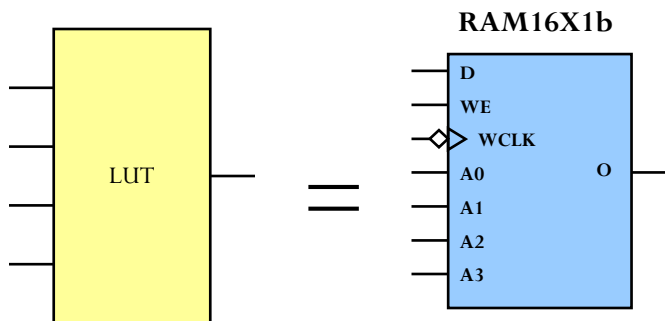- A LUT in a SLICEM may be configured for use as a RAM
 - Implement single and dual port
 - Cascade LUTs to increase size
- Synchronous write only
- Reads may be synchronous or asynchronous.




RAM32X1b

 

or

RAM16X2b

 


Spartan-3 components

- Configurable Logic Blocks (CLB)
- Block RAM
- Programmable Input Output Blocks (IOB)
- Dedicated multipliers

Block RAM

 - On-chip memory blocks of Static RAM
- Both single and dual-port memories
- XC3S400 has two columns of RAM
- Each column contains 8 blocks of RAM (the figure shows 6 blocks!)
- Each block is 18-kilobit synchronous RAM
 - Each block has 16 kb data, 2kb parity
 - Total RAM = $18 \text{ kb} \times 16 \text{ blocks} = 288 \text{ kb}$



Block RAM organization

- Can be used as RAM blocks with different lengths and widths
- 2kb of the RAM is devoted to parity bits
- 16Kx1 configuration can be used as a large lookup table




Configuration	Depth	Data bits	Parity bits
16K x 1	16Kb	1	0
8K x 2	8Kb	2	0
4K x 4	4Kb	4	0
2K x 9	2Kb	8	1
1K x 18	1Kb	16	2
512 x 36	512	32	4

Spartan-3 components

- Configurable Logic Blocks (CLB)
- Block RAM
- Dedicated multipliers
- Programmable Input Output Blocks (IOB)

Multiplier

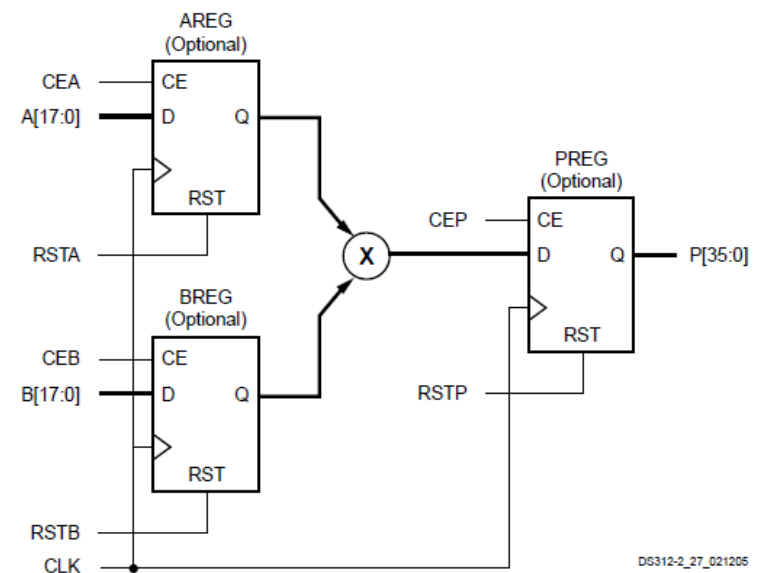  - 18×18 multipliers
- Very fast: single cycle latency
- 16 multipliers in Spartan-3
- Can use registers in input and output of each multiplier
 - For pipelined operation




Spartan-3 components

- Configurable Logic Blocks (CLB)
- Block RAM
- Dedicated multipliers
- Programmable Input Output Blocks (IOB)

I/O resources

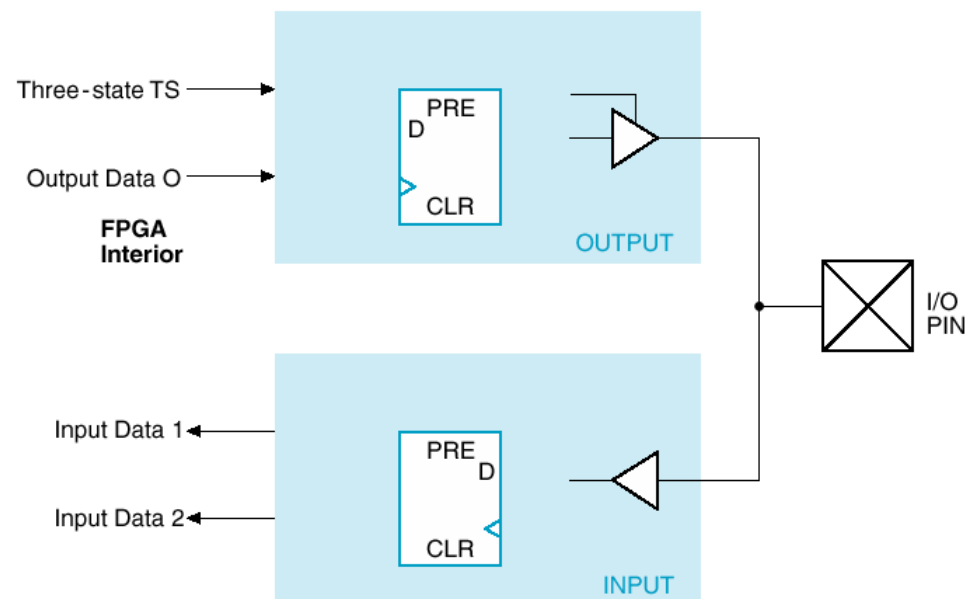
- 264 I/O pins in Spartan-3
- Can be configured as both input and output
- I/O pins have different architectural and electrical aspects
 - The most interesting aspect is the double data rate capability





Basic I/O block
More complex blocks in reality

Spartan-3 I/O- DDR

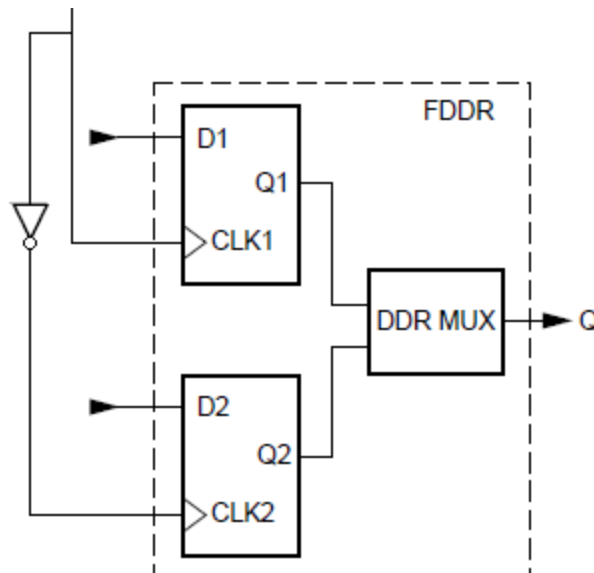- Double-Data-Rate (DDR) transmission describes the technique of sending data on both the rising and falling edges of the clock
- Doubles the bandwidth



Spartan-3 I/O- DDR

 
 


Spartan-3 components

- Configurable Logic Blocks (CLB)
- Block RAM
- Dedicated multipliers
- Programmable Input Output Blocks (IOB)
- Digital Clock Manager (DCM)


Clocking in FPGAs

 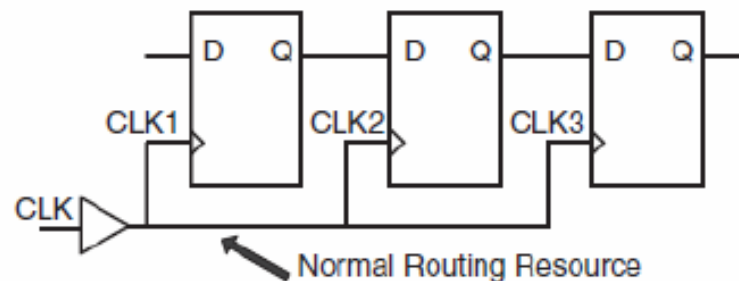- Clock skew is an important problem in clock distribution
- The clock **skew**, S , is the maximum delay from the clock input of one flip-flop to the clock input of another flip-flop.



Clocking in FPGAs- skew problem

- Clock skew is an important problem

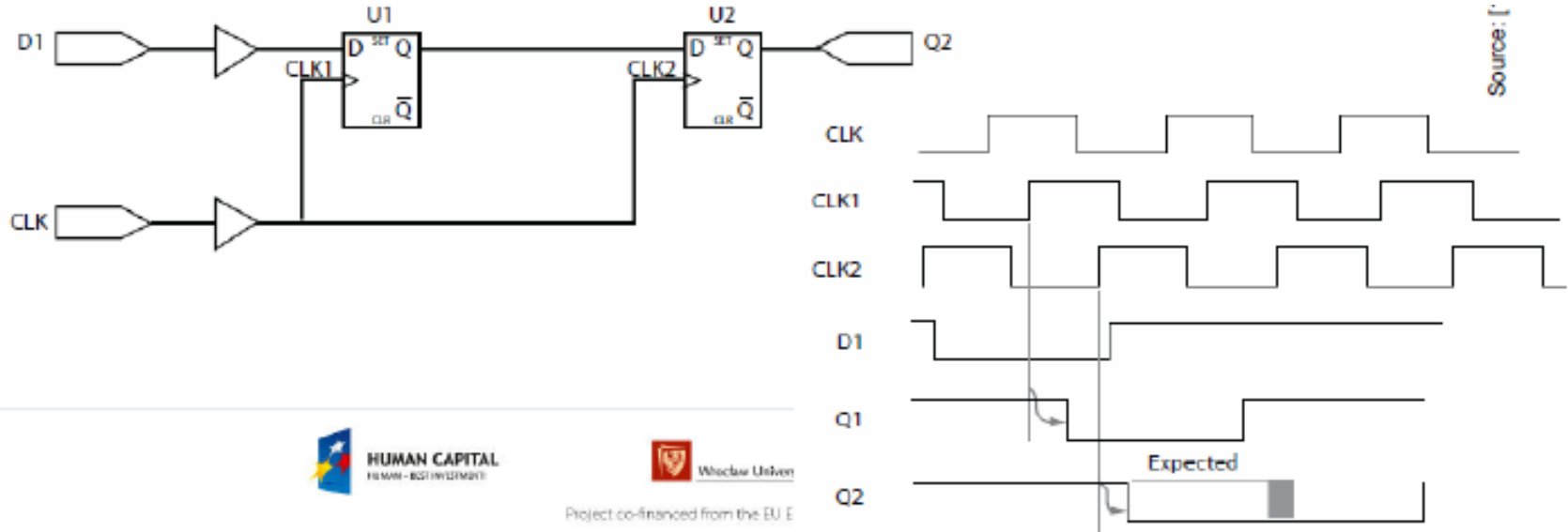

HUMAN CAPITAL
HUMAN - BEST INVESTMENT




Wrocław University



Project co-financed from the EU E

Skew solution

 
- Don't use gated clocks
- Balance clock paths (tree distribution)
- The most common way: H-tree:
 - All FFs (black squares)
receive clock at the same time



Realistic H-trees

  


FPGA clock tree

 



Spartan-3 clock tree

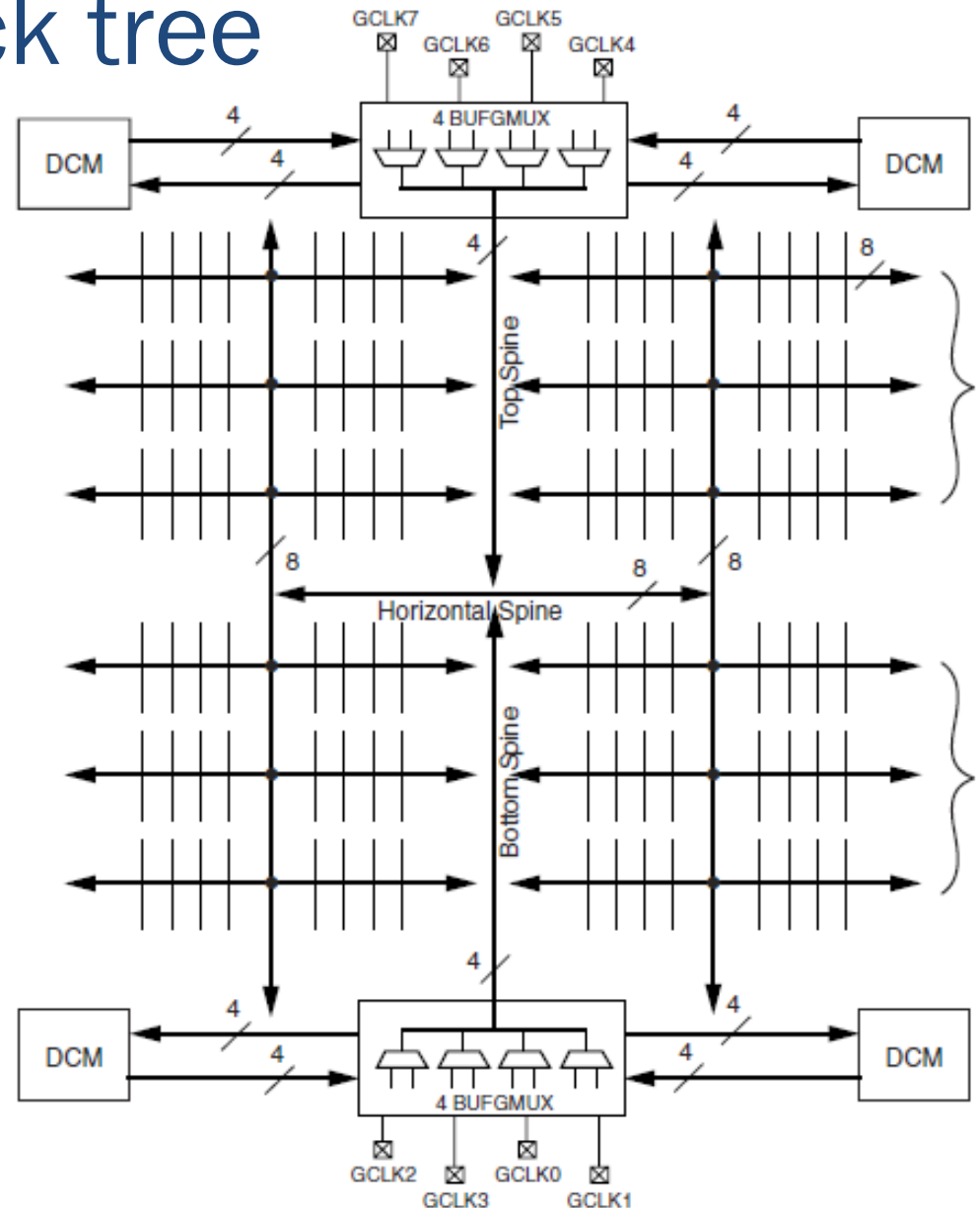- Spartan-3 devices have eight Global Clock input pads called GCLK0 through GCLK7
- The eight BUFGMUX components (4 at the top and 4 at the bottom side) can multiplex between clock sources
 - From input pins or from DCMs



Digital Clock Manager (DCM)

  - Used to generate clock signal for FPGA out of the external clock signal
- Phase Shift a clock signal
- Multiply or divide an incoming clock frequency or synthesize a completely new frequency by a mixture of clock multiplication and division



Phase shift

Modern Xilinx FPGAs

45nm	28nm	20nm	16nm
SPARTAN ⁶	VIRTEX ⁷ KINTEX ⁷ ARTIX ⁷	VIRTEX ⁷ UltraSCALE KINTEX ⁷ UltraSCALE	VIRTEX ⁷ UltraSCALE+ KINTEX ⁷ UltraSCALE+

- Virtex: high capacity (up to 2M logic cells), high-performance
- Kintex: high performance, but smaller than Virtex
- Artix: mid-range, low-cost and low-power
 - Replacement of Spartan

Modern Xilinx FPGAs


- All 7 series families share the same basic building blocks
- The mixture and number of these resources varies across families

 **Logic Fabric**
LUT-6 CLB

 **Precise, Low Jitter Clocking**
MMCMs


 **On-Chip Memory**
36Kbit/18Kbit Block RAM

 **Enhanced Connectivity**
PCIe[®] Interface Blocks


 **DSP Engines**
DSP48E1 Slices

 **Hi-perf. Parallel I/O Connectivity**
SelectIO[™] Technology

 
 **Hi-performance Serial I/O Connectivity**
Transceiver Technology



Artix[™]-7 FPGA

 


Kintex[™]-7 FPGA

 

Virtex[®]-7 FPGA



Artix-7

 - Spartan-6 is the last member of the family
- Replaced by the Artix family





CLB in Artix-7

  - Each CLB has two slices
- Slices still can be either SliceM and SliceL




Slice structure

- Each slice has four 6-input LUTs

 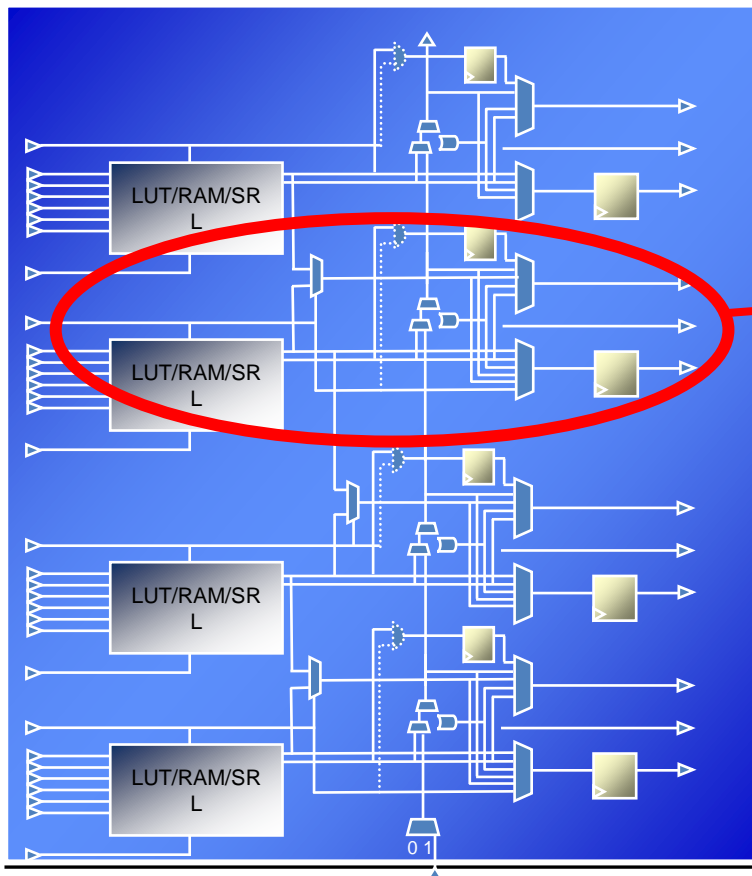


6-Input LUT with Dual Output

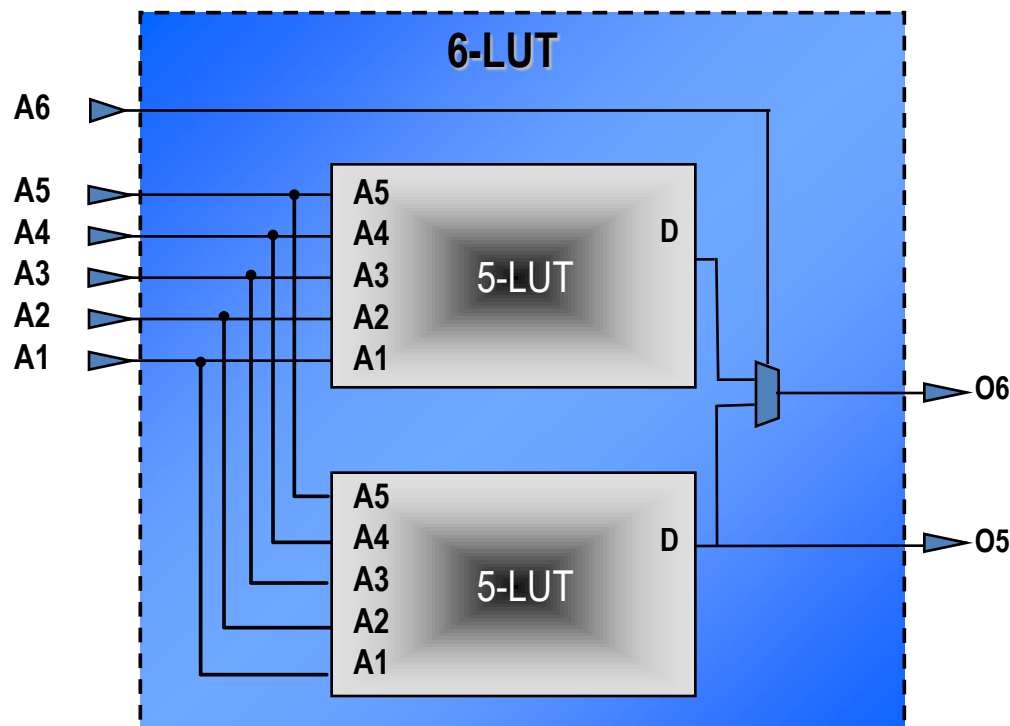- 6-input LUT can be two 5-input LUTs with common inputs
 - Any function of six variables or two independent functions of five variables




Wide Multiplexers

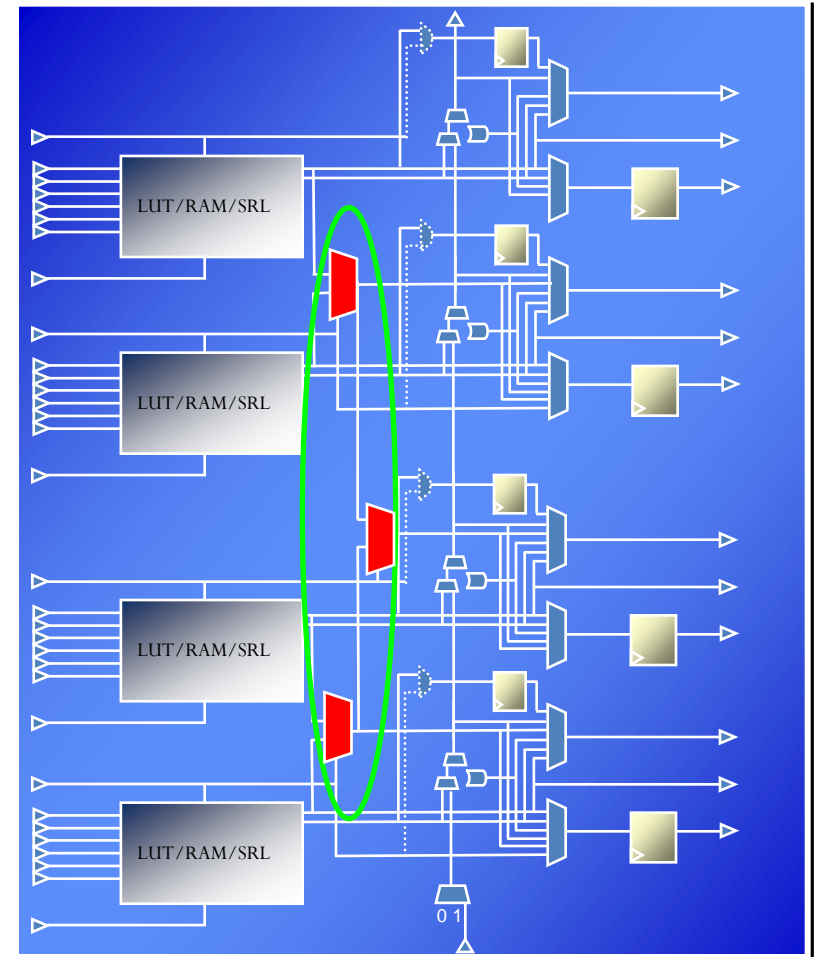- Each F7MUX combines the outputs of two LUTs together
 - Can implement an arbitrary 7-input function
 - Can implement an 8-1 multiplexer
- The F8MUX combines the outputs of the two F7MUXes
 - Can implement an arbitrary 8-input function




Carry Chain

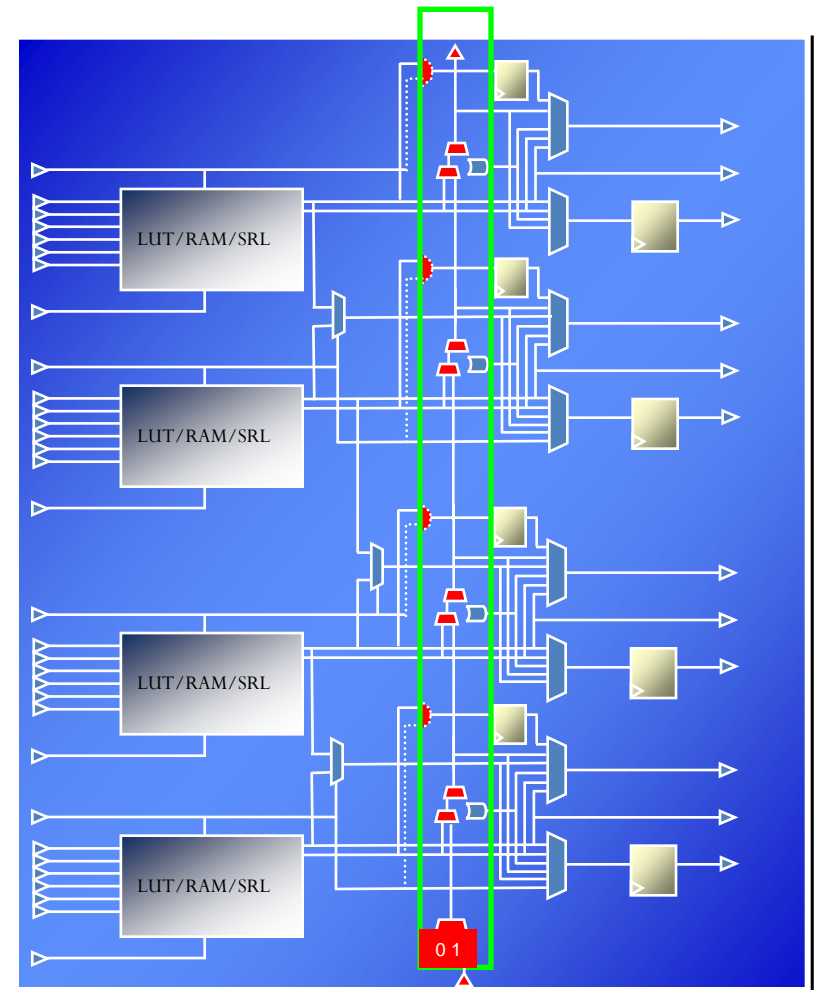- Carry chain can implement fast arithmetic addition and subtraction
 - Carry out is propagated vertically through the four LUTs in a slice
 - The carry chain propagates from one slice to the slice in the same column in the CLB above
- Carry look-ahead
 - Combinatorial carry look-ahead over the four LUTs in a slice
 - Implements faster carry cascading from slice to slice




Interconnects

 - Connections between CLBs and other resources use the fabric routing resources
- Routes connect resources vertically, horizontally, and **diagonally**
- Wires have different lengths (**why?**):
 - Horizontal: Single, Dual, Quad, Long (12)
 - Vertical: Single, Dual, Hex, Long (18)
 - Diagonal: Single, Dual, Hex





Gigabit Transceiver

 


- Modern FPGAs have dedicated Transceiver blocks for high-speed communication


Why differential signalling?

  

Generating a Differential Pair

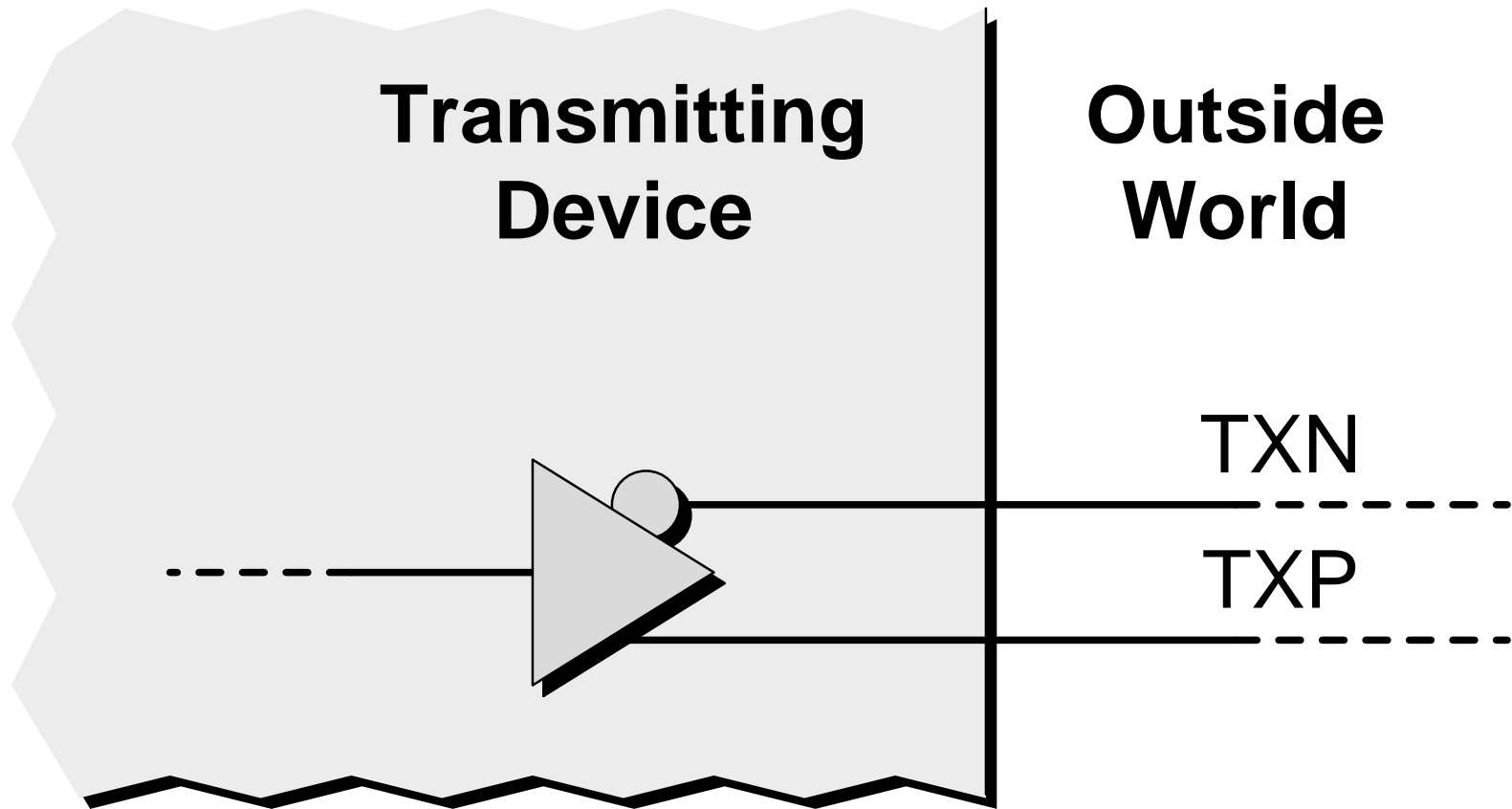

DSP block

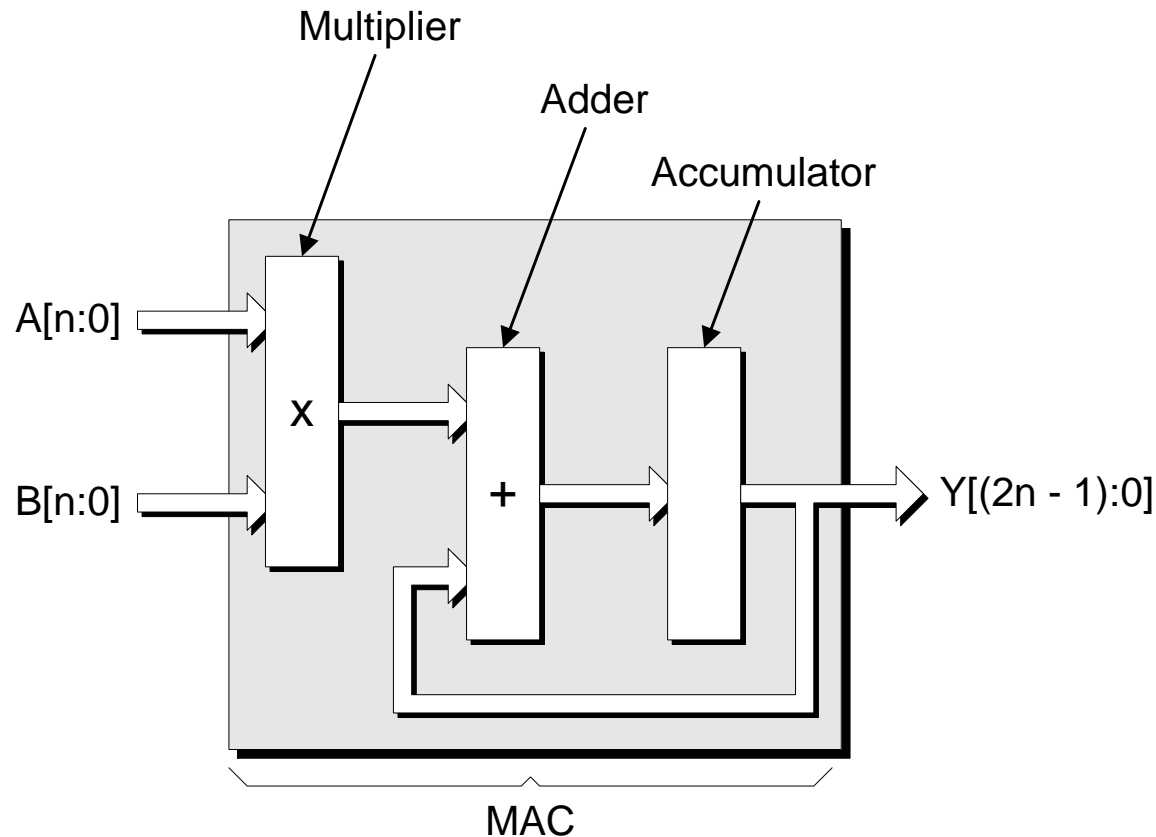


- In 7-series, we have Multiply and accumulate (MAC), instead of simple multiplier

I/O pins

- In addition to more CLBs, Artix family has more I/O pins
- Most Spartan 3 FPGAs have QFP package(or some variant of it)
- Modern FPGA have BGA package(or some variant of it)
- What is BGA? QFP?

QFP

 - Quad Flat Package
- Pins are on each of the four sides of the chip
- Limited number of pins, but easier to mount on board



BGA

- Ball Grid Array
- Pins are placed on the whole bottom surface of the device, instead of just the perimeter.
- More pins, but hard to solder and mount on board

