




1. What is the problem with partial decoding?

2. There are four types of memory modules:


- 16k x 4 bit ROM for 28000-2FFFF (08000 – 0FFFF)
  - 256k x 8 bit SRAM for F0000-FFFFF (E0000 – EFFFF)
  - 512k x 2 bit SRAM for 00000-1FFFF (20000 – 3FFFF)
  - 64K x 1bit SRAM for 60000 – 7FFFF (40000 – 5FFFF)
1. How many modules are required from each type for an 8088 processor.  
2. Design the circuit.

3. for 8086:

   
4. Repeat the problem (how many modules and design)  
5. Draw the timing diagram of 8086 for the execution of this instruction and show which memory modules will be activated (MOV [300H],AX – where AX: 8B3FH and DS:F000H (E000H))




 
256k x 8 bit SRAM for F0000-FFFFF (E0000 – EFFFF)




 • 512k x 2 bit SRAM for 00000-1FFFF (20000 – 3FFFF)



• 64K x 1bit SRAM for 60000 – 7FFFF (40000 – 5FFFF)

 
 


 

for 8086:



- 16k x 4 bit ROM for 28000-2FFFF (08000 - 0FFFF)
- 256k x 8 bit SRAM for F0000-FFFFF (E0000 - EFFFF) ←
- 512k x 2 bit SRAM for 00000-1FFFF (20000 - 3FFFF) ←
- 64K x 1bit SRAM for 60000 - 7FFFF (40000 - 5FFFF)

16k x 4  
14 bit


 
 



18 bit

15 bit

  

   512k x 2 bit SRAM for 00000-1FFFF (20000 - 3FFFF)



 

64K x 1bit SRAM for 60000 - 7FFFF (40000 - 5FFFF)

