

Microprocessor System Design

DRAM Interfacing


Omid Fatemi
(omid@fatemi.net)

Outline


- **A Dynamic cell**
- **Reading / Writing DRAM**
- **RAS / CAS signals**
- **DRAM in PC**
 - **RAS, CAS and address select generation**
 - **Address multiplexing**
- **Wait state generation for IO access**

Dynamic RAM

 
- Capacitor can hold charge
- Transistor acts as gate
- No charge is a 0
- Can close switch & add charge to store a 1
- Then open switch (disconnect)
- Can read by closing switch
 - Sense amps



Hydraulic Analogy

 


Reading

 

DRAM Refreshing


- **Refresh**
 - Destructive read
 - Also, there's steady leakage
 - Charge must be restored periodically

DRAM Logical Diagram

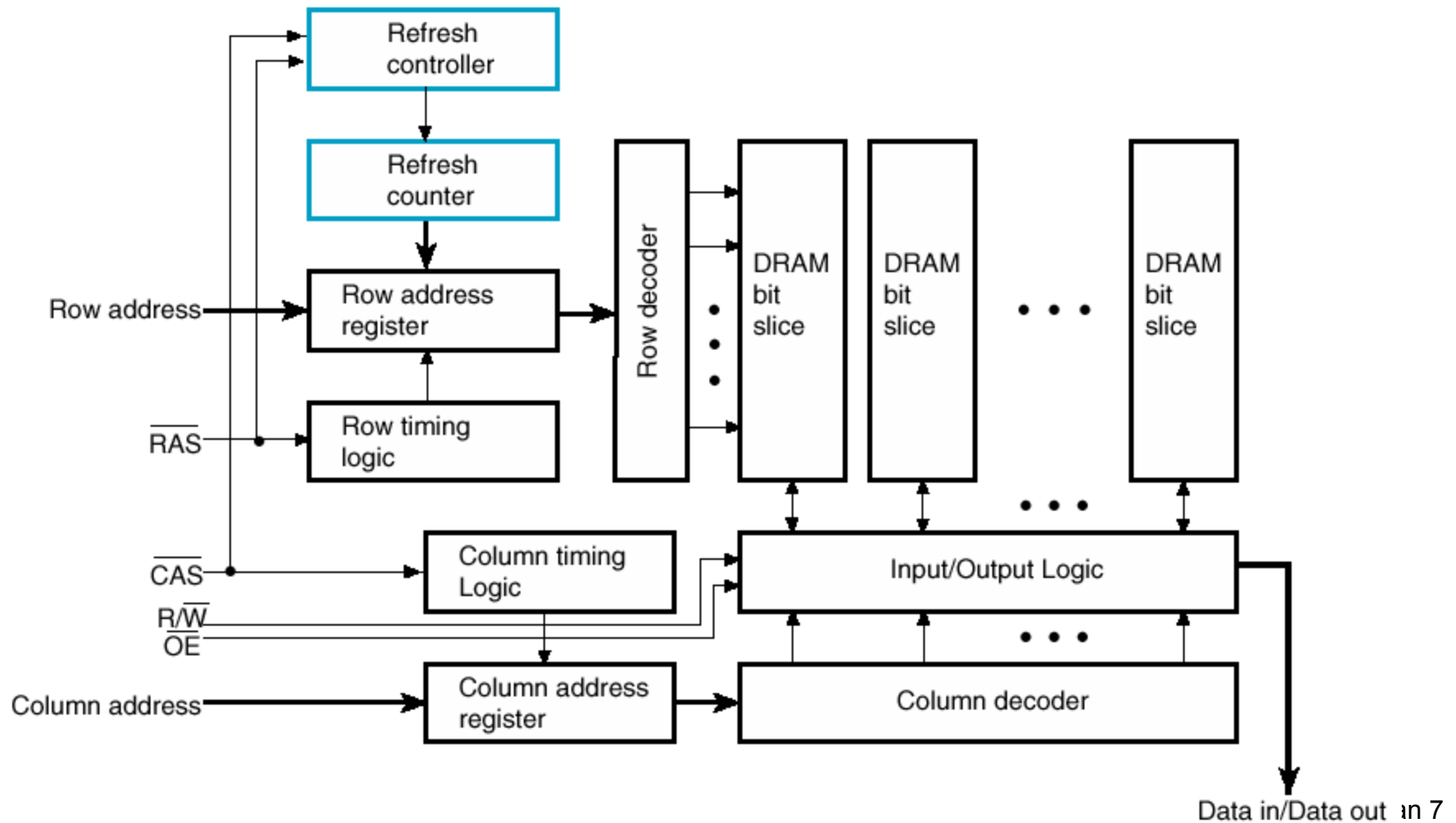


DRAM Read Signaling

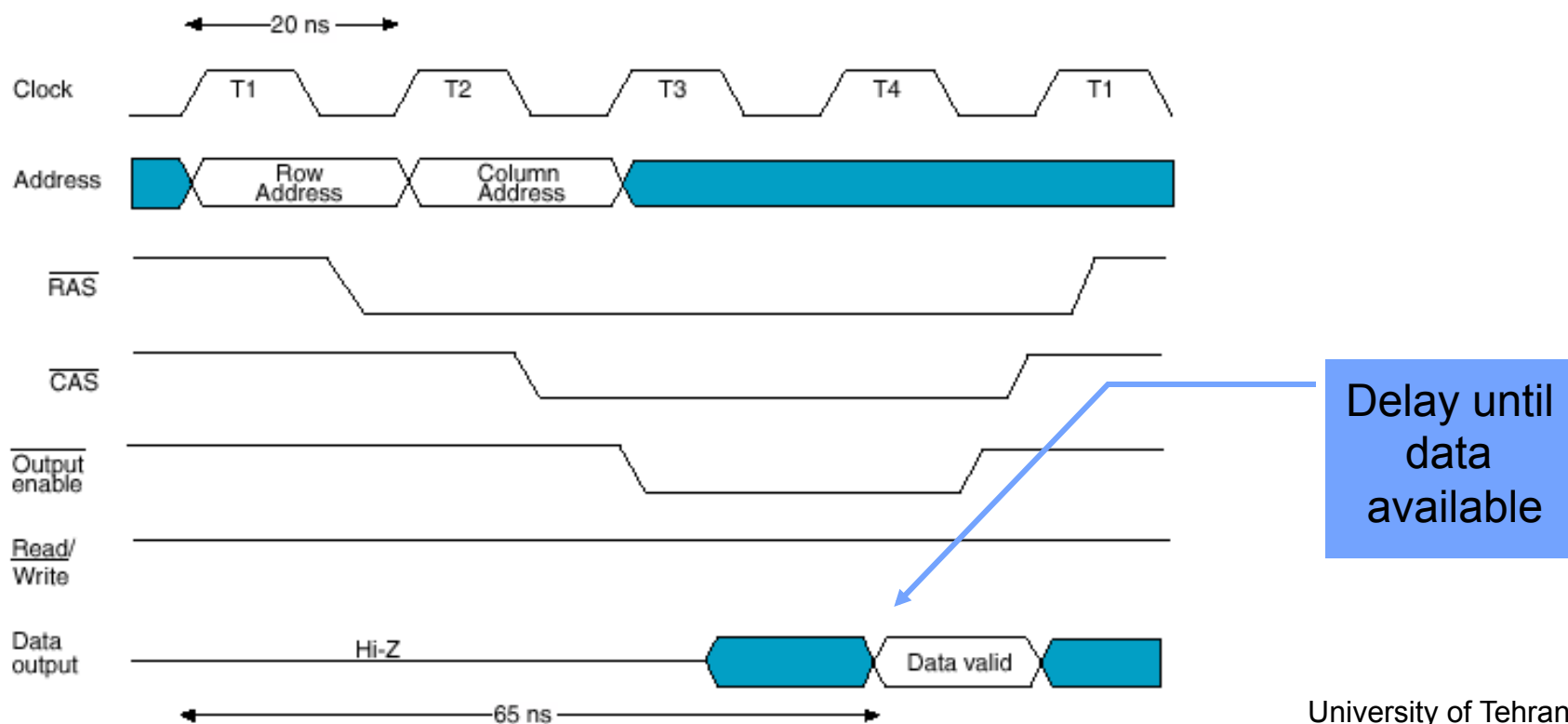- Lower pin count by using same pins for row and column addresses




Standard DRAM Timing

 


DRAM	RAS Access (t_{RAC}) (ns)	Read Cycle (t_{RC}) (ns)	RAS Precharge (t_{RP}) (ns)
MCM44100-60	60	110	45
MCM44100-70	70	130	50
MCM44100-80	80	150	60

(Reprinted by permission of Motorola Corporation, Copyright Motorola Corp. 1993)

DRAM Write Timing

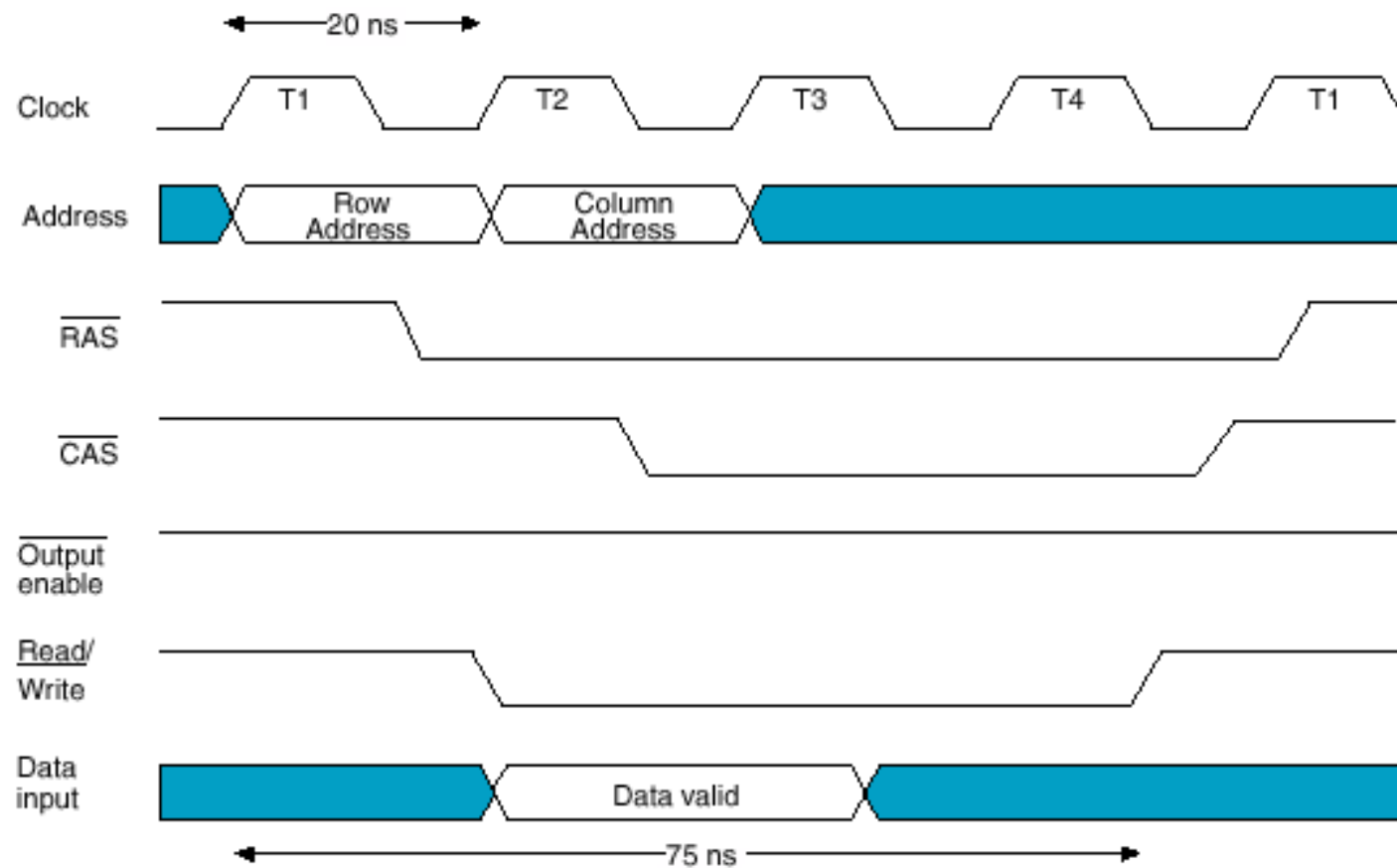

DRAM Address Select

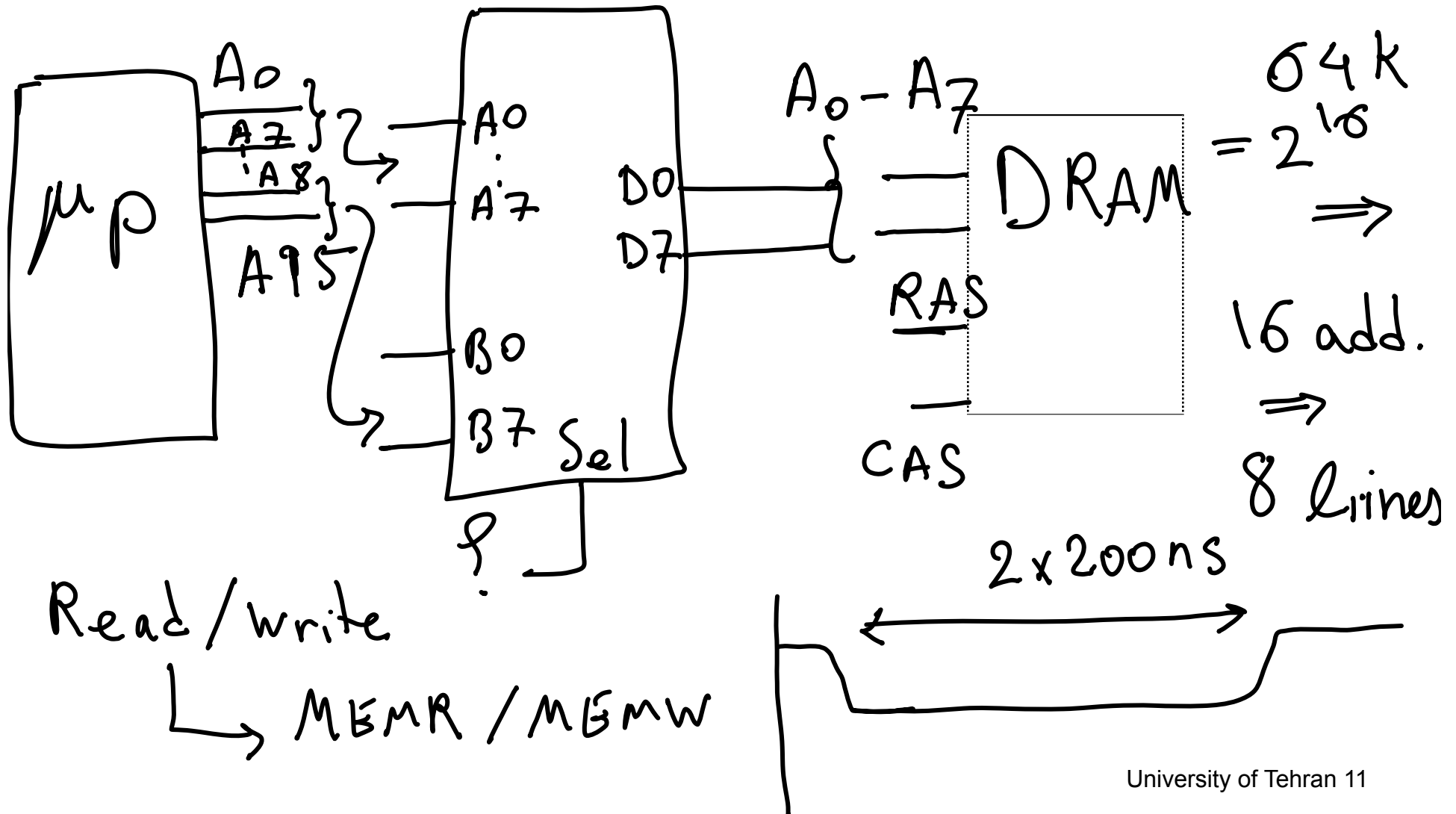


DRAM Timing (signal


T_0 : Row, Read, RAS generation)

T_1 : Col

T_2 : CAS

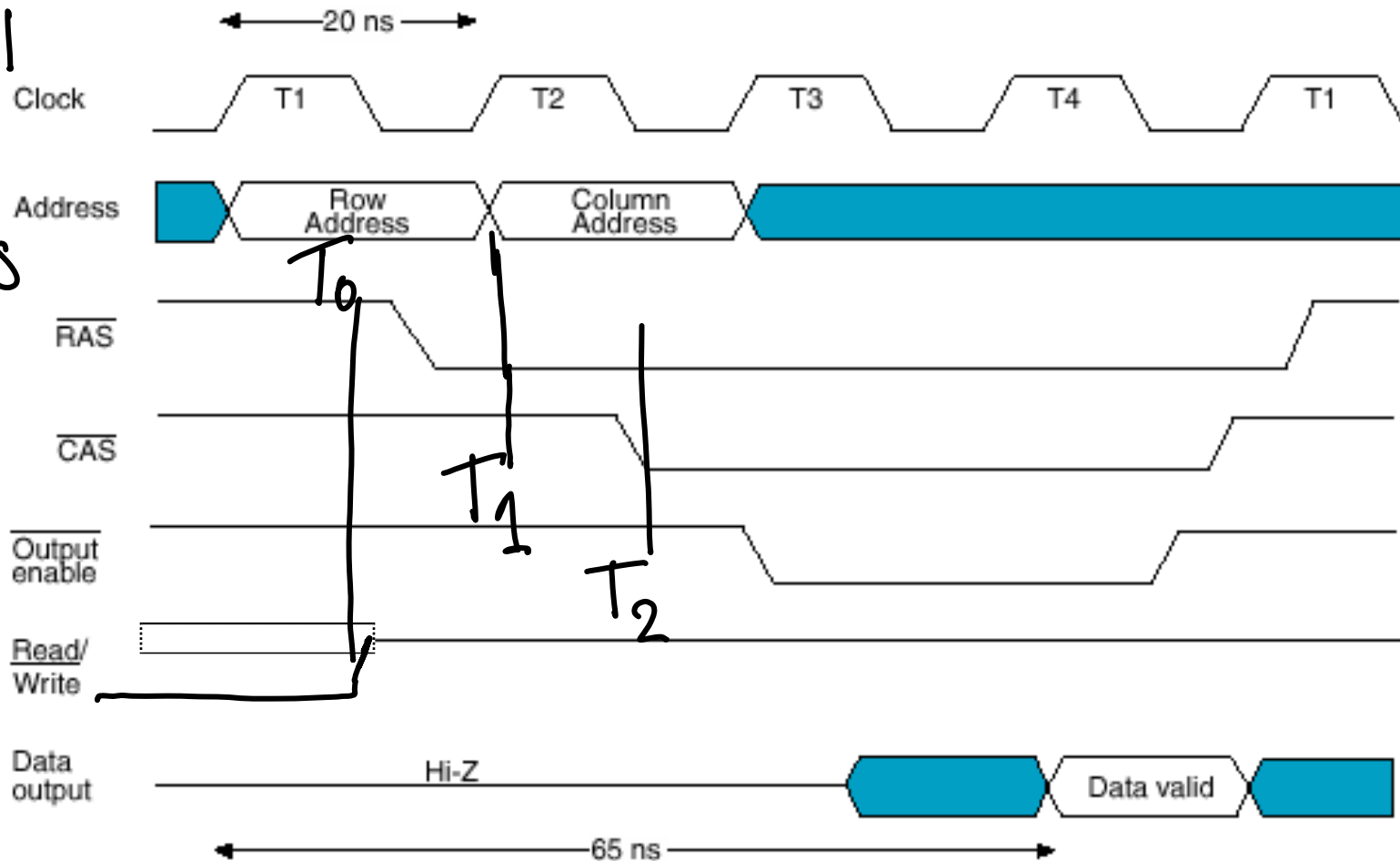

DRAM Connections in PC

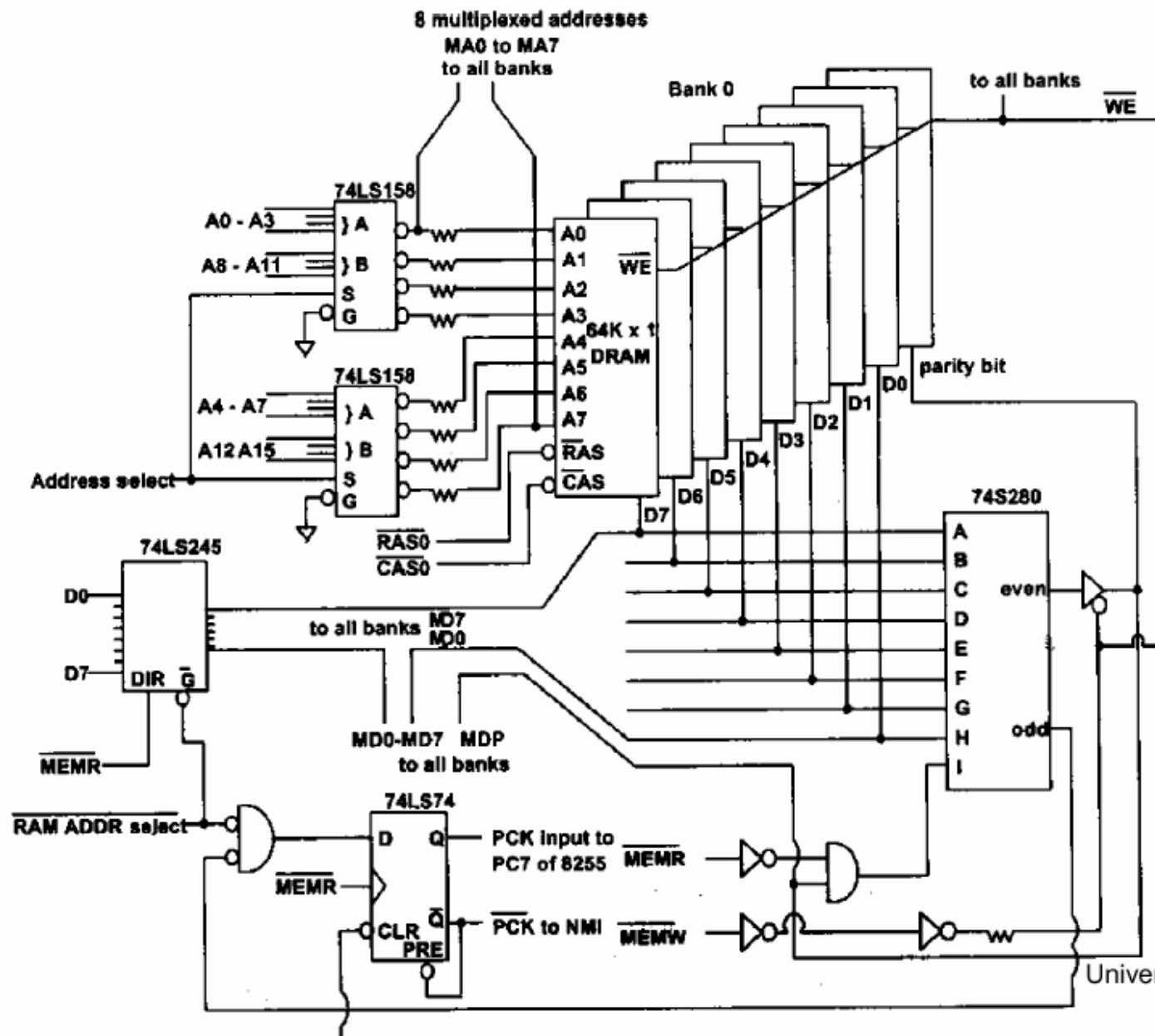

Parity?

PC RAM Interface

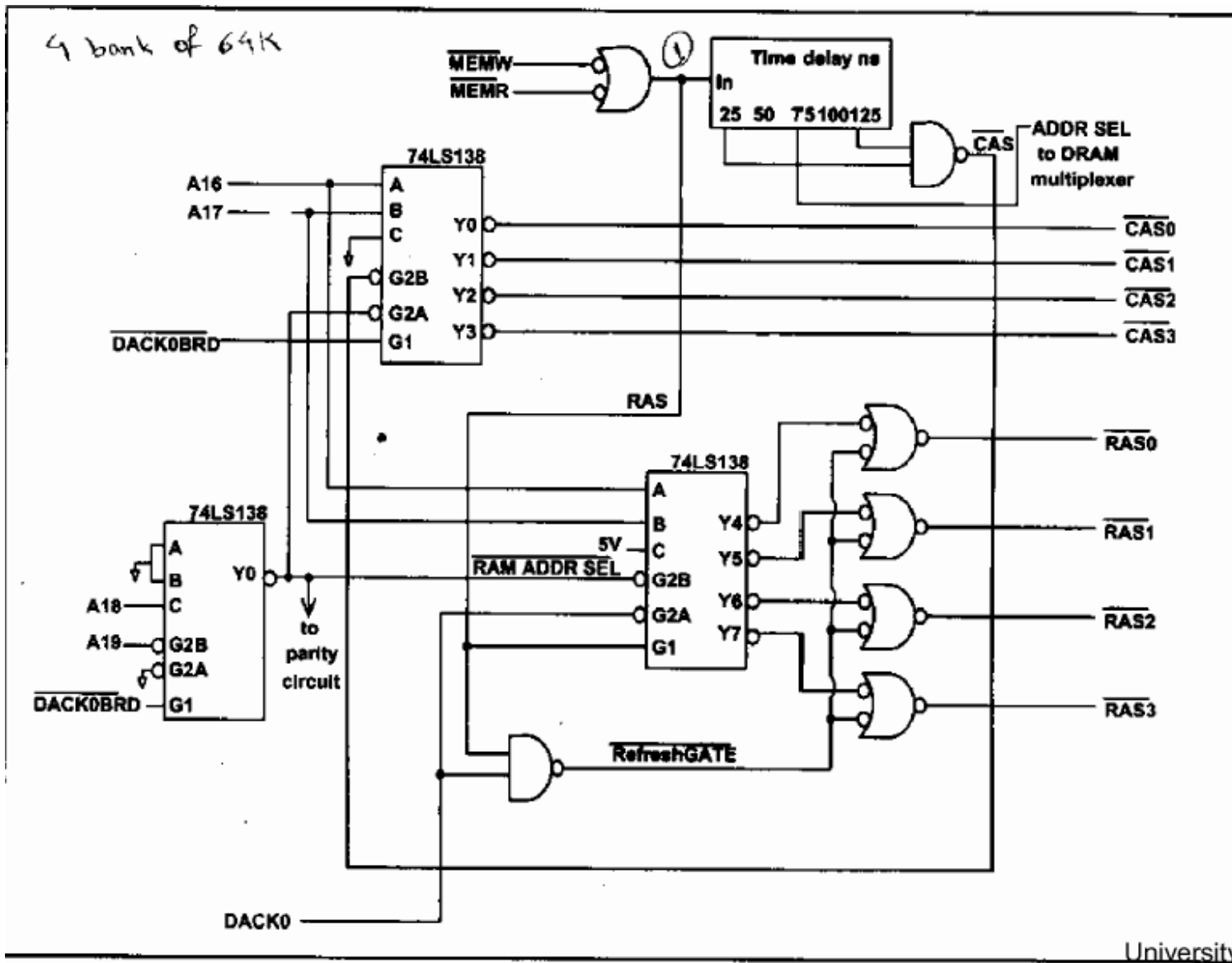


Figure 3-16. IBM PC DRAM Selection for 00000 - 3FFFF

(Reprinted by permission from "IBM Technical Reference" c. 1984 by International Business Machines Corporation)

Wait State Generation

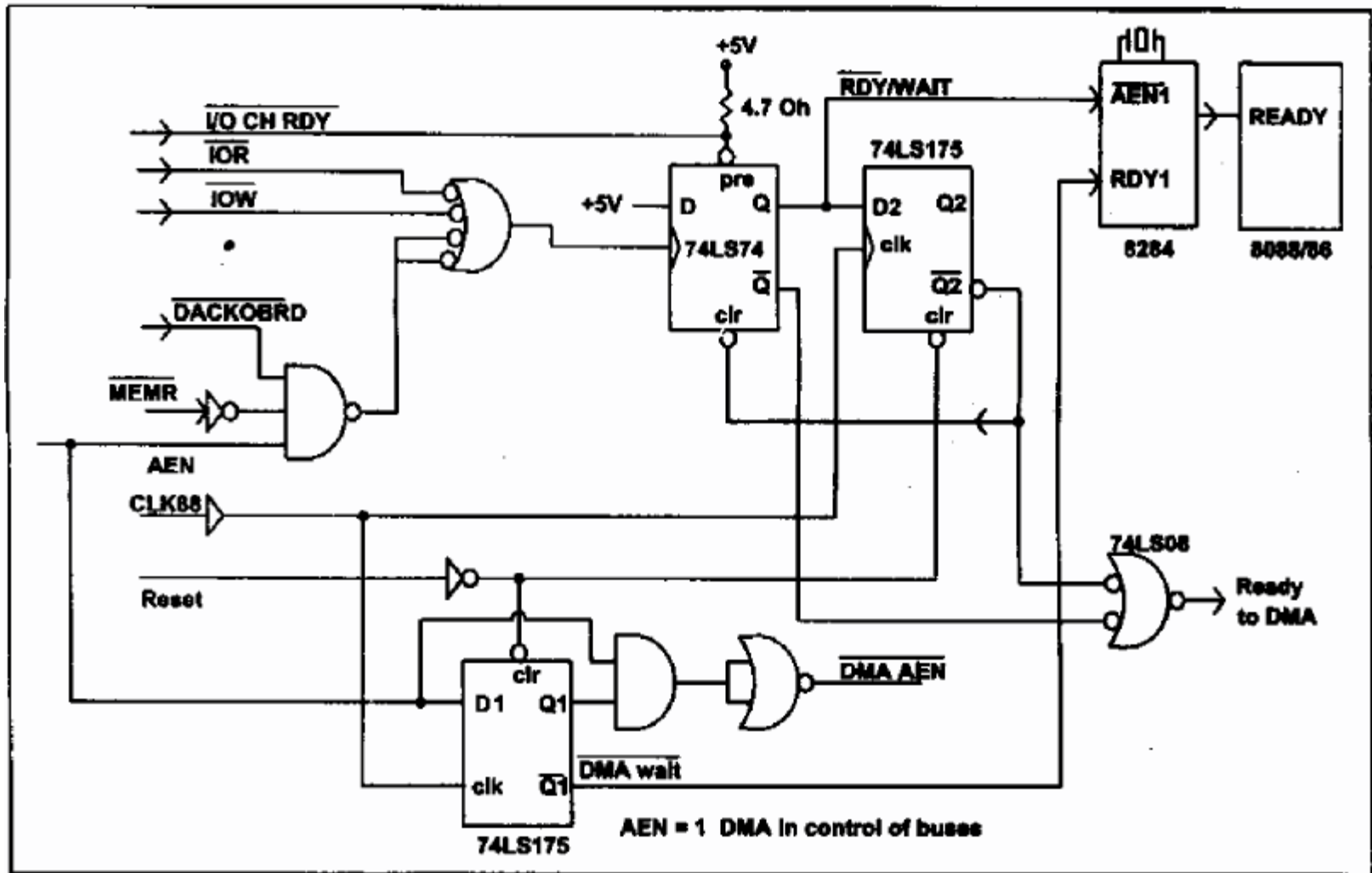


Figure 3-21. Wait-State Generation Circuitry

(Reprinted by permission from "IBM Technical Reference" c. 1984 by International Business Machines Corporation)

DRAM Refresh

- Many strategies
- Logic on chip
- Here a row counter

