

# **Microprocessor System Design Timers**


**Omid Fatemi  
(omid@fatemi.net)**

# Outline

- **Timers / counters / Watchdog timers**
- **8253/4 description**
- **Programming the counters**
- **8253 in a PC**
- **Generating sound**
- **Various modes of operation**
 
# Timers, counters, watchdog timers


- **Timer: measures time intervals**
  - To generate timed output events
    - » e.g., hold traffic light green for 10 s
  - To measure time between events
    - » e.g., measure a car's speed
- **Based on counting clock pulses**
  - » E.g., for a 100 MHz clock, Clk period would be 10 ns
  - » And we count 20,000 Clk pulses
  - » Then 200 microseconds have passed
  - » 16-bit counter would count up to  $2^{16} = 65,535 \times 10 \text{ ns}$   
→ 655.35  $\mu\text{s}$  (range), with a resolution of 10 ns
  - » Top: indicates top count reached, wrap-around
  - » How can we measure a time interval larger than the range?



**cnt:** # of clock pulses since the counter was last reset (set to zero).
 
# Counters



- **Counter:** like a timer, but counts pulses on a *general input signal* rather than clock
  - e.g., count cars passing over a sensor
  - We can often configure device as either a timer or counter
  - Counters and timers can be combined to measure rates, such as the speed of a car (# of times wheel rotates in one second).


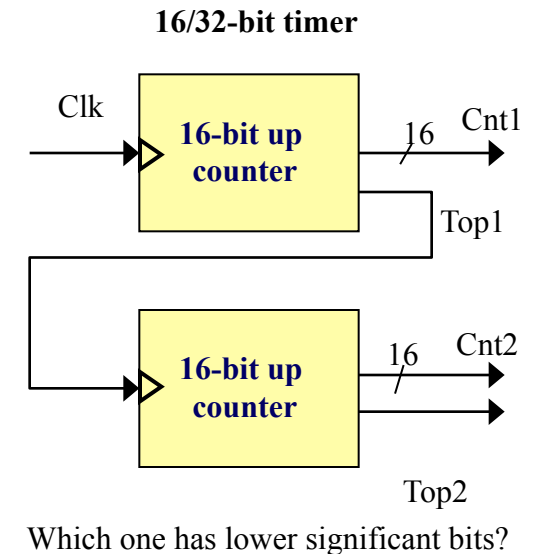 
# Other timer structures

- Interval timer


- Indicates when desired time interval has passed
- We set terminal count to desired interval
  - » **Number of clock cycles = Desired time interval / Clock period**
  - » If  $f_{clock} = 100 \text{ MHz}$ , how many times do we need to count to reach  $3\mu\text{s}$ ?
  - » **Top** both resets the counter, and informs us when the count is up. It is typically connected to an interrupt.
  - » We can also set the count back from terminal count to zero.




- Cascaded counters

- Prescaler

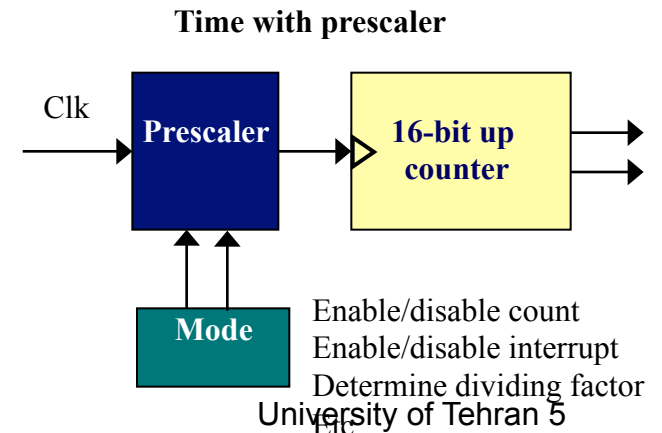- Divides clock
- Increases range, decreases resolution.



# Example: Reaction Timer

 

- **Measure time between turning light on and user pushing button**

- 16-bit timer, clk period is 83.33 ns (12 MHz), counter increments every 6 instruction cycles
- Resolution =  $6 \times 83.33 = 0.5$  microsec (too high).
- Range =  $65535 \times 0.5$  microseconds = 32.77 ms (too low for this application)
- Want program to count 100s of ms, w/o a prescaler, how the extend the range...?
- Initialize timer such that it will overflow in 1 ms, then count the number of overflows!
  - »  $1 \text{ ms} \rightarrow 1 \text{ ms} / (0.5 \mu\text{s}/\text{inst.cycle}) \rightarrow 2000 \text{ inst. cycles}$
  - » so initialize counter to  $65535 - 2000 = 63535$
  - » Counts from 63535  $\rightarrow$  65535 in 1 ms  $\rightarrow$  overflow
  - » What inaccuracy does this solution have?

```
/* pseudocode */

#define MS_INIT    63535
void main(void){
    int count_milliseconds = 0;


    configure timer mode
    set Cnt to MS_INIT

    wait a random amount of time
    turn on indicator light
    start timer

    while (user has not pushed reaction button){
        if(Top) {
            stop timer
            set Cnt to MS_INIT
            start timer
            reset Top
            count_milliseconds++;
        }
    }
    turn light off
    printf("time: %i ms", count_milliseconds);
}
```
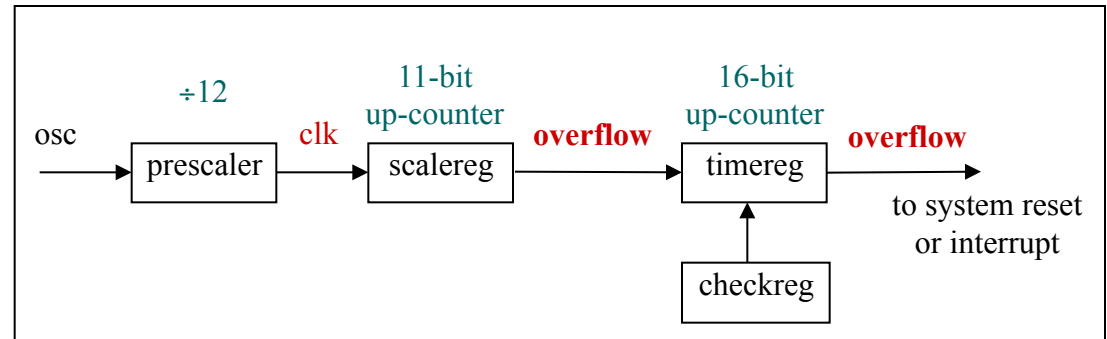
# Watchdog Timer

- Instead of timer generating a signal every X time units, we must reset timer every X time unit, else timer generates a signal (time-out!)
- Under normal operation, we deliberately reset the watch-dog timer every so often.
- Timer out is typically connected to the  $\mu P$  interrupt in. Common use: detect failure, self-reset



```

/* main.c */

main(){
    wait until card inserted
    call watchdog_reset_routine

    while(transaction in progress){
        if(button pressed){
            perform corresponding action
            call watchdog_reset_routine
        }
    }

    /* if watchdog_reset_routine not called every
    < 2 minutes, interrupt_service_routine is
    called */
}
  
```

```

watchdog_reset_routine(){
    /* checkreg is set so we can load value
    into timereg. Zero is loaded into scalereg
    and 11070 is loaded into timereg */

    checkreg = 1
    scalereg = 0
    timereg = 11070
}

void interrupt_service_routine(){
    eject card
    reset screen
}
  
```

→ *timereg* range:  $2 \times (2^{16} - 1) = 131070$  ms

→ *timereg* = 11,070

# 8253/54 Chip



- **Main function:**
  - Dividing clock frequency
- **Three counters**
- **Models**
  - 8253: 2 MHz
  - 8254: 8 MHz
  - 8254-2: 10 MHz




# Addressing 8253

#CS	A1	A0	Port
0	0	0	Counter0
0	0	1	Counter1
0	1	0	Counter2
0	1	1	Control register
1	x	x	Not selected

# Pin Description

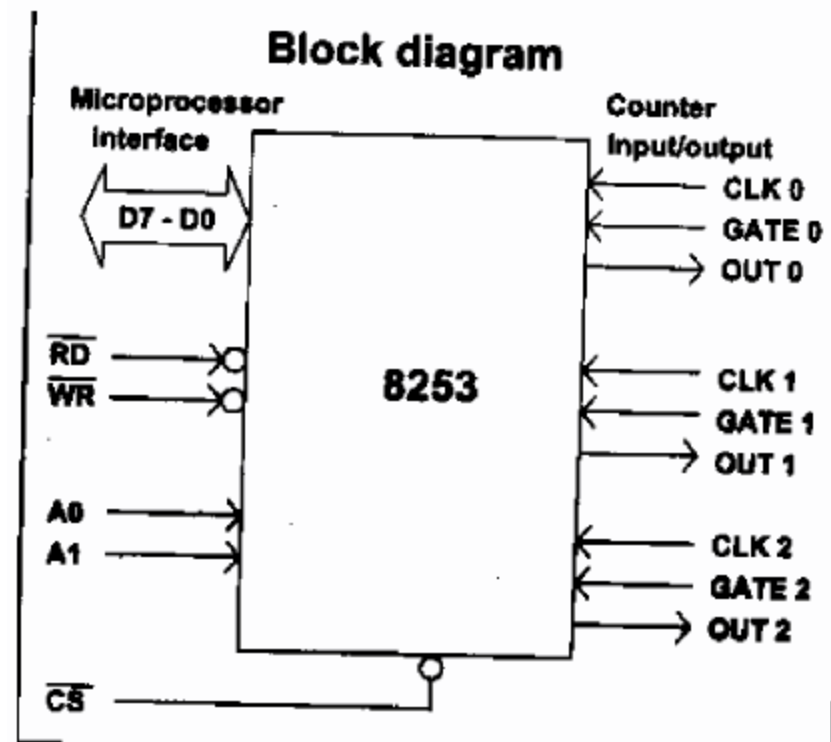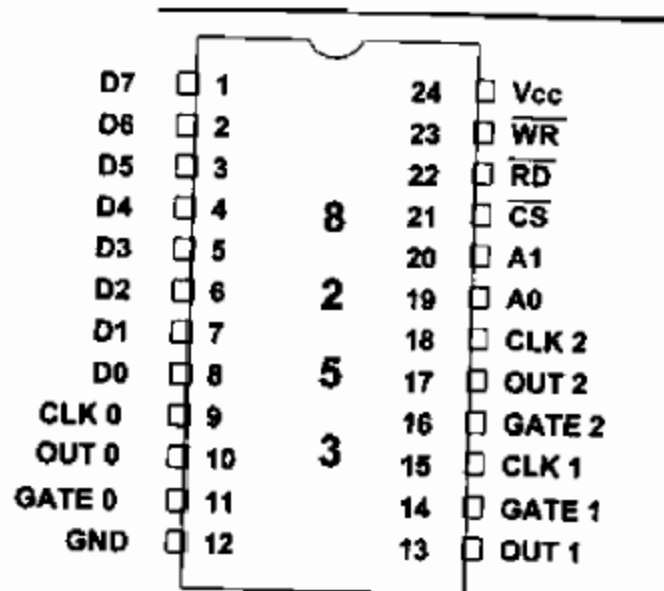

# Control Word

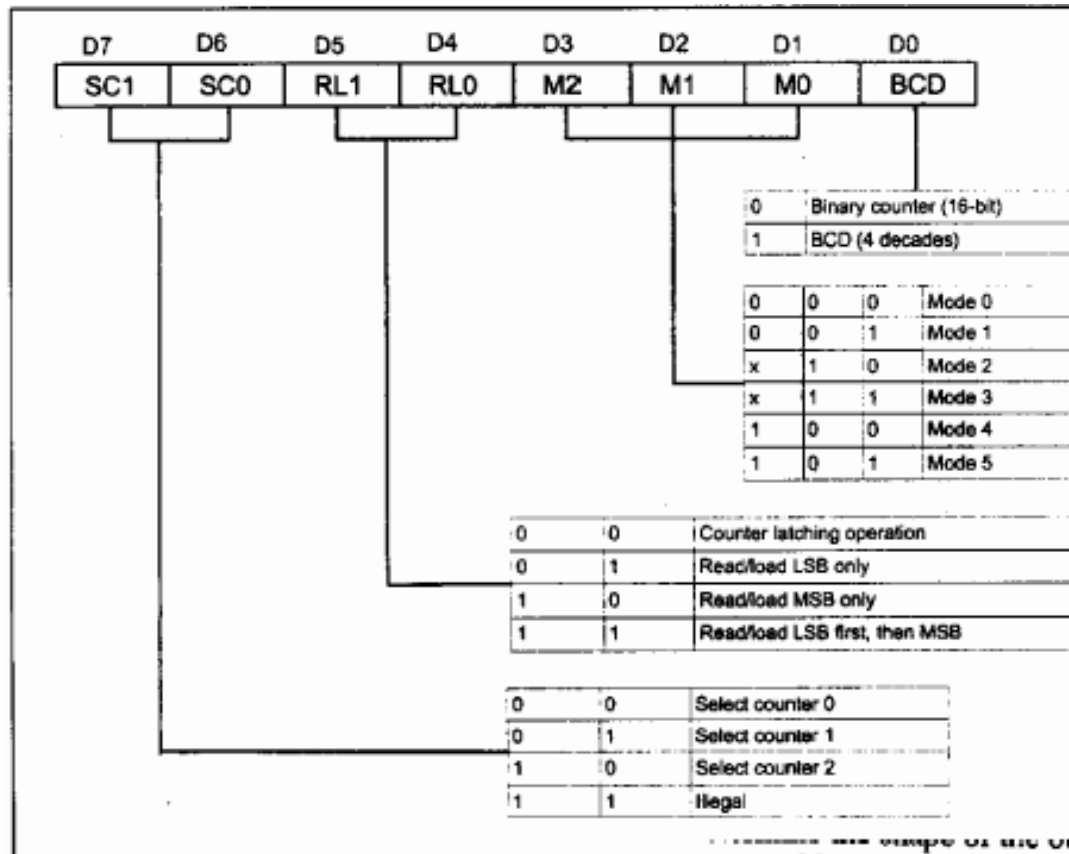

Mode 0 Interrupt on terminal count  
 Mode 1 Programmable one-shot  
 Mode 2 Rate generator  
 Mode 3 Square wave rate generator  
 Mode 4 Software triggered strobe  
 Mode 5 Hardware triggered strobe

# Example

Pin  $\overline{CS}$  of a given 8253/54 is activated by binary address  $A7 - A2 = 100101$ .

(a) Find the port addresses assigned to this 8253/54.

(b) Find the configuration for this 8253/54 if the control register is programmed as follows.

```
MOV  AL,00110110
OUT  97H,AL
```

## Example 5-2

Use the port addresses in Example 5-1 to program:

- (a) counter 0 for binary count of mode 3 (square wave) to divide CLK0 by number 4282 (BCD)
- (b) counter 2 for binary count of mode 3 (square wave) to divide CLK2 by number C26A hex
- (c) Find the frequency of OUT0 and OUT2 in (a) and (b) if CLK0 = 1.2 MHz, CLK2 = 1.8 MHz.

**Solution:**

# 8253 Decoding in PC

Table 5-2: 8253/4 Port Address Calculation in the PC

Binary Address											Hex Address	Function
AEN	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0		
1	0	0	0	1	0	x	x	x	0	0	40	Counter 0
1	0	0	0	1	0	x	x	x	0	1	41	Counter 1
1	0	0	0	1	0	x	x	x	1	0	42	Counter 2
1	0	0	0	1	0	x	x	x	1	1	43	Control register

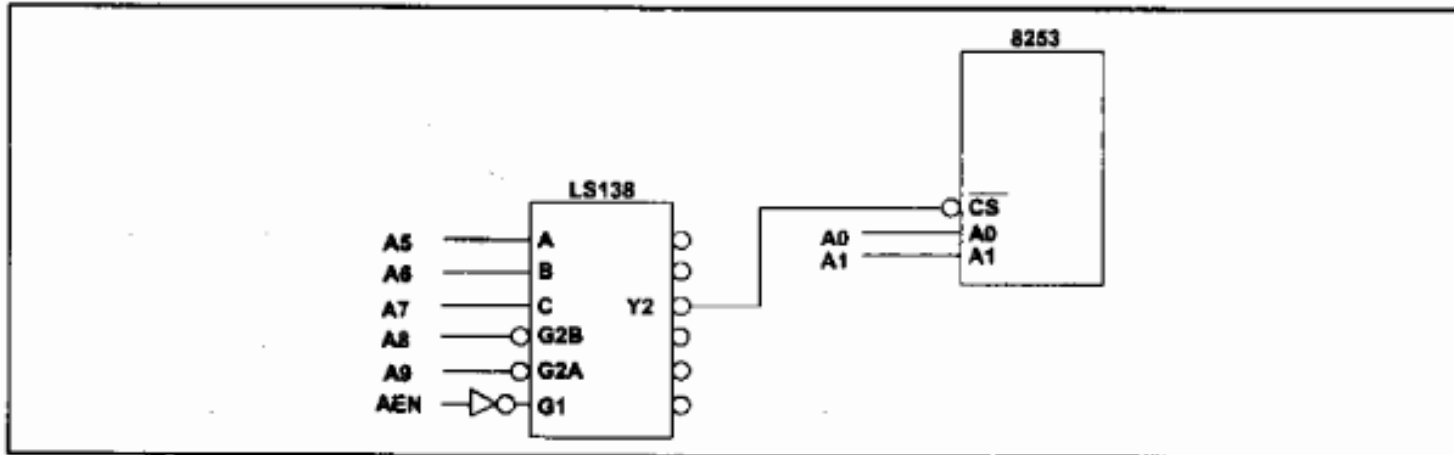


Figure 5-3. 8253 Port Selection in the PC/XT

# PC Board

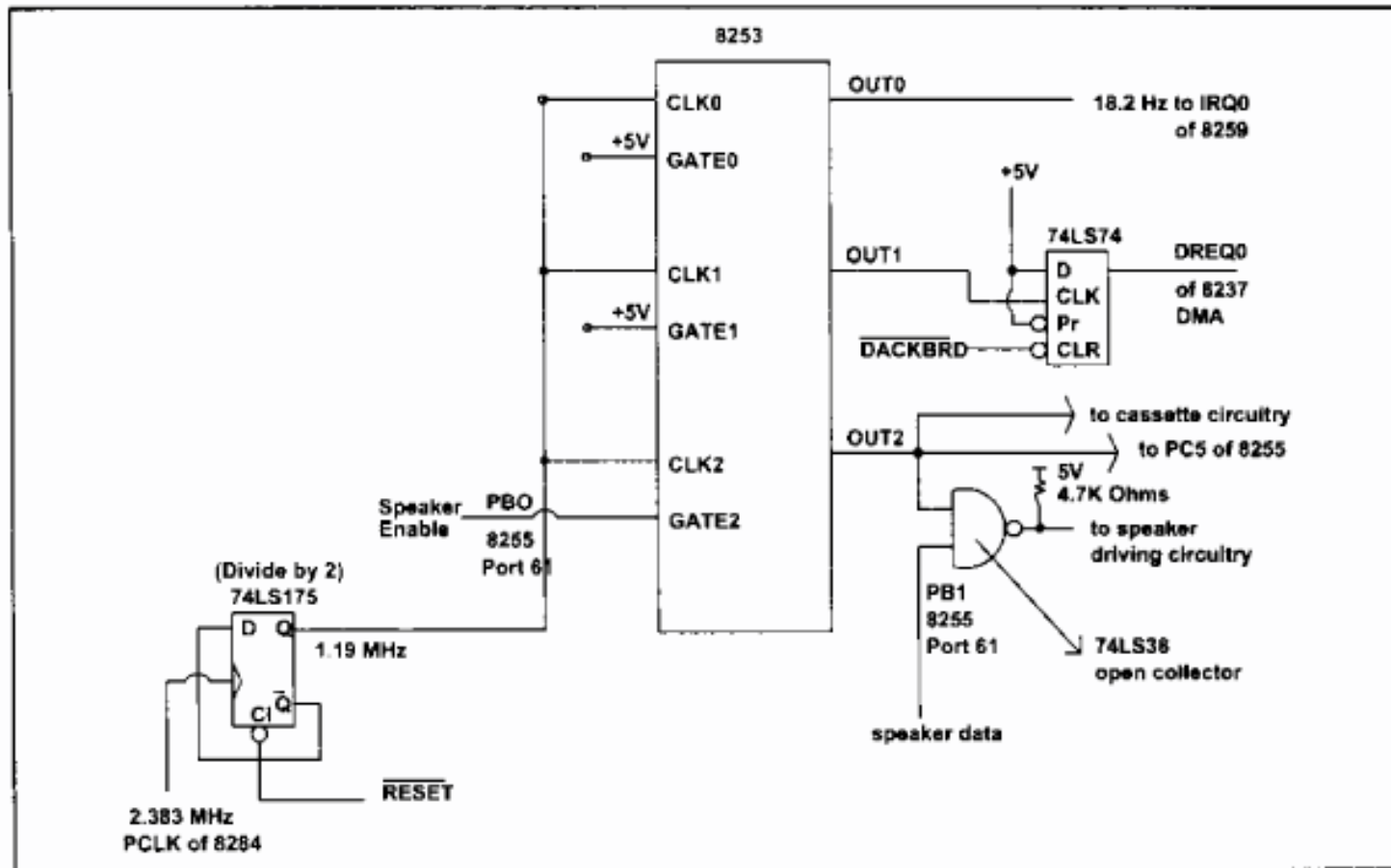


Figure 5-4. 8253 Chip Connections in the PC

# Timers in PC

- **Counter 0**
  - IRQ0 – TOD (time of day)
  - 18.2 Hz (1.193 MHz / 65536)
  - Mode 3, control word: 36H
- **Counter 1**
  - DRAM refresh – using DMA (at least every .015ms)
  - 2 ms / 128 rows = .015 ms (.015ms = 66278Hz → 1.193/18)
  - Mode 2, control word: 54H
- **Counter 2**
  - Speaker and PC5
  - 896 Hz (1.193MHz / 1331)
  - Mode 3, control word: B6H
  - GATE2 is connected to PB0 (port 61H)

Summarizing the above gives the following control word:

D7	D6	D5	D4	D3	D2	D1	D0	
0	0	1	1	0	1	1	0	= 36H

The programming of counter 0 is as follows:

MOV	AL,36H	;control word
OUT	43H,AL	;to control register of 8253
MOV	AL,00	;00 LSB and MSB of the divisor
OUT	40H,AL	;LSB to timer 0
OUT	40H,AL	;MSB to timer 0



# Time Delay in PC

- **Using software**
  - » **MOV CX, N**
  - » **AGAIN: Loop AGAIN (17 clock cycles)**
  - **More than  $N * T(210\text{ns}) * 17$**
  - » **SUB CX,CX**
  - » **G7: Loop G7 (234ms or better 250ms)**
  - » **DEC BL**
  - » **JNZ G7**
- **Hardware**
  - **PB4 of port 61H toggle every 15.085 micro**
  - **Delay.com program**

# Music Using Beep

```

DELAY PROC NEAR
      MOV CX,16578      ;16578 x 15.08 microsec = 250 ms
      PUSH AX
WAIT:
      IN AL,61H
      AND AL,10H        ;check PB4
      CMP AL,AH          ;did it just change?
      JE WAIT           ;wait for change
      MOV AH,AL          ;save the new PB4 status
      LOOP WAIT          ;decrement CX and continue
                        ;until CX becomes 0
      POP AX
      RET
DELAY ENDP

DELAY_OFF PROC NEAR
      MOV CX,331        ;331 x 15.08 micro sec = 5 ms
      PUSH AX
WAIT:
      IN AL,61H
      AND AL,10H        ;check PB4
      CMP AL,AH          ;did it just change?
      JE WAIT           ;wait for change
      MOV AH,AL          ;save the new PB4 status
      LOOP WAIT          ;continue until CX becomes 0
      POP AX
      RET
DELAY_OFF ENDP

```

The following creates a delay for the 8088-based PC/XT of 4.7 Ml

```

DELAY PROC NEAR
      SUB CX,CX
G7:    LOOP G7
      RET
ELAY ENDP

```

# Music Program

D3 note

A3 note

A4 note

```

MOV AL,0B6H           ;control byte:counter2,lsb,msb,binary
OUT 43H,AL            ;send the control byte to control reg
;load the counter2 value for D3 and play it for 250 ms
MOV AX,1FB4H          ;for D3 note
OUT 42H,AL            ;the low byte
MOV AL,AH             ;the high byte
OUT 42H,AL
;turn the speaker on
IN AL,61H             ;get the current setting of port b
MOV AH,AL             ;save it
OR AL,00000011B       ;make pb0 =1 and pb1 =1
OUT 61H,AL            ;turn the speaker on
CALL DELAY            ;play this note for 250 ms
MOV AL,AH             ;get the original setting of port b
OUT 61H,AL            ;turn off the speaker
CALL DELAY_OFF        ;speaker off for this duration
;load the counter2 value for A3 and play it for 500 ms
MOV AX,152FH          ;for A3 note
OUT 42H,AL            ;the low byte
MOV AL,AH             ;the high byte
OUT 42H,AL
;turn the speaker on
IN AL,61H             ;get the current setting of port b
MOV AH,AL             ;save it
OR AL,00000011B       ;make PB0 =1 and PB1 =1
OUT 61H,AL            ;turn the speaker on
CALL DELAY            ;play for 250 ms
CALL DELAY            ;play for another 250 ms
MOV AL,AH             ;get the original setting of port b
OUT 61H,AL            ;turn off the speaker
CALL DELAY_OFF        ;speaker off for this duration
;load the counter2 value for A4 and play it for 500 ms
MOV AX,0A97H          ;for A4 note
OUT 42H,AL            ;the low byte
MOV AL,AH             ;the high byte
OUT 42H,AL
;turn the speaker on
IN AL,61H             ;get the current setting of port b
MOV AH,AL             ;save it
OR AL,00000011B       ;make PB0 =1 and PB1 =1
OUT 61H,AL            ;turn the speaker on
CALL DELAY            ;play for 250 ms
MOV AL,AH             ;get the original setting of port b
OUT 61H,AL            ;turn off the speaker

```

# Output Shapes in PC

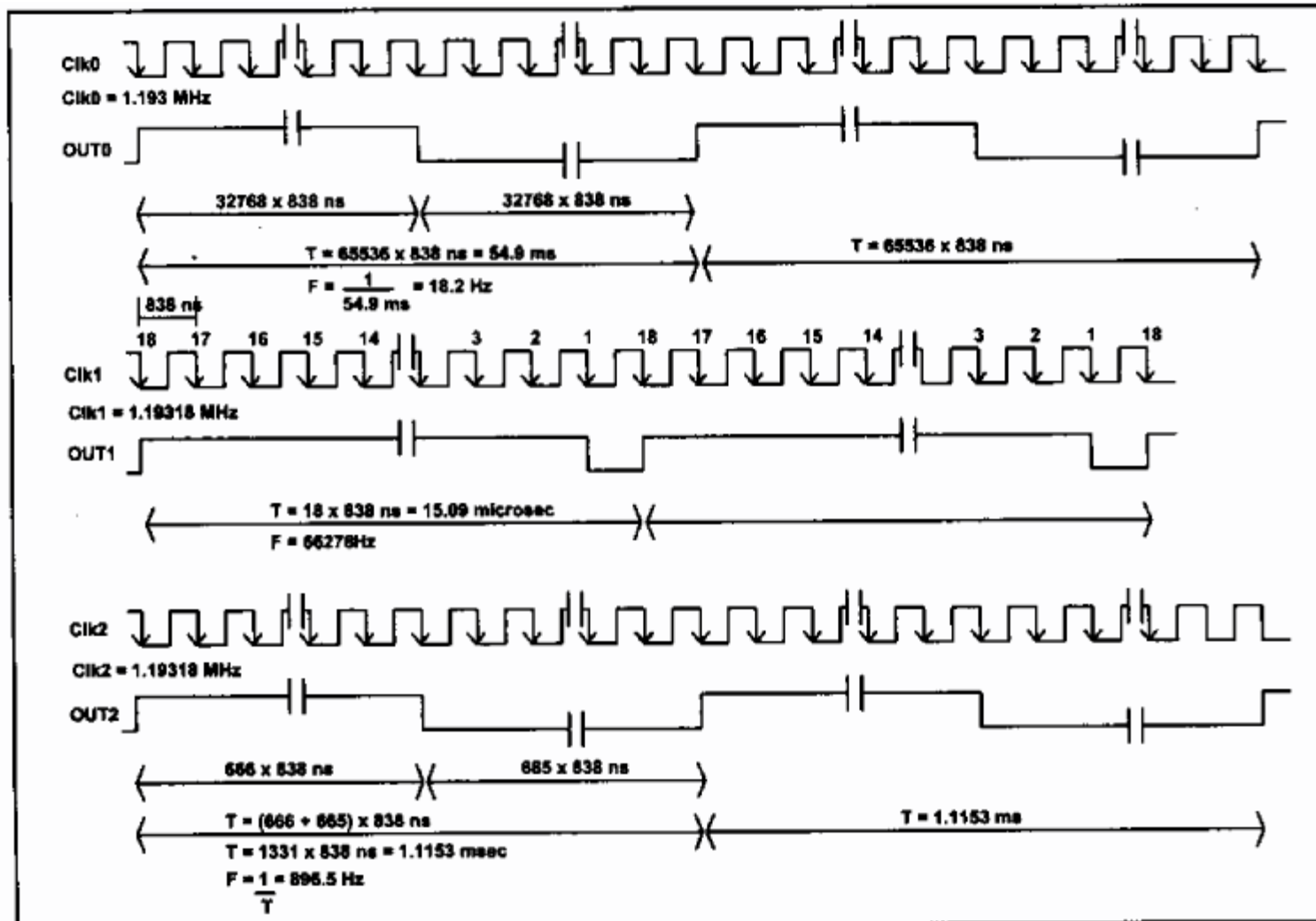


Figure 5-6. 8253/54 Out Timing Diagrams in the PC

# Mode 0


- Interrupt on terminal count
- Low for  $N \cdot T$  then high (Remain high until new control word or count number)

## Example 5-8

In Example 5-7, assume that GATE1 becomes zero for  $400 \mu\text{s}$ . What is the width of the low pulse for OUT1?
 
### Solution:


It is  $1000 \mu\text{s} + 400 \mu\text{s} = 1400 \mu\text{s}$ , as shown next.



□
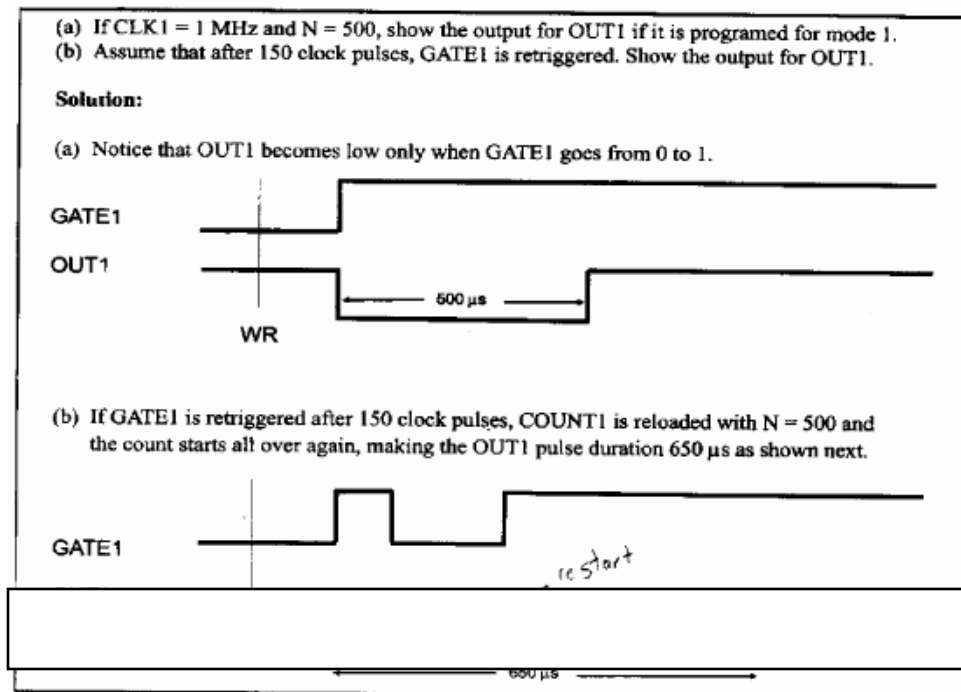
# Programmable One Shot (mode 1)

- Programmable one-shot (hardware triggerable one shot)
- 0 to 1 on GATE (low for  $N \cdot T$ )



□


# Rate Generator (mode 2)

- Rate generator (divide by N counter)
- High for  $N \cdot T$  and low for  $1 \cdot T$
- As long as GATE

If  $\text{CLK2} = 1 \text{ MHz}$ ,  $\text{GATE2} = 1$ , and  $N = 750$ , show  $\text{OUT2}$  if  $\text{COUNT2}$  is programmed for mode 2.

 **Solution:**

Notice that the count is reloaded automatically and the counter continues to produce  $\text{OUT2}$ .



# Square Wave (Mode 3)


- Square wave rate generator
- Low  $N/2$  high  $N/2$  ( $(N+1)/2$  if  $N$  odd)

If  $CLK2 = 1\text{ MHz}$ ,  $GATE1 = 1$ ,  $N = 1000$ , show  $OUT1$  if  $COUNT1$  is programmed for mode 3.

**Solution:**

Since the clock period is  $1\text{ }\mu\text{s}$ ,  $OUT1$  is high for  $500\text{ }\mu\text{s}$  and low for  $500\text{ }\mu\text{s}$ , producing the square wave of  $1\text{ ms}$  period continuously, as shown next.

$GATE1 = 1$

 



# Mode 4

- Software triggered strobe
- Starts upon loading the count
- High for  $N \cdot T$  low for 1 and then high

---

If  $\text{CLK0} = 1 \text{ MHz}$ ,  $\text{GATE0} = 1$ , and  $N = 600$ , show the shape of  $\text{OUT0}$  where counter 0 is programmed for mode 4.

**Solution:**

Since the  $\text{CLK0}$  period is  $1 \mu\text{s}$ , after the count is loaded  $\text{OUT0}$  will be high for  $600 \mu\text{s}$  and will go low for  $1 \mu\text{s}$ . Then it will go high again and stay high until the counter is reprogrammed, as shown below.




# Mode 5

- Hardware triggered strobe
- 0 to 1 pulse on GATE

In Example 5-13, assume that GATE1 is retriggered after 150 pulses. Show the output for OUT1.

 **Solution:**

If GATE1 is retriggered after 150 clock pulses into the countdown, COUNT1 is reloaded with  $N = 400$  and the counts begins again, making the OUT1 pulse duration  $550 \mu s$ , as shown next.



# Exercises from Book

- **Text book, Vol. 2 (Page 189-191)**
- **Problems 3, 8, 18, 20, 29**