


CE233(CAD), Lecture 2:

# Introduction to PLDs

Mehdi Modarressi


Department of Electrical and Computer Engineering,  
University of Tehran

# World of integrated circuits

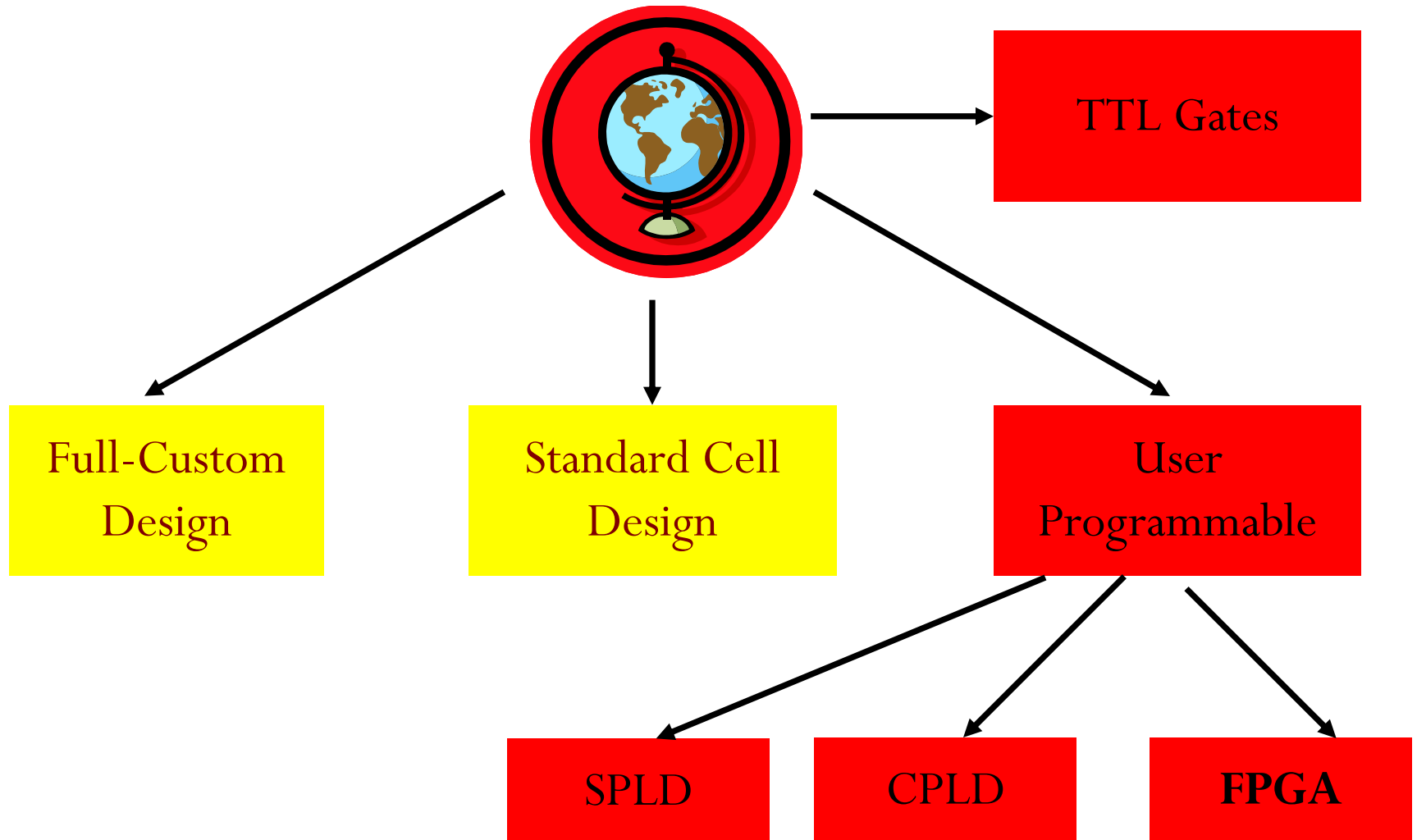

 
# Full-custom ICs

- General-purpose processors
  - Example: Intel and AMD microprocessors
- Application-specific processors
  - Example: Embedded processor of a digital camera
- Requires establishing a fabrication line
  - You will learn more about this in the VLSI Design course


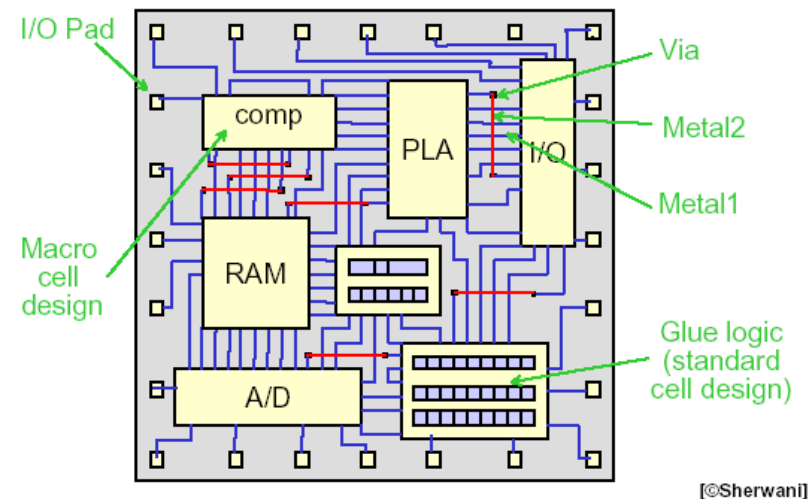
# Full-custom design

- Very efficient in terms of performance, but:
  - Long design and manufacturing cycles
  - Very expensive, sometimes several million dollars
  - Once manufactured, the logic can't simply be altered
    - large penalty if a bug is found





# Full-custom design

- Requires establishing a fabrication (production) line
- Suitable for large volume production
- Example: General-purpose processors
  - Intel and AMD microprocessors

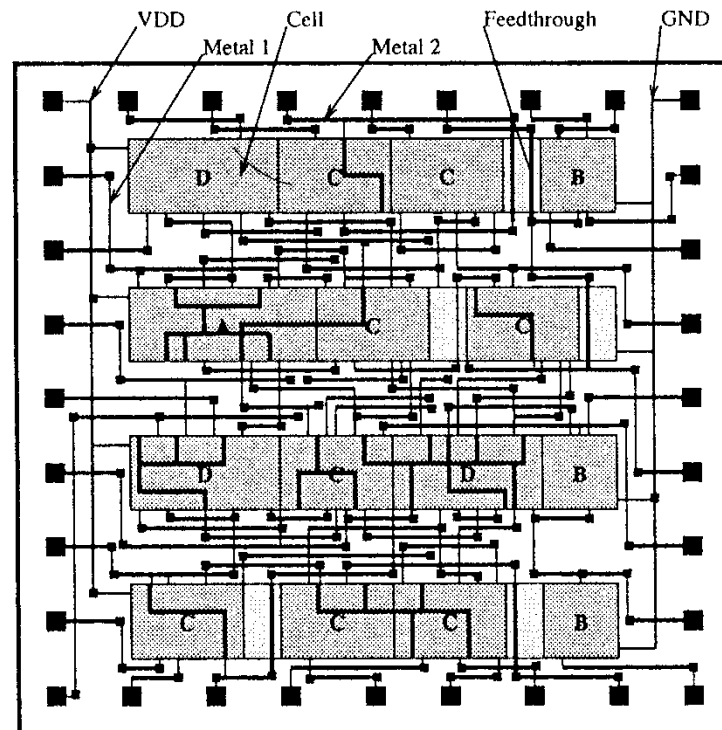 
# Standard-cell design

- Still needs fabrication line, but the logic are selected from a library



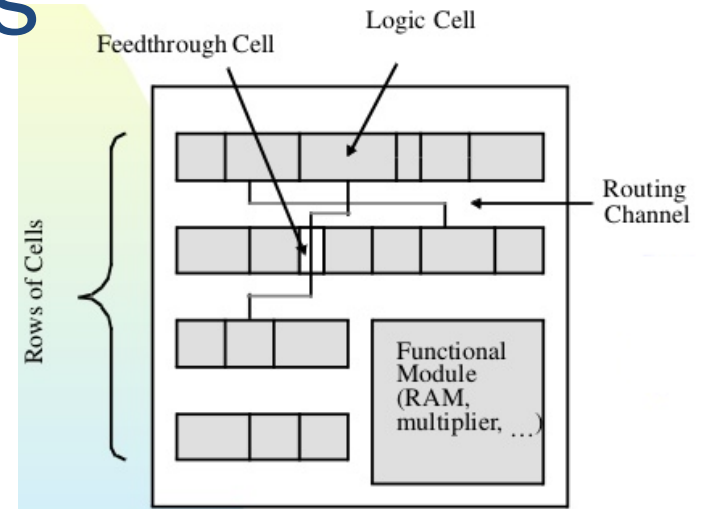
# Semi-custom designs


- Designers use standard libraries and pre-defined chip layouts to ease implementation
  - To reduce design time/effort



Full custom

 


Standard cell

 
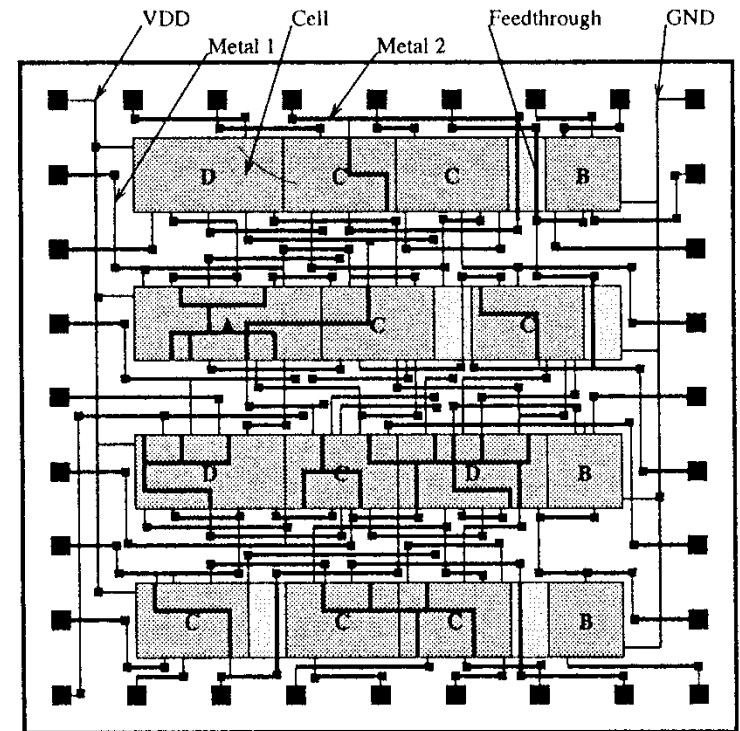
# Standard-cell design


- Cell library
- Cell: a transistor level implementation of a function (e.g. mux, register, adder,...) in a rectangular shape of the same height
- Cells placed in rows and space between rows are used for routing








 
# VLSI design process


- System specification
  - Functional design
  - Logic design
  - Circuit design
  - Physical design
  - Fabrication and packaging
- Test or verification after each step


    
$$x = (AB*CD)+(A+D)+(A(B+C))$$
$$Y=(A(B+C)+AC+D+A(BC+D))$$



# Physical design in ASICs

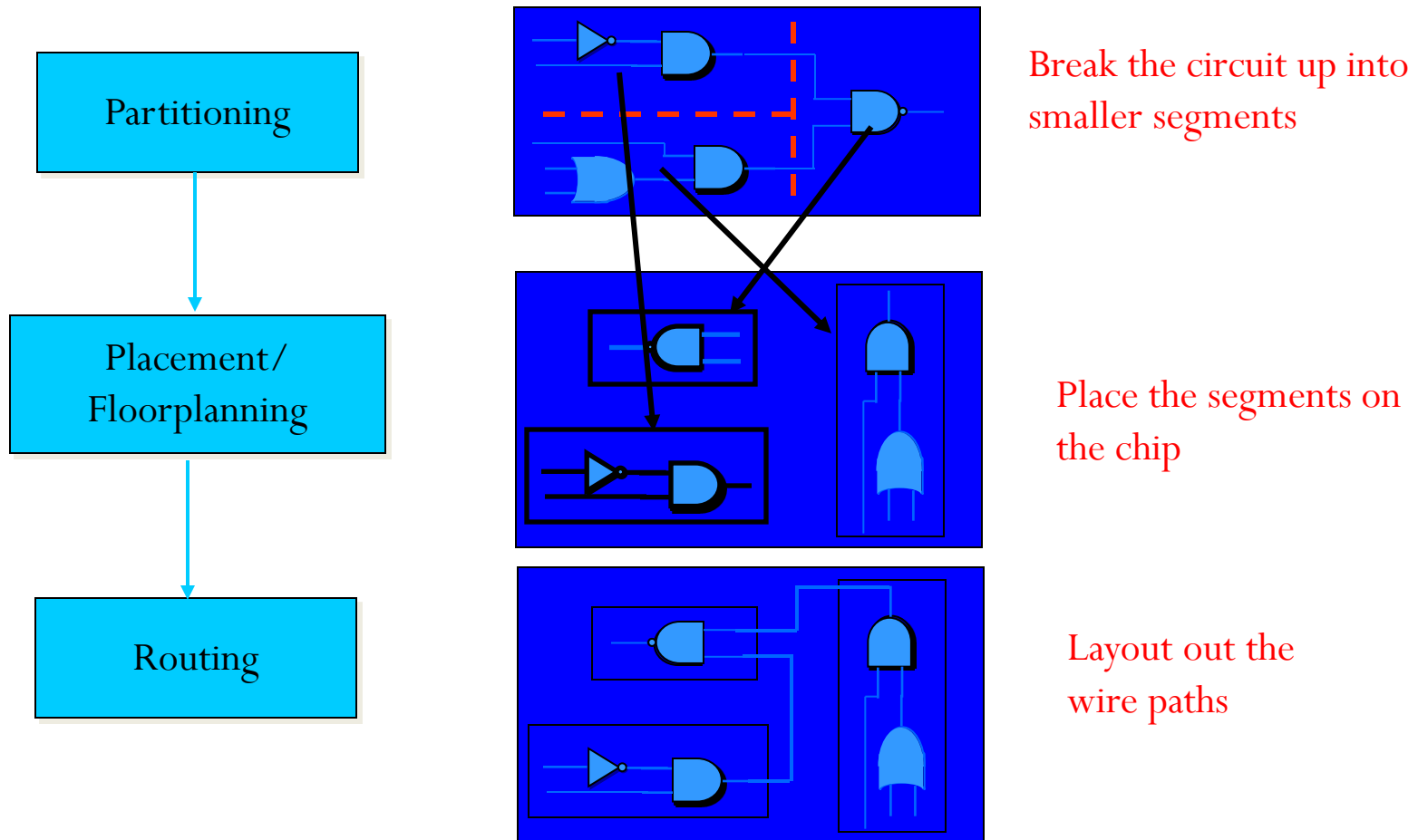

# IC fabrication process

- Silicon fabrication lab




AMD's 65 nm fabrication lab (control and clean room)


Find an interesting video at:

<http://www.bloomberg.com/news/articles/2016-06-09/how-intel-makes-a-chip>


# VLSI process for full custom ICs

 

# VLSI process for full custom ICs

 


# VLSI process for full custom ICs

 




# VLSI process for full custom ICs

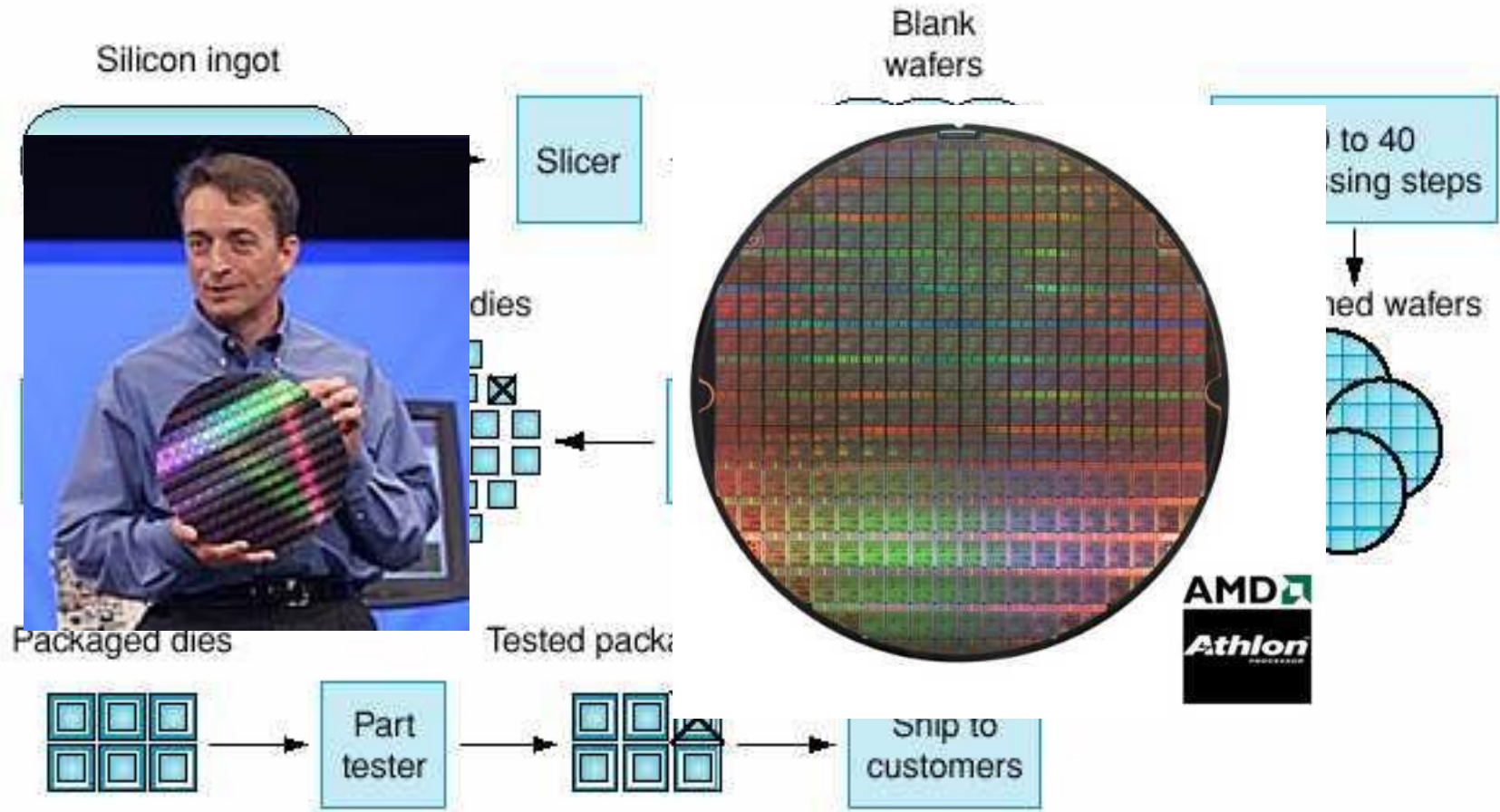


# VLSI process for full custom ICs

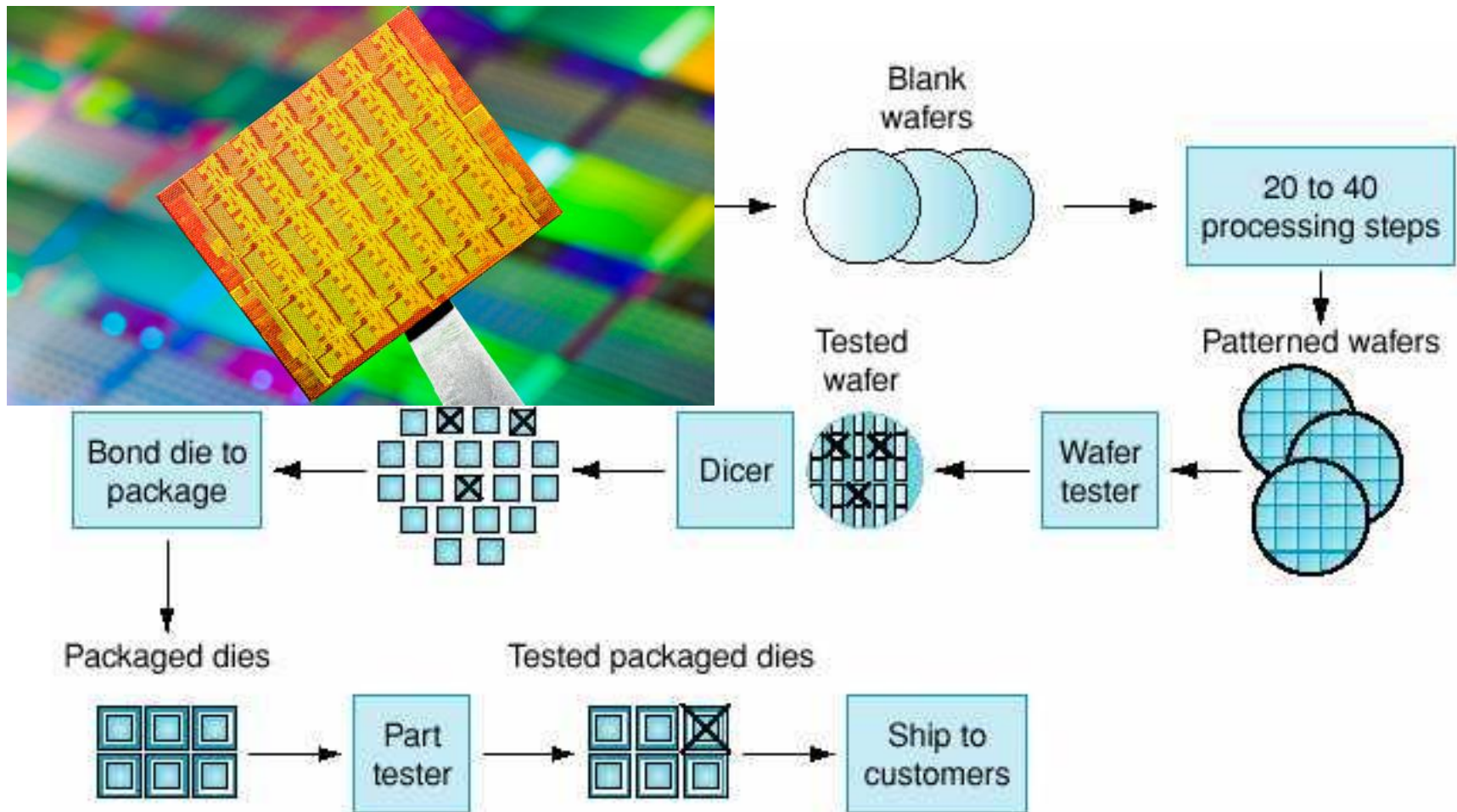





# VLSI process for full custom ICs

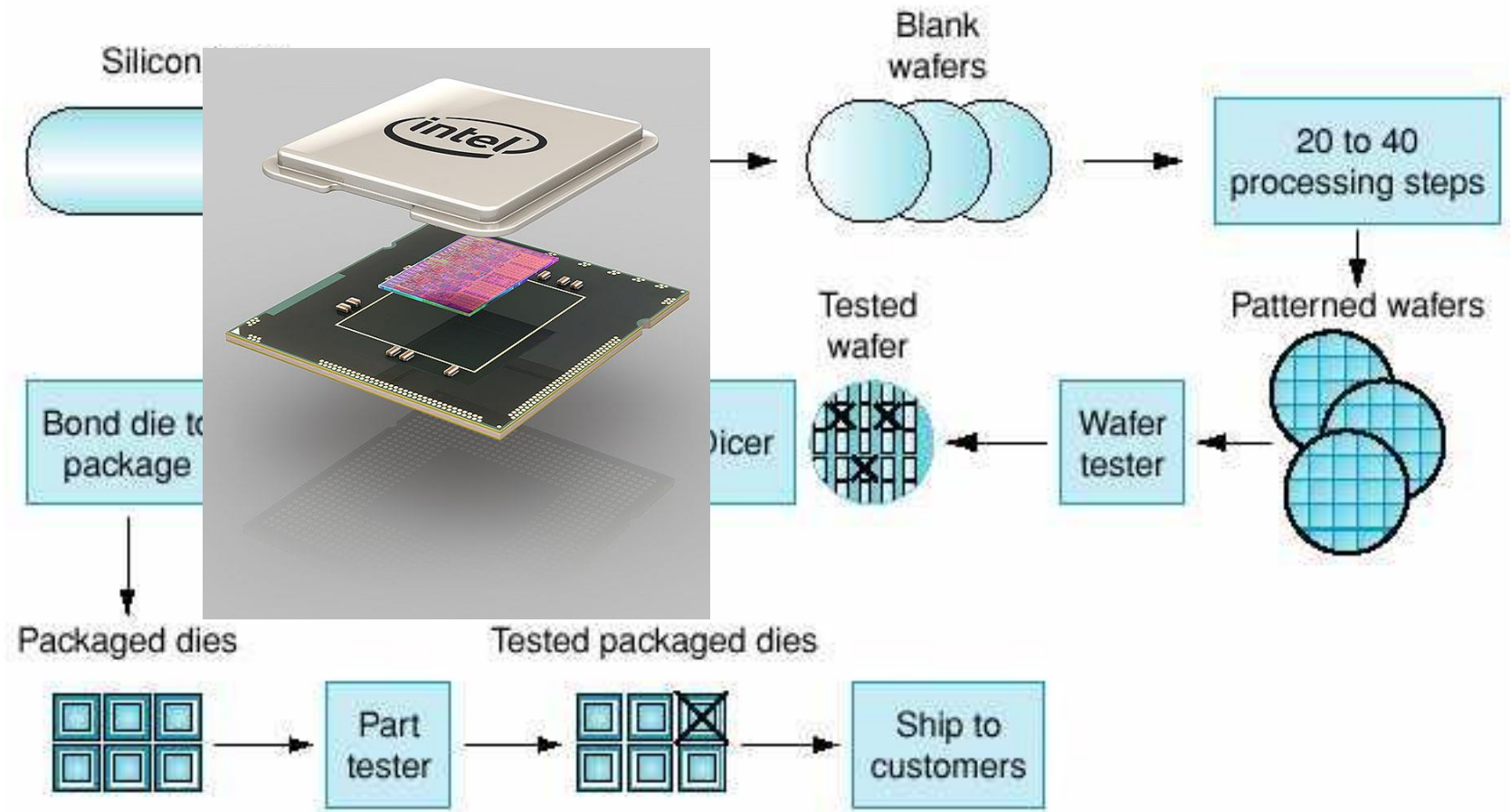
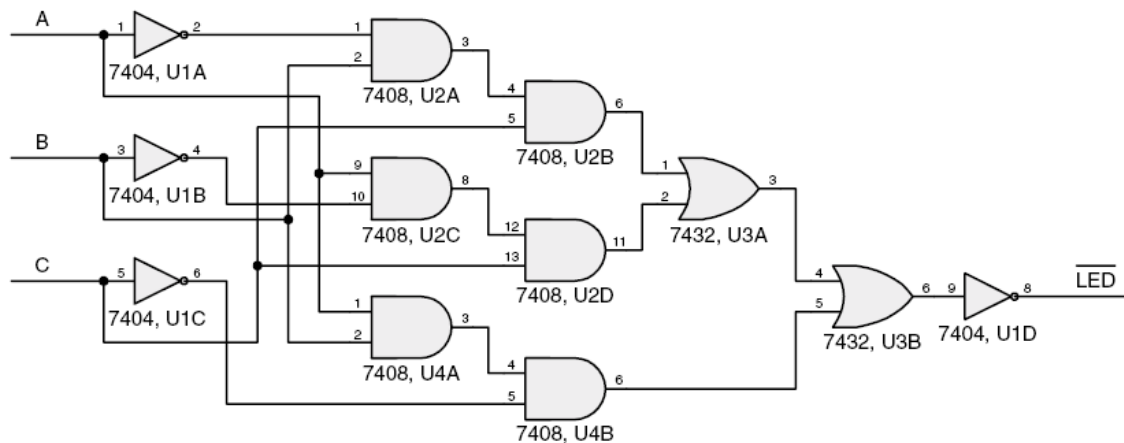 
# TTL gates

- For very simple hardware only
- 74 series
  - 7404: hex NOT
  - 7408: quad 2-input AND
  - 74374: Flip-flop
  - 74193: 4-bit counter




# Programmable logic devices

- Some degrees of reconfigurability in ICs
- Fabricate gates, memories, interconnects into a single chip
- Let the final user to implement logic functions by appropriately connecting these devices
- PLD chips are themselves constructed by a standard cell or full-custom method
  - But final function implementation is done by the end user
- Programmable Logic Devices (PLD) are the most common target for HDL codes
  - In comparison to standard cell and full-custom chips
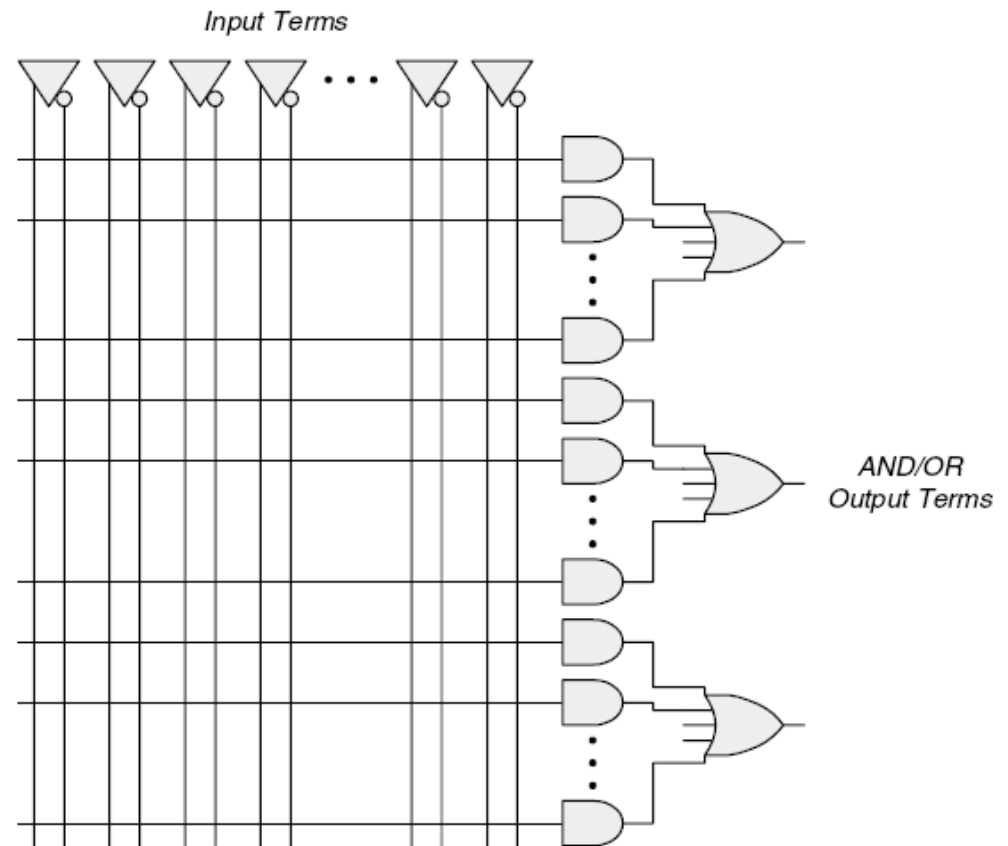
# Programmable devices

- You know simple PLDs from the Logic Design course
- *We will review them again shortly*
- Example: PAL
  - Very simple programmable IC
  - The base of more complex programmable ICs




# Advantages of PLDs

- Field Programmable
  - Reduced TTM and design cost
  - Accessible everywhere: easy-to-implement functions
- Erasable and reprogrammable
  - Updating a device or correction of errors
    - By a simple patch
  - Used for full-custom prototyping


# Programmable logic technologies

- Simple Programmable Logic Device (SPLD)
  - Read Only Memory (ROM)
  - Programmable Array Logic (PAL)
  - Programmable Logic Array (PLA)
- Complex Programmable Logic Device (CPLD)
- Field- Programmable Gate Array (FPGA)


# ROM, PAL and PLA

 

PROM

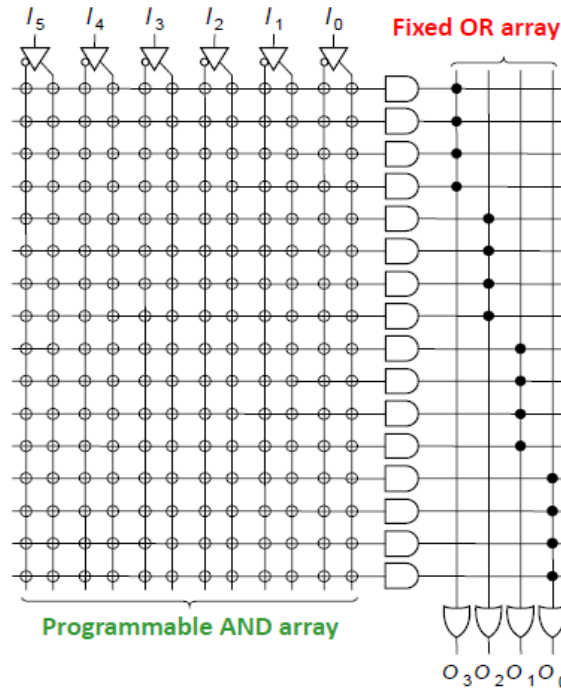


PAL

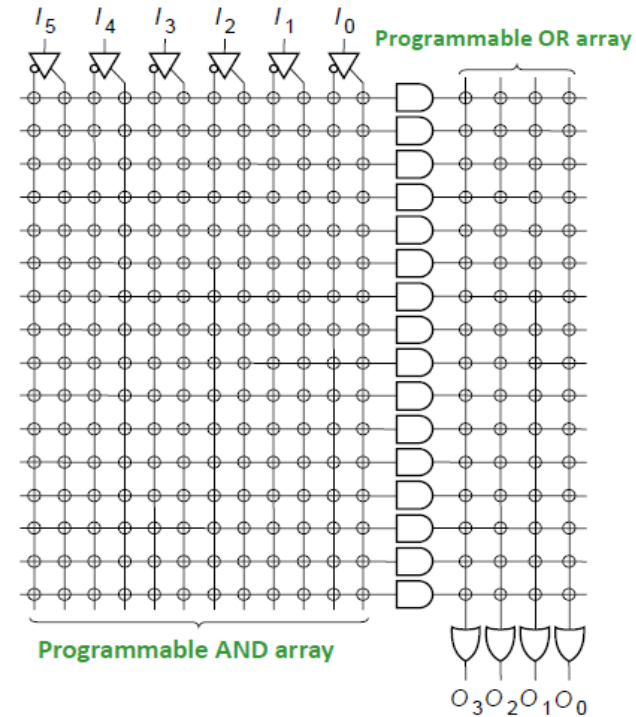


PLA


# ROM, PAL and PLA configurations

 

(a) Programmable read-only memory (PROM)

 

 
(b) Programmable array logic (PAL) device




(c) Programmable logic array (PLA) device




# ROM

 


# PAL

 


# PLA

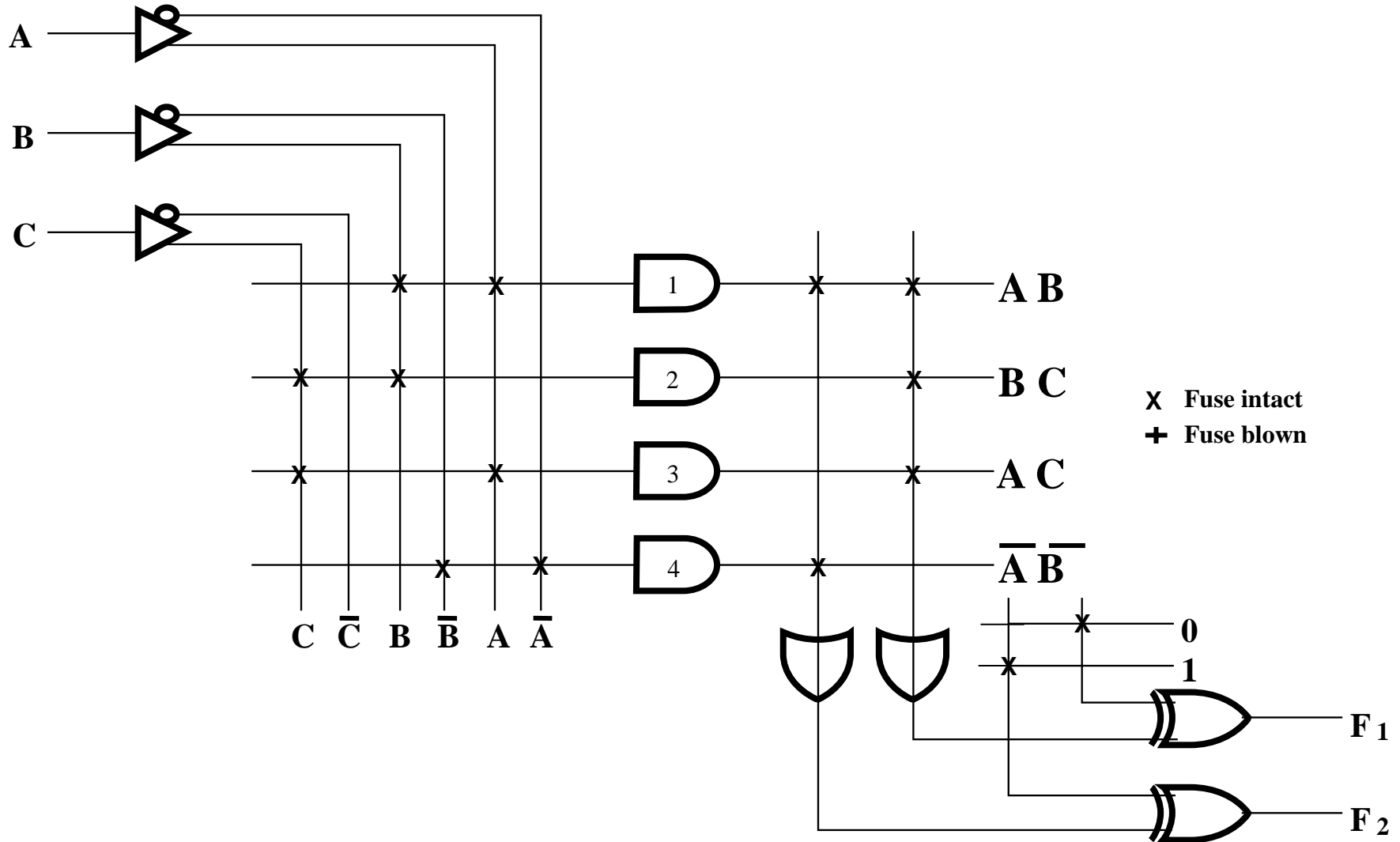

# Technology trade-offs

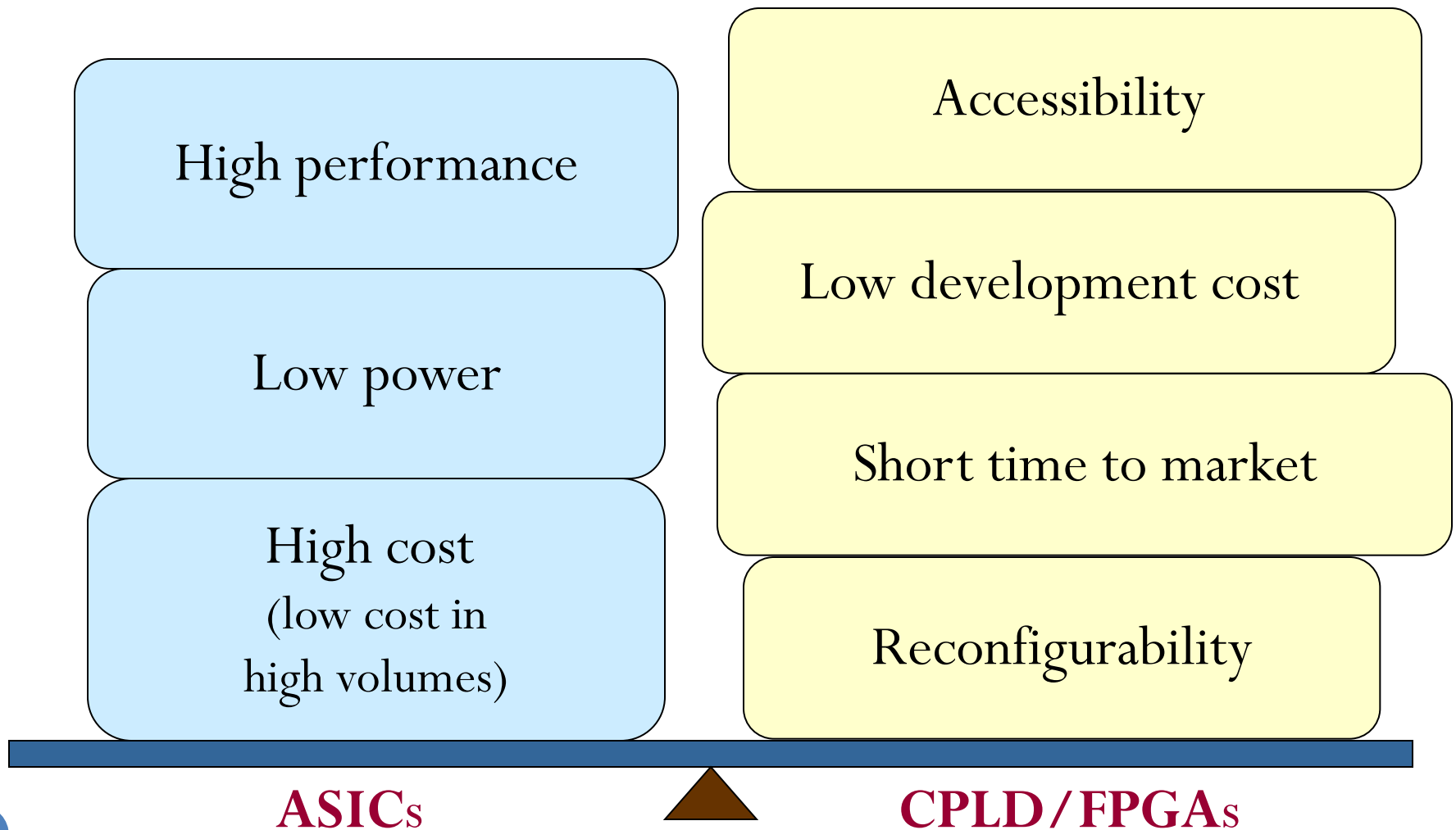

# Full adder

 


**PLA**

56 PS

182 PJ

Latency=

Energy=

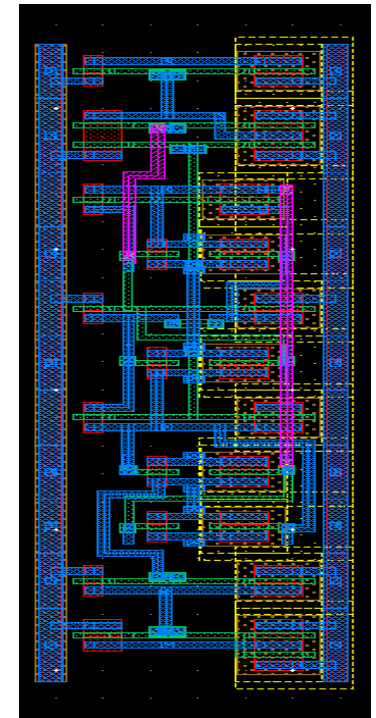

**ASIC**

3.7 PS

47PJ

# PLD architectures

- PAL and PLA are simple devices and called SPLD (simple PLD)
- Two types complex programmable devices:

## CPLDs


- Often composed of some large blocks
  - Each block is a PAL plus some storage elements
- Connection among blocks by a central interconnection part

## FPGAs

- Often composed of tens to hundreds of smaller logic blocks
  - Each block has a few lookup tables plus some storage elements
- The blocks are surrounded by a sea of interconnects

 
# CPLD

- Each block is like a large PAL with some memory elements



# CPLD example

Altera® MAX 5000

 





# Altera® MAX 5000

- Each LAB contains 16-32 Macrocells

## Logic Array Block (LAB)

 


## Global Interconnect (PIA)

 



# Altera® MAX 5000

- Each Macrocell is a PAL: calculates a SoP (sum of products)
- A 3-input OR, each input comes from a programmable AND

Logic Array Block  
(LAB)

 


Global Interconnect  
(GIA)

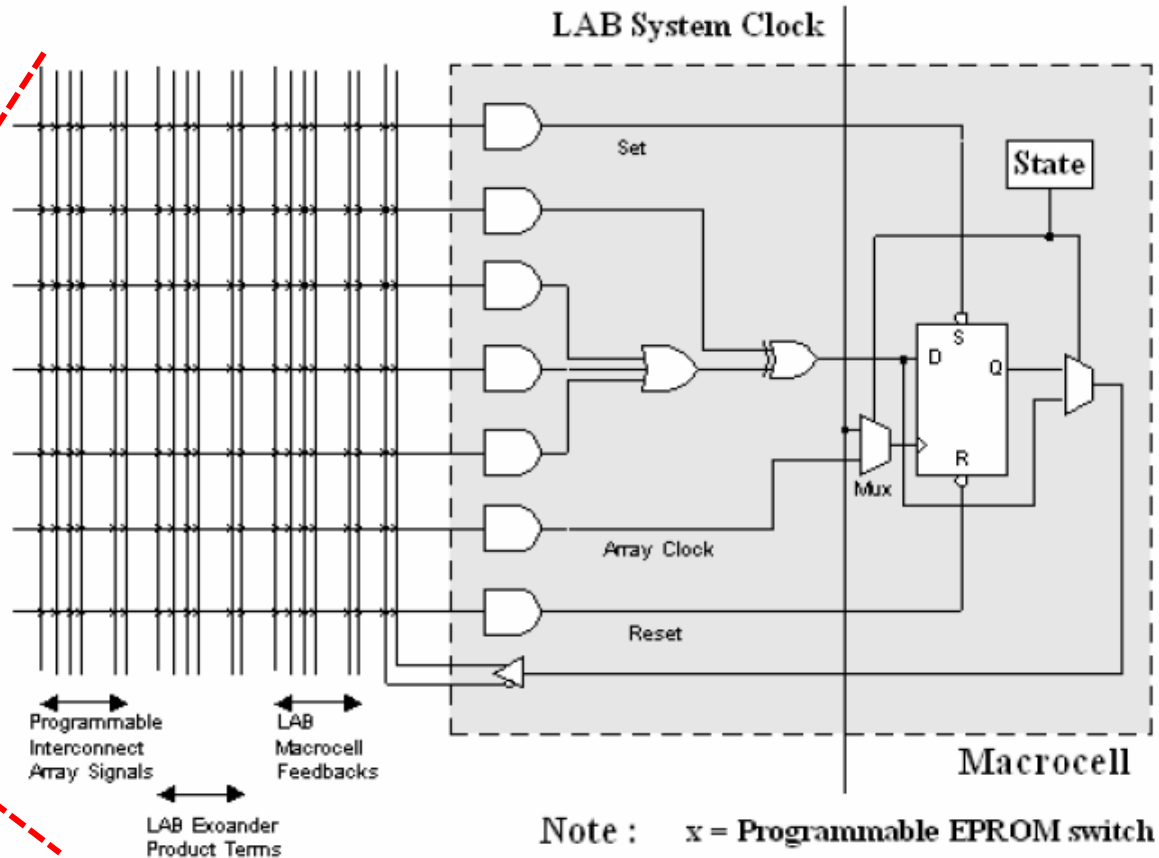 
 
# FPGA


- An array of logic cells in a sea of interconnects



# FPGA - generic structure

 
## FPGA building blocks:

- Programmable logic blocks  
Implement combinatorial and sequential logic
- Programmable interconnect  
Wires to connect inputs and outputs to logic blocks
- Programmable I/O blocks  
Special logic blocks at the periphery of device for external connections



# FPGA

- FPGA: Filed Programmable Gate Array

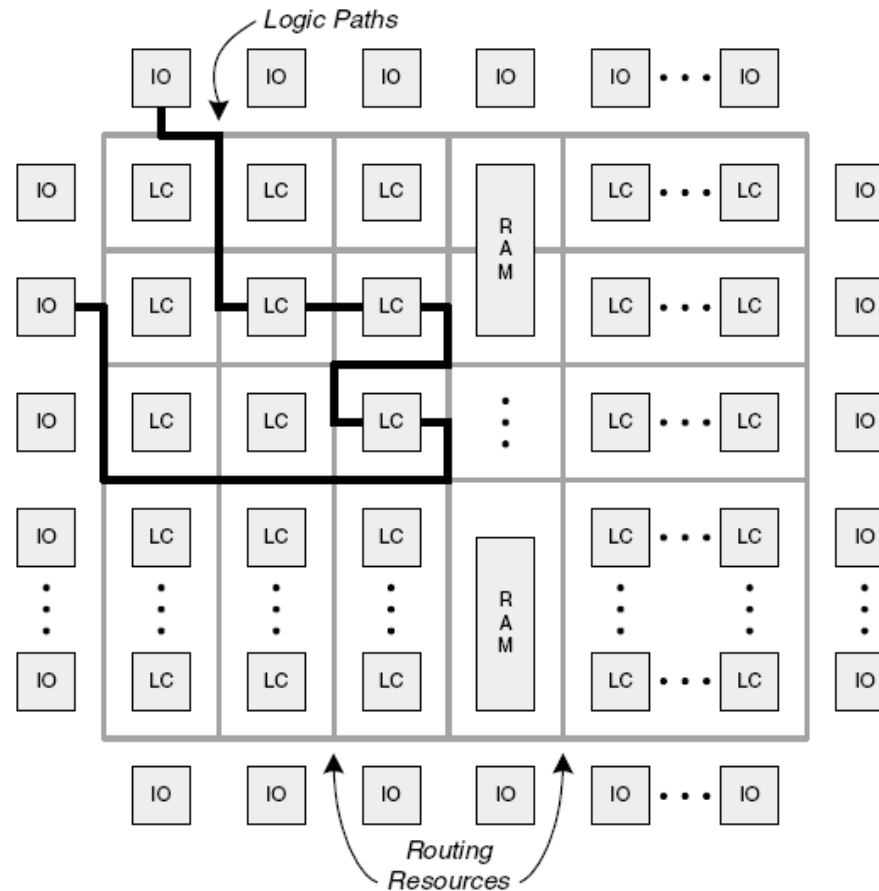


LC= logic cell, can be a PAL


# Digital design flow for FPGAs

- Design entry
- Logic synthesis
- Partitioning
- Placement
- Routing
- Pin assignment


Physical Design

 

# Digital design flow for FPGAs

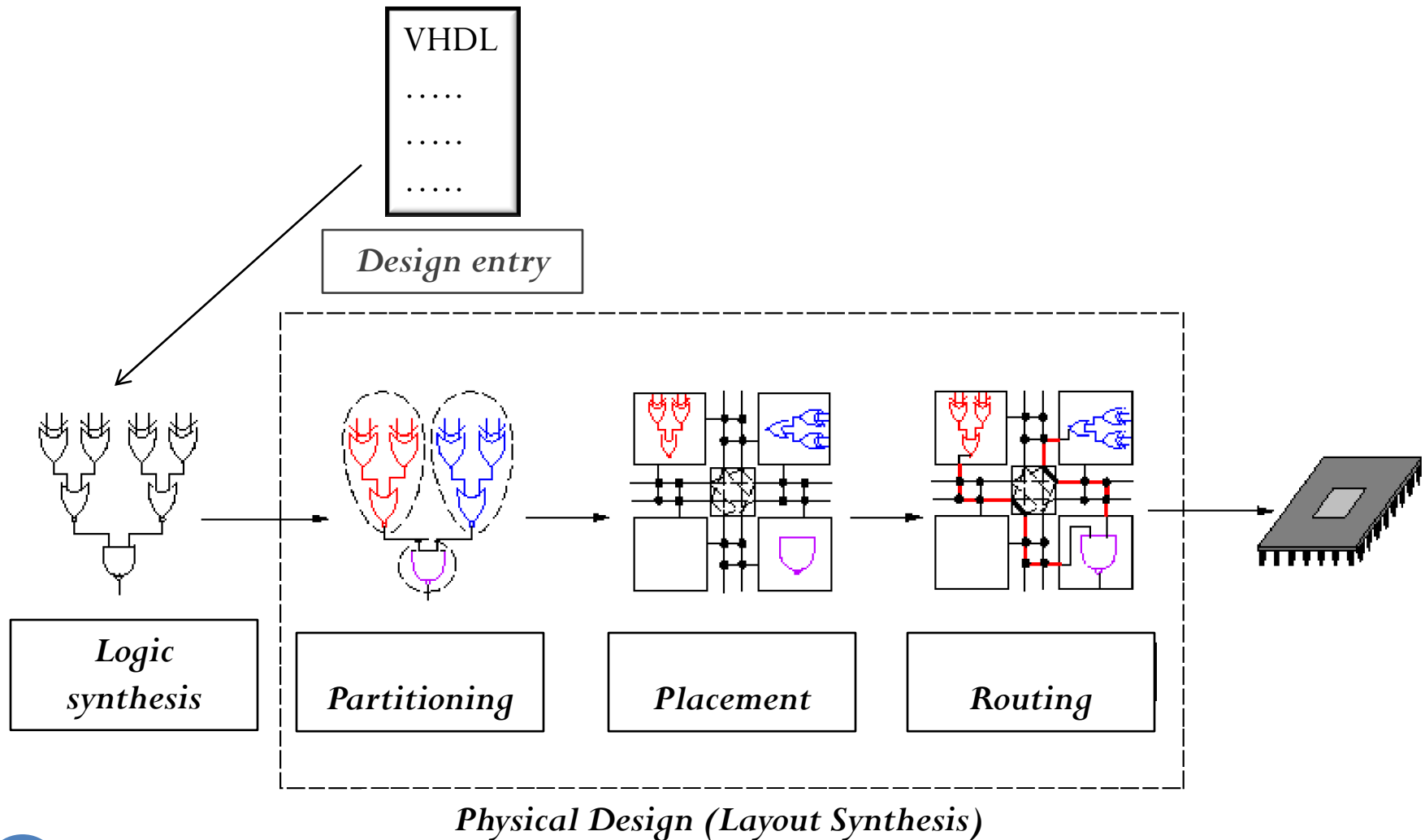


# FPGA physical design

 




# Programmable routing

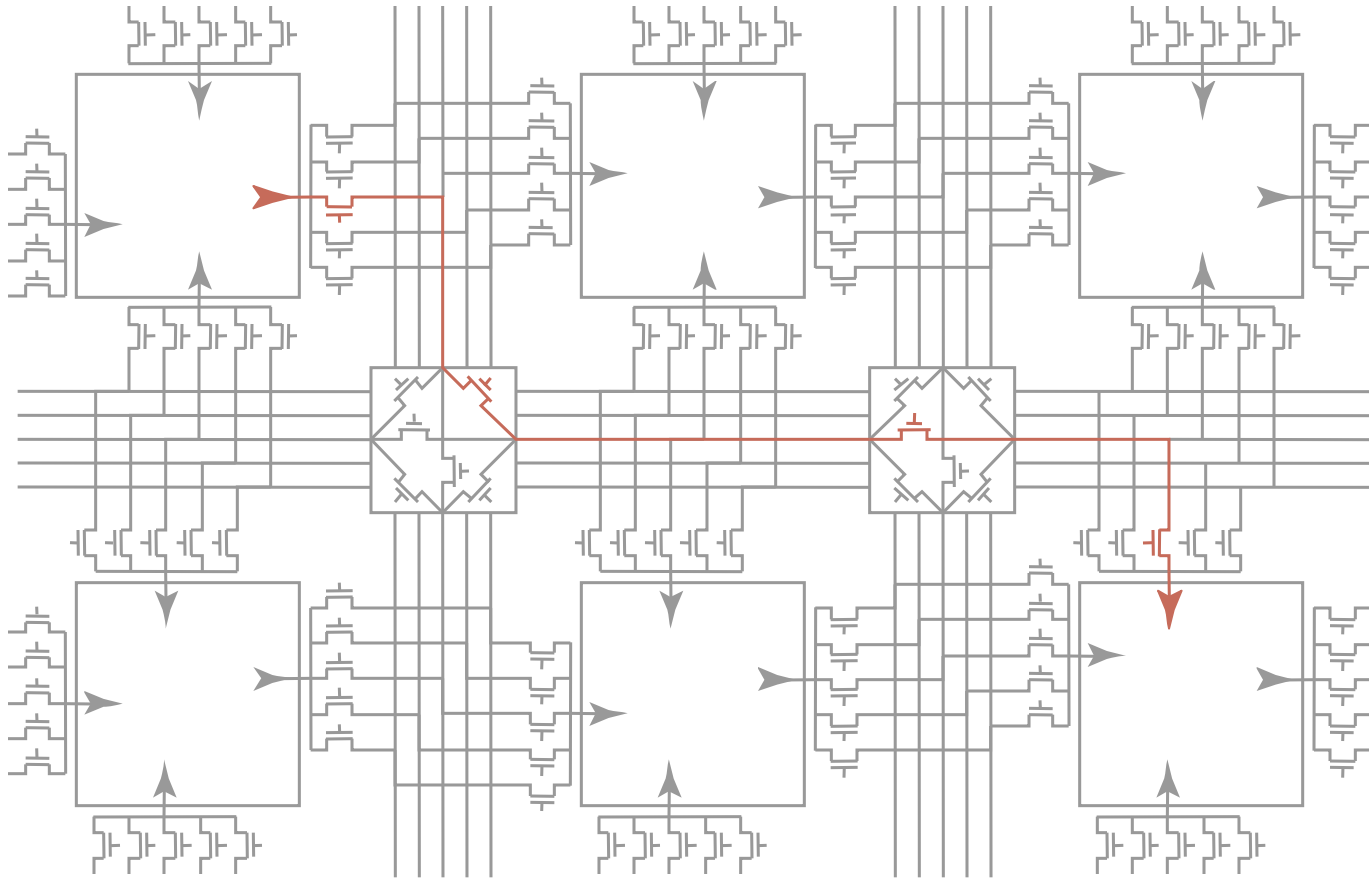
 
# Programming technology

- Must use a programmable technology to implement the reconfigurable parts



# Programmable parts


- PAL and PLA connection points
  - Multiplexers
  - Interconnects among different components in a programmable chip
  - Lookup table entries
- These parts will be introduced soon!

# Programming technologies

- How the programmable parts are constructed
- Three major technologies
  - SRAM+ transistor switches
  - ROM
  - Antifuse


 
# Programming technology- SRAM

Recall the transistor functionality as a switch



  
# Programming technology- SRAM

- The switch should be controlled by some memory element
  - To keep the configuration
- A Static Random Access Memory (SRAM) is used
  - Each switch is a pass transistor controlled by the state of an SRAM bit
  - Needs to be configured at power-on



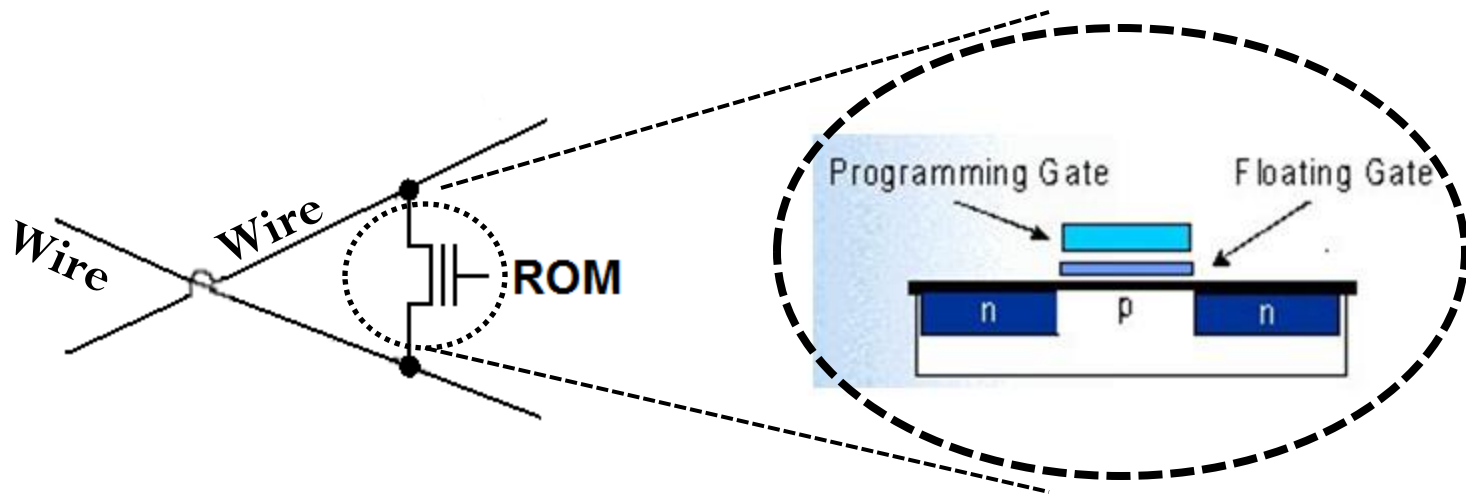
# Programming technology- ROM

- Flash Erasable Programmable ROM (Flash)
  - Device itself holds the program
  - Reprogrammable, even in-circuit
  - The configuration is kept, even if the circuit is shut down


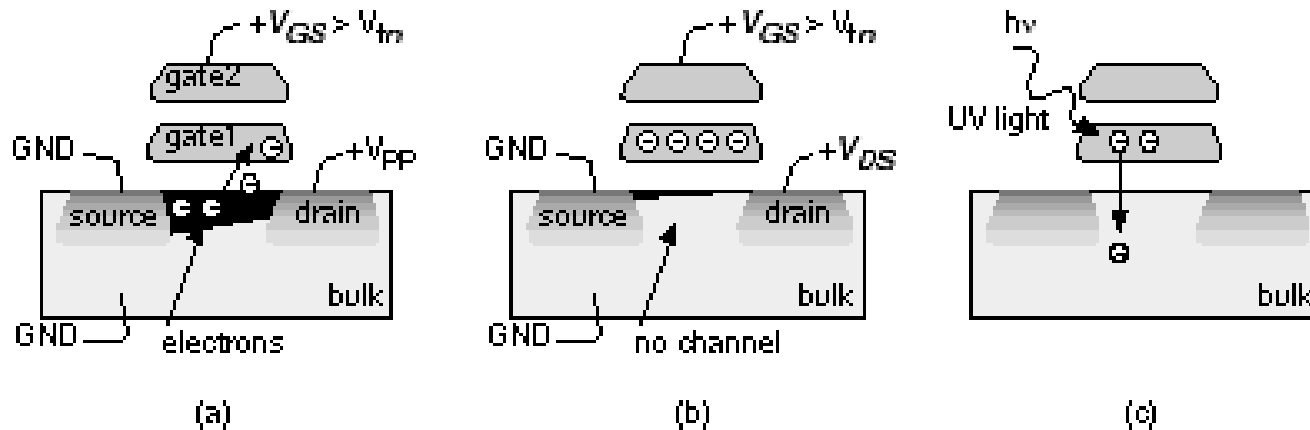
# Programming technology- ROM


- ROM: a transistor switch has an additional floating-gate
  - Can be turned off by injecting negative charge onto the floating gate: negative charge prevents channel formation
  - Can be turned on by discharging the floating gate
- EPROM: discharging by UV light
- EEPROM: discharging by electrical voltage





 
# Programming technology- Antifuse

- Fusible Links (“Antifuse”)
  - Forms a low resistance path when electrically programmed
- Lower area and higher speed than SRAM and ROM
- Once the fuse is programmed, the state never changes
  - One-time programmable



 
# FPGA market

- Several companies produce FPGAs and CPLDs
- Two major companies: Altera and Xilinx



source: <http://www.fpgadeveloper.com>

# FPGA example: Xilinx Spartan-II

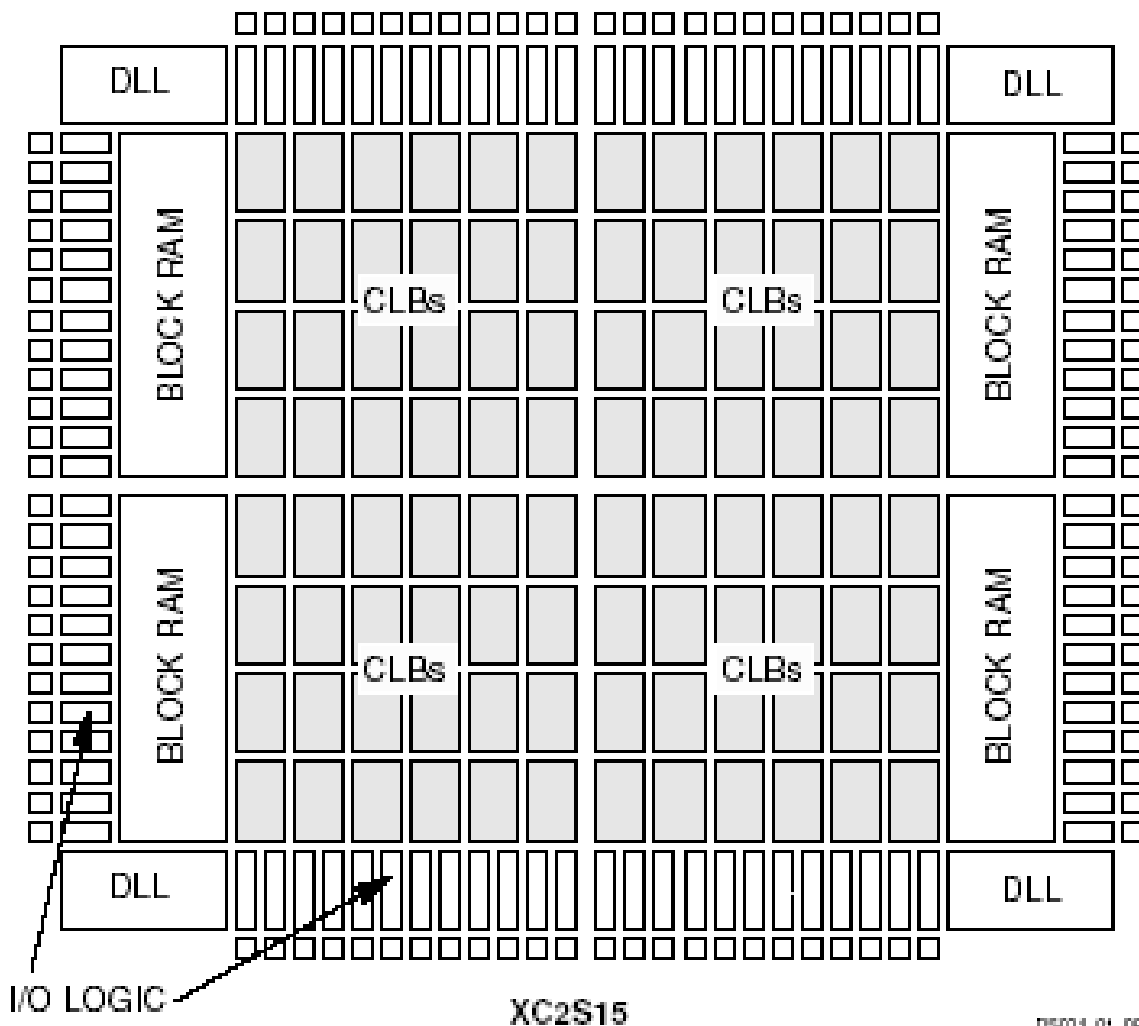

# FPGA example: Altera Apex 20K

