

ECE381(CAD), Lecture 14:

# Design Example- pipeline

Mehdi Modarressi




Department of Electrical and Computer Engineering,  
University of Tehran

# Introduction


- Pipelining a datapath
- Reading:
  - “Designers Guide To VHDL”: chapter 6
   
# Pipeline

- Pipelining is Natural!
- A laundry with 4 loads
  - Washer takes 30 minutes
  - Dryer takes 40 minutes
  - Folder takes 20 minutes




# Sequential laundry

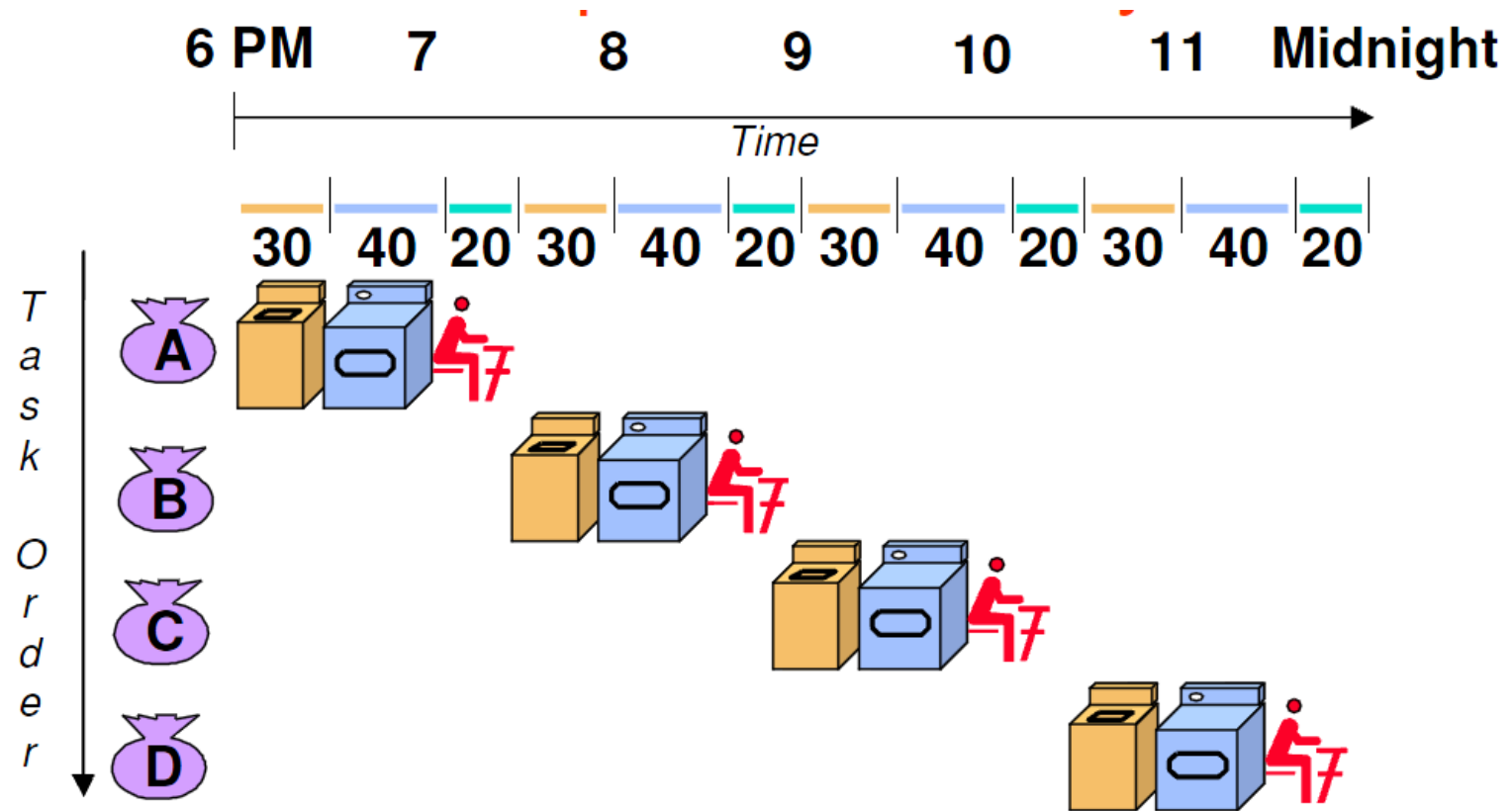

- Will take 6 hours

# Pipelined laundry

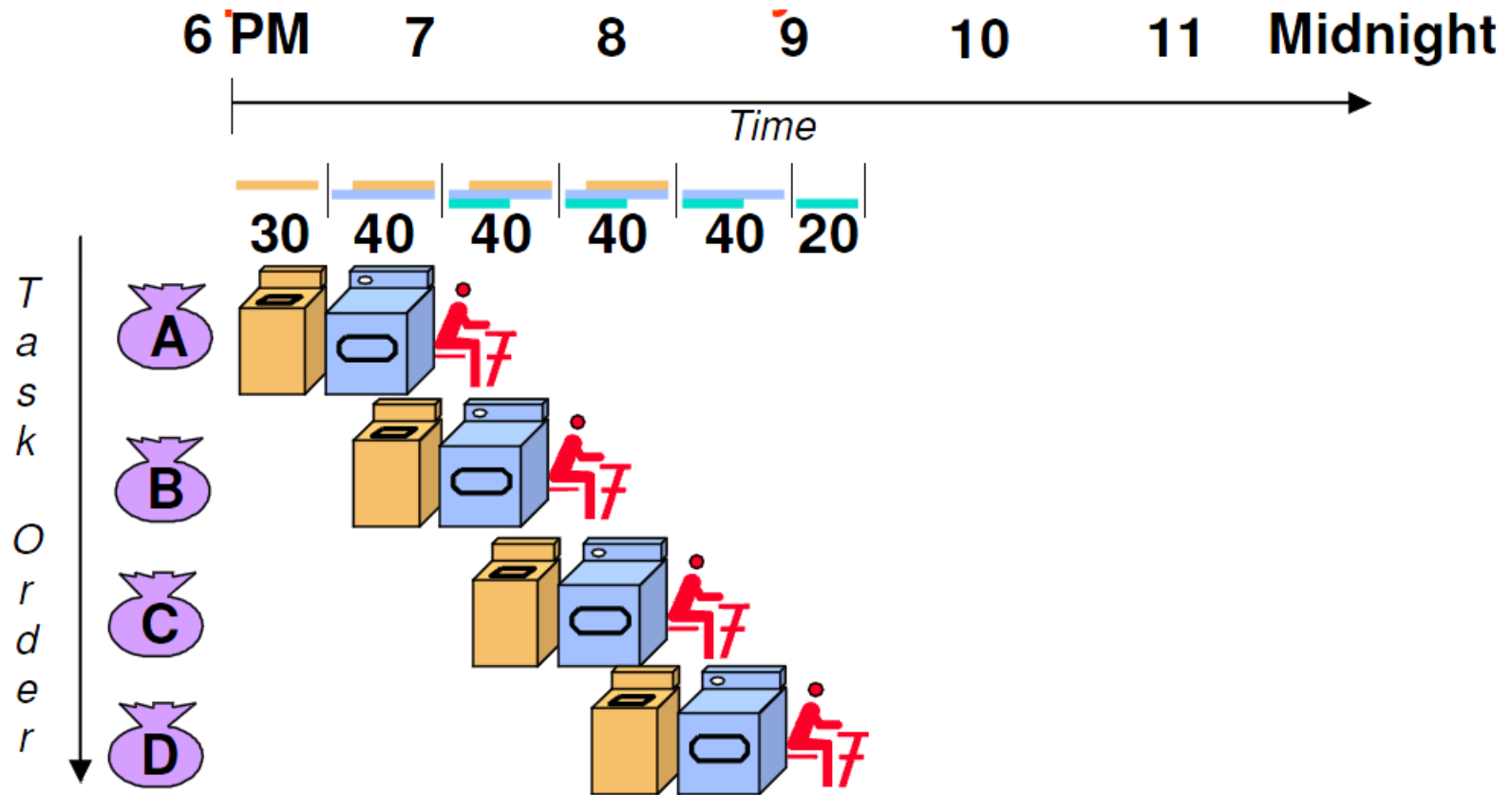

- Will take 3.5 hours

# Pipelining

- Pipelining doesn't reduce single task latency
  - It helps throughput of entire System
- Latency
  - Time from start of task to end of that task
- Throughput
  - The number of completed tasks per time unit
- Pipeline rate limited by slowest pipeline stage
- Potential speedup = Number pipe stages

# Pipeline

- Multiple tasks operating simultaneously using different resources

- **Sequential**



- **Pipelined**



# Pipeline vs parallel processing

- **Parallel**




Parallelism requires more hardware

- **Sequential and Pipelined have same hardware**




 - **Pipelined schedule, not hardware units**





# Pipeline

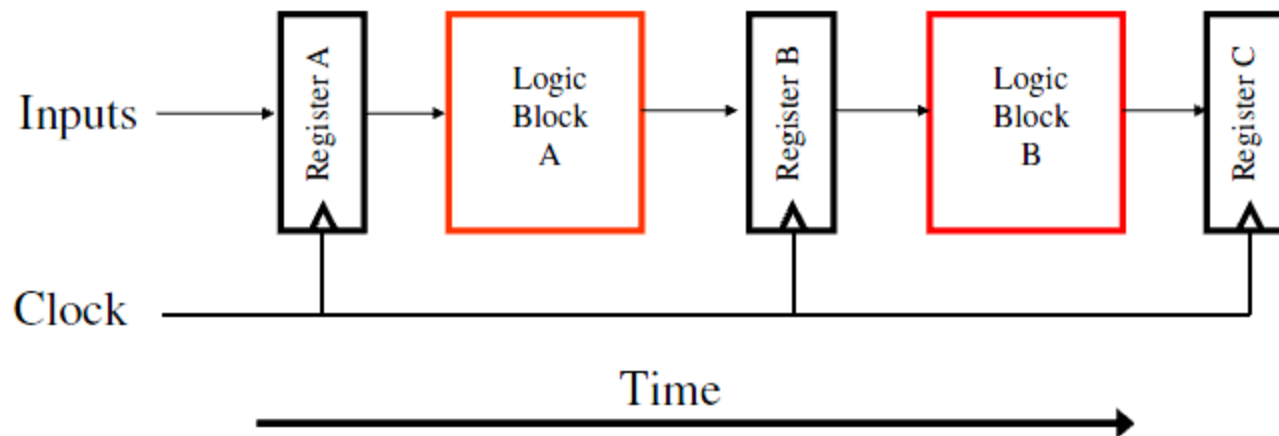

- Datapath + staging registers

# Pipeline example: MAC

- A pipelined multiplier accumulator (MAC) for a stream of complex numbers
  - Many digital signal processing algorithms
- A complex MAC operates on two sequences of complex numbers
  - Multiplies corresponding elements of the sequences and accumulates the sum of the products

$$\sum_{i=1}^N x_i y_i$$

Multiplication of x and y:

$$p_{\text{real}} = x_{\text{real}} \times y_{\text{real}} - x_{\text{imag}} \times y_{\text{imag}}$$

$$p_{\text{imag}} = x_{\text{real}} \times y_{\text{imag}} + x_{\text{imag}} \times y_{\text{real}}$$


sum of x and y:

$$s_{\text{real}} = x_{\text{real}} + y_{\text{real}}$$

$$s_{\text{imag}} = x_{\text{imag}} + y_{\text{imag}}$$

# MAC diagram

- MAC without pipelining

 

$$p_{\text{real}} = x_{\text{real}} \times y_{\text{real}} - x_{\text{imag}} \times y_{\text{imag}}$$



$$p_{\text{imag}} = x_{\text{real}} \times y_{\text{imag}} + x_{\text{imag}} \times y_{\text{real}}$$

$$s_{\text{real}} = x_{\text{real}} + y_{\text{real}}$$

$$s_{\text{imag}} = x_{\text{imag}} + y_{\text{imag}}$$
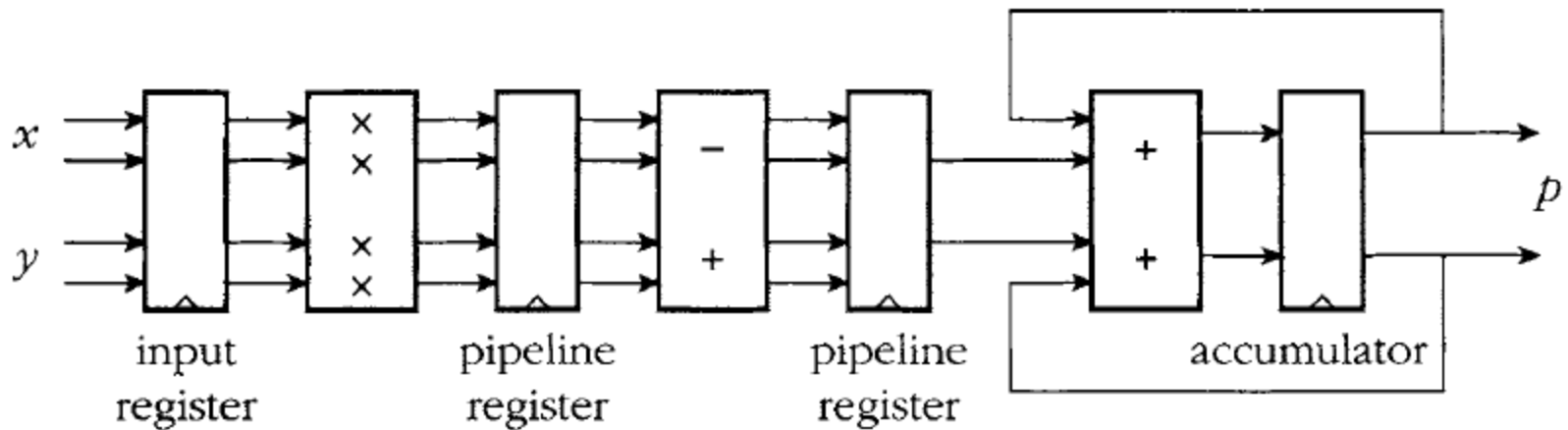 
# MAC diagram

- MAC with (bottom) and without (up) pipelining



# MAC entity declaration

```
library ieee; use ieee.std_logic_1164.all;
```


```
entity mac is
```

```
  port ( clk, clr : in std_logic;
        x_real : in std_logic_vector(15 downto 0);
        x_imag : in std_logic_vector(15 downto 0);
        y_real : in std_logic_vector(15 downto 0);
        y_imag : in std_logic_vector(15 downto 0);
        s_real : out std_logic_vector(15 downto 0);
        s_imag : out std_logic_vector(15 downto 0);
        ovf : out std_logic );
```

```
end entity mac;
```

$$p_{\text{real}} = x_{\text{real}} \times y_{\text{real}} - x_{\text{imag}} \times y_{\text{imag}}$$
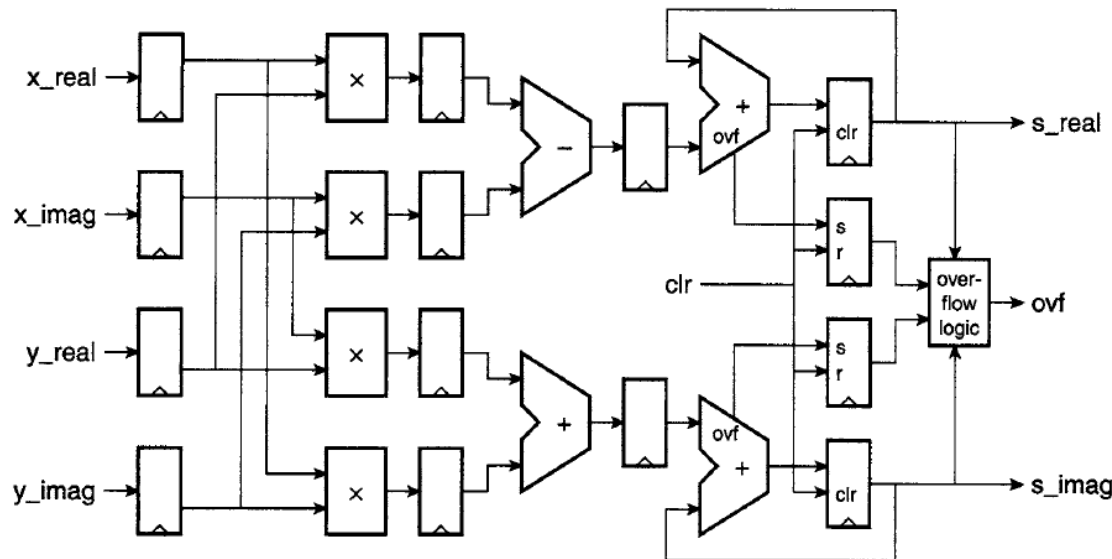
$$p_{\text{imag}} = x_{\text{real}} \times y_{\text{imag}} + x_{\text{imag}} \times y_{\text{real}}$$



More detailed  
structural diagram of  
MAC

# Conversion entities

- The ports are *std\_logic\_vector*, but the operations are to be made on *real* numbers

```
library ieee; use ieee.std_logic_1164.all;
entity mac is
  port ( clk, clr : in std_ulogic;
        x_real : in std_ulogic_vector(15 downto 0);
        x_imag : in std_ulogic_vector(15 downto 0);
        y_real : in std_ulogic_vector(15 downto 0);
        y_imag : in std_ulogic_vector(15 downto 0);
        s_real : out std_ulogic_vector(15 downto 0);
        s_imag : out std_ulogic_vector(15 downto 0);
        ovf : out std_ulogic );
end entity mac;
```

```
library ieee; use ieee.std_logic_1164.all;
entity to_fp is
  port ( vec : in std_ulogic_vector(15 downto 0);
        r : out real );
end entity to_fp;
```

```
library ieee; use ieee.std_logic_1164.all;
entity to_vector is
  port ( r : in real;
        vec : out std_ulogic_vector(15 downto 0) );
end entity to_vector;
```

**architecture behavioral of mac is**

**constant** Tpd\_clk\_out : time := 3 ns;

**signal** fp\_x\_real, fp\_x\_imag,  
fp\_y\_real, fp\_y\_imag,  
fp\_s\_real, fp\_s\_imag : real := 0.0;

**begin**

x\_real\_converter : **entity** work.to\_fp(behavioral)  
**port map** ( x\_real, fp\_x\_real );

x\_imag\_converter : **entity** work.to\_fp(behavioral)  
**port map** ( x\_imag, fp\_x\_imag );

y\_real\_converter : **entity** work.to\_fp(behavioral)  
**port map** ( y\_real, fp\_y\_real );

y\_imag\_converter : **entity** work.to\_fp(behavioral)  
**port map** ( y\_imag, fp\_y\_imag );

s\_real\_converter : **entity** work.to\_vector(behavioral)  
**port map** ( fp\_s\_real, s\_real );

s\_imag\_converter : **entity** work.to\_vector(behavioral)  
**port map** ( fp\_s\_imag, s\_imag );

Converter components are placed between the inputs and MAC structure to convert data

Direct instantiation—no component definition is needed

# The main process

behavior : **process** (clk) is

```
variable input_x_real, input_x_imag, input_y_real, input_y_imag : real := 0.0;  
variable real_part_product_1, real_part_product_2,  
          imag_part_product_1, imag_part_product_2 : real := 0.0;  
variable real_product, imag_product : real := 0.0;  
variable real_sum, imag_sum : real := 0.0;  
variable real_accumulator_ovf, imag_accumulator_ovf : boolean := false;  
type boolean_to_stdulogic_table is array (boolean) of std_ulogic;  
constant boolean_to_stdulogic : boolean_to_stdulogic_table  
          := (false => '0', true => '1');
```

**begin**



# Main PROCESS- handling reset

```
if rising_edge(clk) then  
    -- work from the end of the pipeline back to the start, so as  
    -- not to overwrite previous results in pipeline registers before  
    -- they are used  
    -- update accumulator and generate outputs  
    if To_X01(clr) = '1' then  
        real_sum := 0.0;  
        real_accumulator_ovf := false;  
        imag_sum := 0.0;  
        imag_accumulator_ovf := false;  
    else  
        .  
        .  
        .
```

behavior : **process** (clk) is

⋮  
**if** rising\_edge(clk) **then**

**if** To\_X01(clr) = '1' **then**

        ⋮  
    **else**

        real\_sum := real\_product + real\_sum;

        real\_accumulator\_ovf := real\_accumulator\_ovf

**or** real\_sum < -16.0

**or** real\_sum >= +16.0;

        imag\_sum := imag\_product + imag\_sum;


        imag\_accumulator\_ovf := imag\_accumulator\_ovf

**or** imag\_sum < -16.0

**or** imag\_sum >= +16.0;

**end if;**

    ⋮

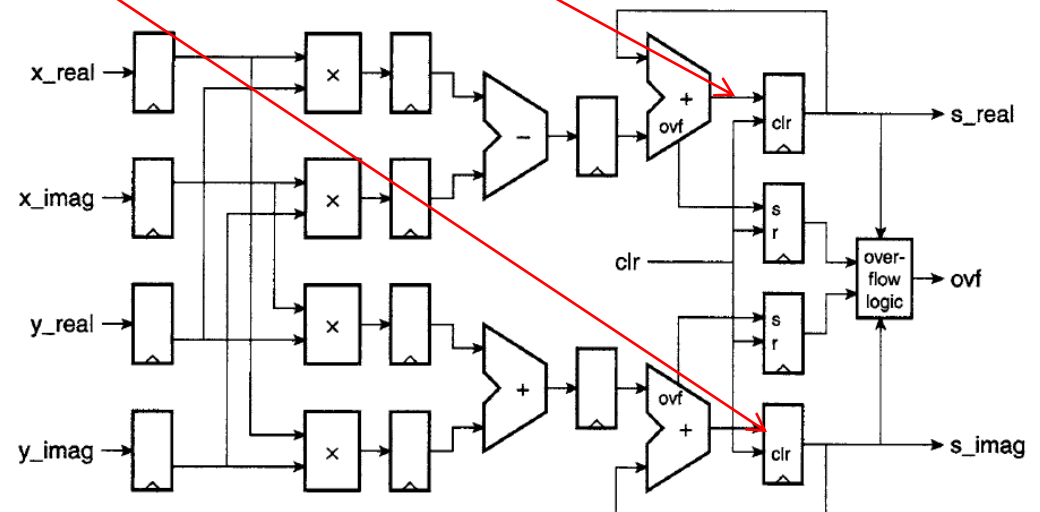

behavior : **process** (clk) is

⋮

*-- update product registers using partial products*

real\_product := real\_part\_product\_1 - real\_part\_product\_2;

imag\_product := imag\_part\_product\_1 + imag\_part\_product\_2;

*-- update partial product registers using latched inputs*

real\_part\_product\_1 := input\_x\_real \* input\_y\_real;

real\_part\_product\_2 := input\_x\_imag \* input\_y\_imag;

imag\_part\_product\_1 := input\_x\_real \* input\_y\_imag;

imag\_part\_product\_2 := input\_x\_imag \* input\_y\_real;

*-- update input registers using MAC inputs*


input\_x\_real := fp\_x\_real;

input\_x\_imag := fp\_x\_imag;

input\_y\_real := fp\_y\_real;

input\_y\_imag := fp\_y\_imag;

**end process** behavior;

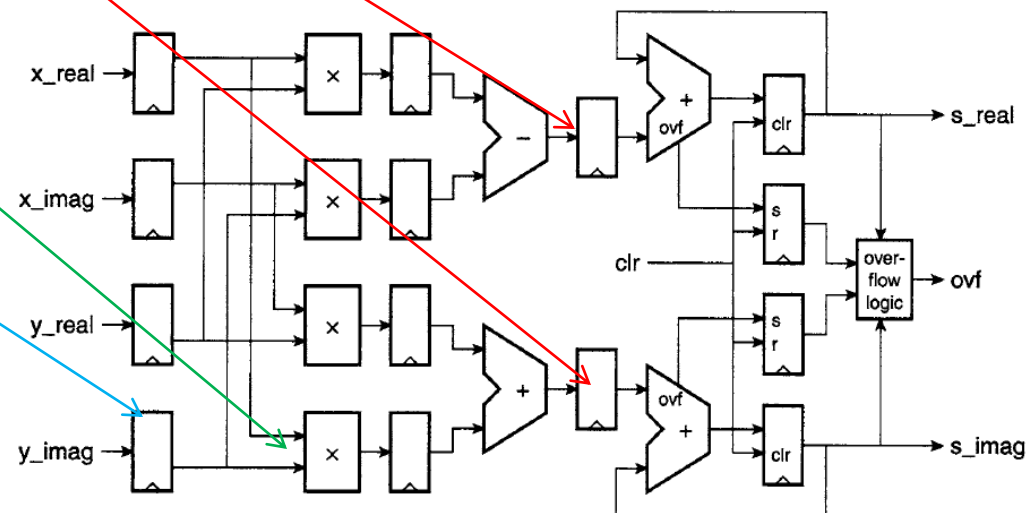

```

-- update product registers using partial products
real_product := real_part_product_1 - real_part_product_2;
imag_product := imag_part_product_1 + imag_part_product_2;


-- update partial product registers using latched inputs
real_part_product_1 := input_x_real * input_y_real;
real_part_product_2 := input_x_imag * input_y_imag;
imag_part_product_1 := input_x_real * input_y_imag;
imag_part_product_2 := input_x_imag * input_y_real;

-- update input registers using MAC inputs
input_x_real := fp_x_real;
input_x_imag := fp_x_imag;
input_y_real := fp_y_real;
input_y_imag := fp_y_imag;

```

**end if;**  
**end process** behavior;

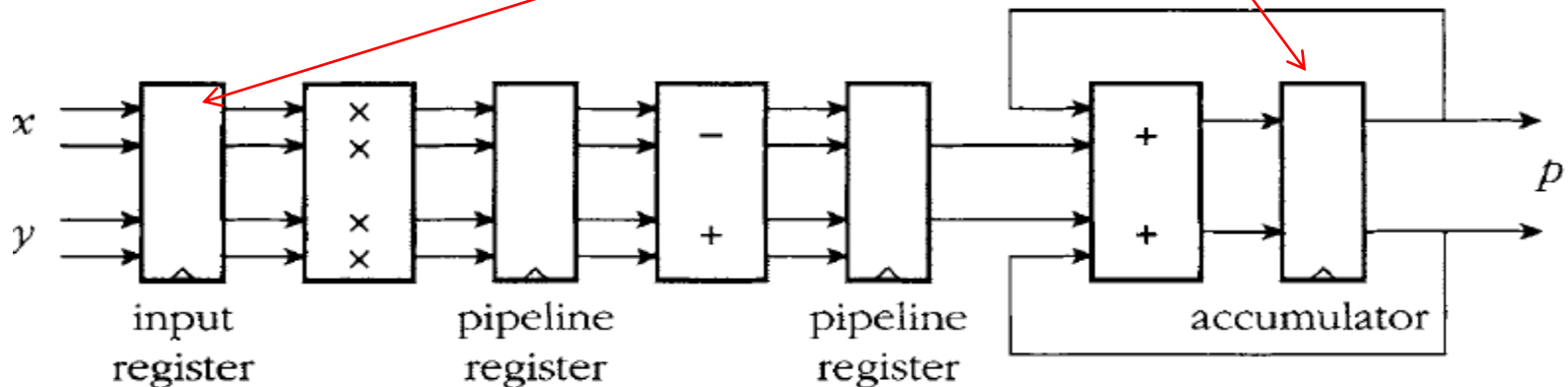Start from the last register and calculate the result  
 (input of the next register) based on inputs.  
 Why starting from the last one? Why don't we start  
 from the first register?



# Generating final output

```
fp_s_real <= real_sum after Tpd_clk_out;  
fp_s_imag <= imag_sum after Tpd_clk_out;  
ovf <= boolean_to_stdulogic(  
    real_accumulator_ovf or imag_accumulator_ovf  
    or real_sum < -1.0 or real_sum >= +1.0  
    or imag_sum < -1.0 or imag_sum >= +1.0 )  
    after Tpd_clk_out;
```

# Reference

- See chapter 6 of “The designers guide to VHDL” for a complete design

# Exercise

- Write a VHDL code to implement a pipelined datapath with highest throughput for  $f$ . Assume the latency of the addition, multiplication, and division operations are 12, 45, and 50 ns, respectively. The register latency is 2 ns. Use the *real* data type for the ports and predefined VHDL operations for *real* in the low-level entities.

$$f = ((a \times b + c \times d) / d)^2$$